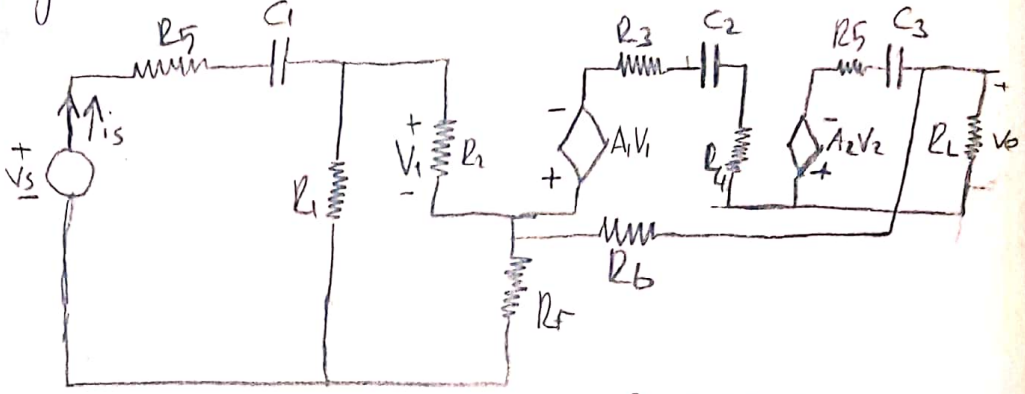



Q1 : The feedback amplifier in Fig P.10.13 has $A_1 = 50$

Amir

$A_2 = 60$, $R_3 = 500\Omega$, $R_1 = 15k\Omega$, $R_2 = 1.5k\Omega$, $R_3 = 250\Omega$, $R_4 = 1.5k\Omega$,
 $R_5 = 250\Omega$, $R_6 = 2k\Omega$, $R_L = 4.7k\Omega$, $R_F = 500\Omega$ $C_1 = C_2 = C_3 = 0.1\mu F$ and $V_S = 100mV$
 Determine (a) the input resistance $R_{if} = V_S / i_S$ (b) the output resistance R_{of} ,
 and (c) the overall voltage gain of $A_f = V_o / V_S$. Assume C_1 , C_2 and C_3 are shorted.
 at the operating frequency



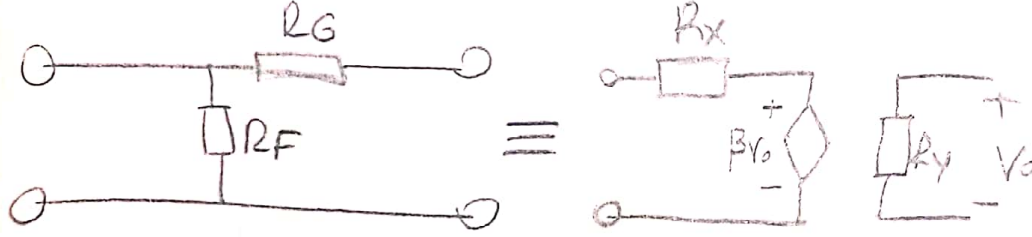Öncelikle bu bir voltage amplifier olduğundan voltage-series feedback yapıyoruz




$$R_x = R_F \parallel R_G$$

$$R_y = R_F + R_G$$

$$\beta = \frac{R_F}{R_F + R_G}$$

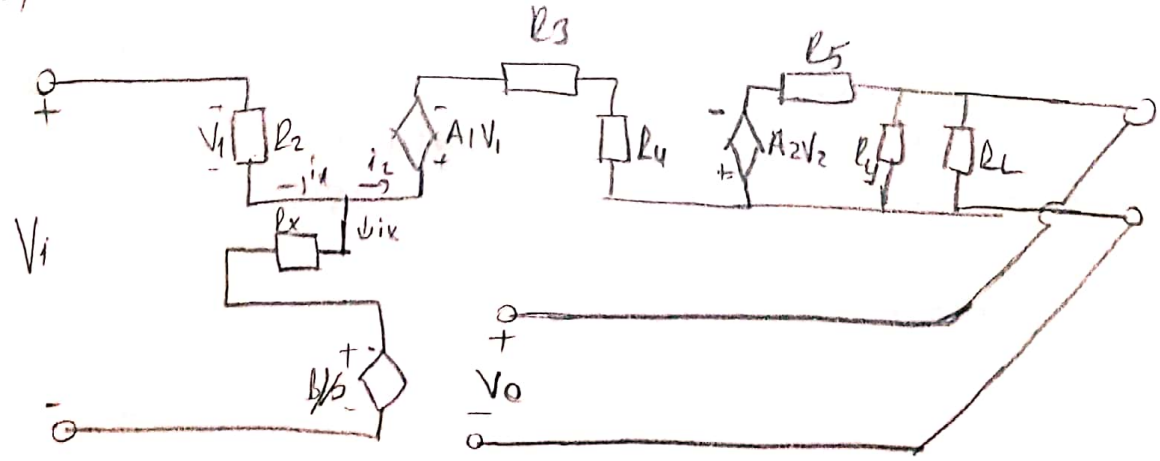V.A.f'l Sematigi (feedback-loaded voltage Amplifier and the idealized feedback network)



VA. fl analizir $\beta = 0$ için (Amag: $\frac{V_1}{V_i} = ?$ $\frac{V_2}{V_i} = ?$ $\frac{V_i}{V_1} = ?$)

Mesh analysis

$$V_i - V_1 - A_1 V_1 - (R_3 + R_4) i_2 = 0$$

$$V_i - V_1 - i_2 R_x = 0$$

Node Analysis

$$\bar{i}_1 = \bar{i}_2 + \bar{i}_x$$

$$V_1 = \bar{i}_1 R_2$$

$$V_2 = \bar{i}_2 R_4$$

$$V_i = (1 + A_1) V_1 + (R_3 + R_4) i_2$$

$$\frac{V_1}{R_2} = \bar{i}_2 + \bar{i}_x$$

$$\frac{V_i - V_1}{R_x} = \bar{i}_x$$

$$V_i \left[1 + \frac{R_3 + R_4}{R_x} \right] = V_1 \left[1 + A_1 + \frac{R_3 R_4}{R_2 \parallel R_x} \right]$$

$$\Rightarrow \frac{V_1}{V_i} = \frac{\left[1 + \frac{R_3 + R_4}{R_x} \right]}{\left[(1 + A_1) + \left(\frac{R_3 + R_4}{R_2 \parallel R_x} \right) \right]} \quad \star$$

$$\frac{V_1}{V_i} = \frac{\bar{i}_1 R_2}{V_i} \Rightarrow \frac{V_1}{\bar{i}_1} = \frac{V_i}{V_1} \cdot R_2$$

$$\frac{V_i}{V_1} = \left(\frac{V_1}{V_i} \right)^{-1} \Rightarrow \frac{V_i}{\bar{i}_1} = R_2 \cdot \frac{\left[(1 + A_1) + \left(\frac{R_3 + R_4}{R_2 \parallel R_x} \right) \right]}{\left[1 + \frac{R_3 + R_4}{R_x} \right]} \quad \star$$

$$\frac{V_2}{V_i} = \frac{R_4 i_2}{V_i} = \frac{R_4}{V_i} \left[\frac{V_1}{R_2} - \frac{V_i - V_1}{R_x} \right] \leftarrow \bar{i}_2 = \left[\frac{V_1}{R_2} - \frac{V_i - V_1}{R_x} \right]$$

$$= \frac{R_4}{V_i} \left[\frac{V_1}{R_2 \parallel R_x} - \frac{V_i}{R_x} \right]$$

$$= \frac{R_4}{V_i} \cdot \frac{V_1}{R_2 \parallel R_x} - \frac{R_4 \cdot V_i}{V_i \cdot R_x}$$

$$\frac{V_1}{R_2} + \frac{V_1}{R_x} - \frac{V_i}{R_x}$$

$$\frac{V_1}{R_2 \parallel R_x} - \frac{V_i}{R_x}$$

$$\frac{V_2}{V_1} = \frac{R_4}{R_2 \parallel R_x} \cdot \left[\frac{\left[1 + \frac{R_3 + R_4}{R_x} \right]}{\left[(1 + A_1) + \left(\frac{R_3 + R_4}{R_2 \parallel R_x} \right) \right]} \right] - \frac{R_4}{R_x} < 0$$

$$\approx \frac{1.5k}{1.5k \parallel R_x} \cdot \left[\frac{1 + \frac{1750}{R_x}}{51 + \frac{1750}{R_x \parallel 1.5k}} \right] \cdot \frac{V_1}{V_i} \rightarrow \frac{1.5k}{R_x} < 0$$

$$R_4 = 1.5k\Omega$$

$$R_2 = 1.5k\Omega$$

$$R_3 = 250\Omega$$

$$A_1 = 50$$

$$R_x$$

$$\Rightarrow \frac{1500 \cdot (1500 + R_x)}{1500 R_x} \cdot \left[\frac{\frac{R_x + 1750}{R_x}}{51 + \frac{1750(1500 + R_x)}{1500 R_x}} \right] < \frac{1500}{R_x}$$

$$= \frac{(1500 + R_x)}{1500} \cdot \left[\frac{(R_x + 1750) \cdot 1500 R_x}{R_x \cdot ((51 \cdot 1500 R_x) + 1750(1500 + R_x))} \right] < 1$$

$$= \frac{(1500 + R_x)(1750 + R_x)}{76500 R_x + 2,625 \times 10^6 + 1750 R_x} < 1$$

$$= (R_x)^2 + 3250 R_x + 2,625 \times 10^6 < 2,625 \times 10^6 + 78250 R_x$$

$$= (R_x)^2 - 75000 R_x < 0$$

$$(R_x) \cdot (R_x - 75000) < 0$$

$$0 < R_x < 75k\Omega \text{ için}$$

$$\frac{V_2}{V_i} < 0 \text{ olduğu belirlenmiştir.}$$

(3)

$$\frac{V_o}{V_2} = (-A_2) \frac{R_y \parallel R_L}{R_y \parallel R_L + R_5} < 0 \text{ if } A_2 > 0$$

then

$$\frac{V_o}{V_i} = \frac{V_2}{V_i} \cdot \frac{V_o}{V_2} = A_{VA,fl}$$

$$A_{VA,fl} = \left[\frac{R_4}{R_2 \parallel R_x} \cdot \underbrace{\left[\frac{(1 + \frac{R_3 + R_4}{R_x})}{(1 + A_1) + (\frac{R_3 + R_4}{R_2 \parallel R_x})} \right]}_{< 0} - \frac{R_4}{R_x} \right] \cdot \underbrace{(-A_2) \frac{R_y \parallel R_L}{R_y \parallel R_L + R_5}}_{< 0}$$


$$R_{out,VA,fl} = R_5 \parallel R_y \parallel R_L$$

$$A_{VA,fl} > 0$$

Theoritz formiller

$$A_f = \frac{A_{VA,fl}}{1 + \beta A_{VA,fl}}, \quad r_{in,f} = (1 + \beta A_{VA,fl}) r_{in,VA,fl}$$

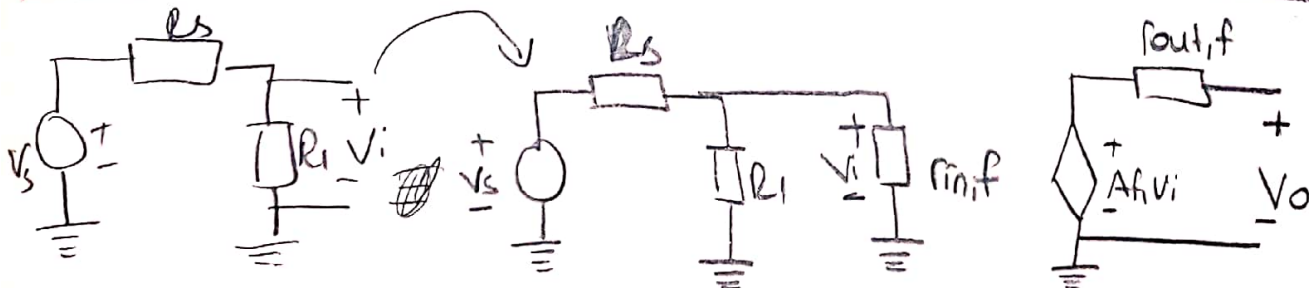
$$R_{out,f} = \frac{R_{out,VA,fl}}{1 + \beta A_{VA,fl}}$$



$$\frac{V_o}{V_s} = \frac{r_{in,f} \parallel R_1}{r_{in,f} \parallel R_1 + R_s} \cdot A_f$$


4

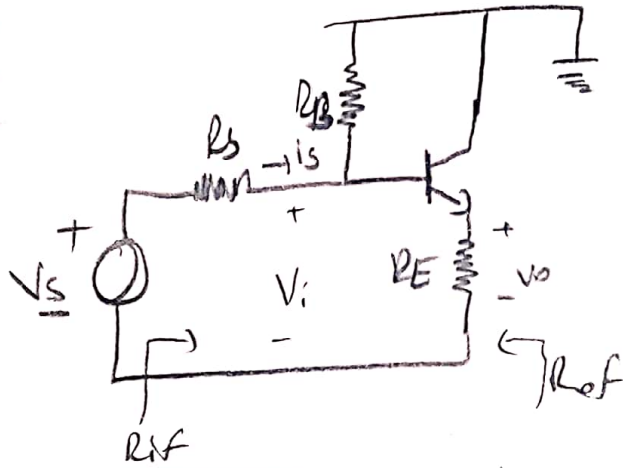Q2) The emitter follower in Fig P.10.18 has $R_B = 75k\Omega$, $R_E = 750\Omega$, $R_L = 1k\Omega$ and $R_S = 250\Omega$. The transistor parameters are $h_{fe} = 150$, $r_{\pi} = 250\Omega$, and $r_o = r_{\infty}$. Draw a block diagram of the feedback mechanism. Use the techniques of feedback analysis to calculate (a) input resistance (b) the output resistance R_{of} , and (c) the close loop voltage gain A_f .





- small signal esdegeri ulz.
- voltage amp. için voltage-series feedback. parametreleri bul.
- Feedback network duzden analizi gerceklestin. direct amplifier için sonucu bul.
- Feedback network ile parametreleri bul.

Small signal esdegeri


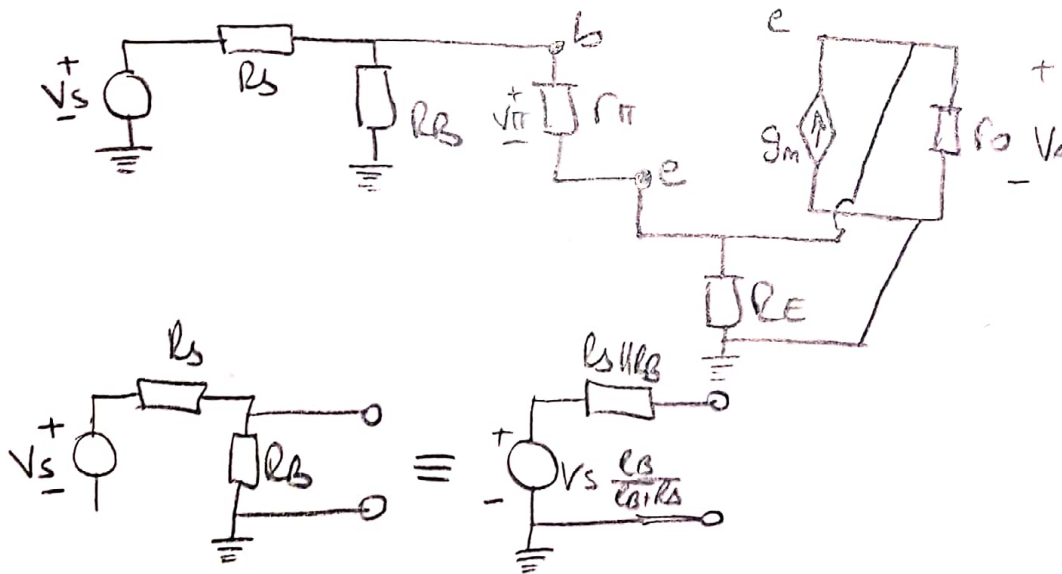


Feedback network analizi

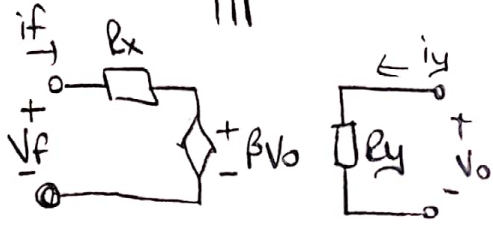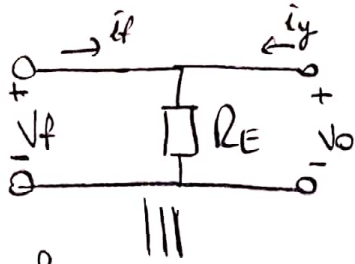

$$\beta = \frac{V_f}{V_o} \Big|_{i_f=0} = 1 \quad R_y = \frac{V_o}{i_y} \Big|_{i_f=0} = R_E$$

$$R_x = \frac{V_f}{i_f} \Big|_{V_o=0} = 0$$

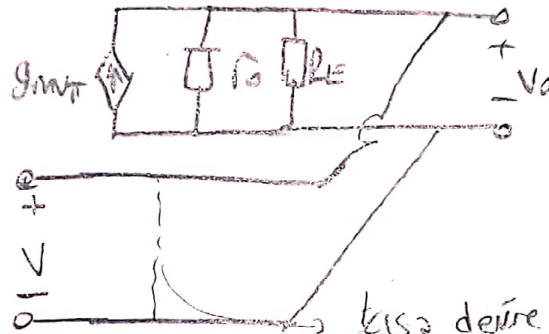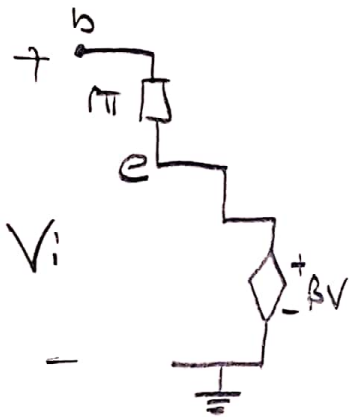

kısa devre yapılarak $V=0 \Rightarrow \beta V=0$
(Analiz için) $V_i = V_{\pi}$ sağlanır

$$A_{VA,fl} = g_m(r_o \parallel R_E)$$

$$r_{in,VA,fl} = r_{\pi}$$

$$r_{out,VA,fl} = r_o \parallel R_E$$

eq.1

$$A_f = \frac{g_m(r_o \parallel R_E)}{1 + g_m(r_o \parallel R_E)}$$

eq.2

$$r_{in,f} = r_{\pi}(1 + g_m(r_o \parallel R_E))$$

eq.3

$$r_{out,f} = \frac{r_o \parallel R_E}{1 + g_m(r_o \parallel R_E)}$$

$r_o \gg R_E$
için

$\beta = 1$ için

$$A_f = \frac{A_{VA,fl}}{1 + A_{VA,fl} \cdot \beta} \quad \text{eq.1}$$

$$r_{in,f} = r_{in,VA,fl}(1 + A_{VA,fl} \cdot \beta) \quad \text{eq.2}$$

$$r_{out,f} = \frac{r_{out,VA,fl}}{1 + A_{VA,fl} \cdot \beta} \quad \text{eq.3}$$


$$A_f = \frac{g_m R_E}{1 + g_m R_E}$$

$$r_{in,f} = r_{\pi}(1 + g_m R_E)$$

$$r_{out,f} = \frac{R_E}{1 + g_m R_E}$$


(6)

feedback bağlantılı analizi

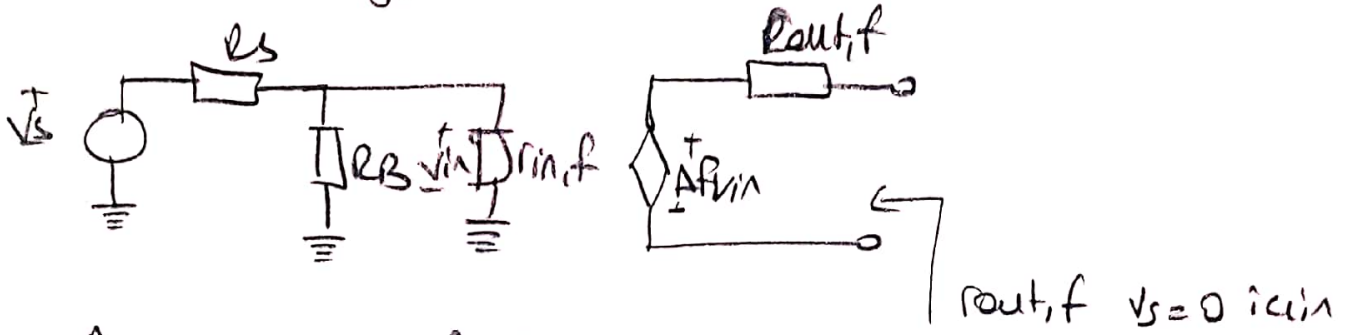

$$A_{realized} = \frac{r_{in,f} \parallel R_B}{r_{in,f} \parallel R_B + R_s} \cdot A_f$$


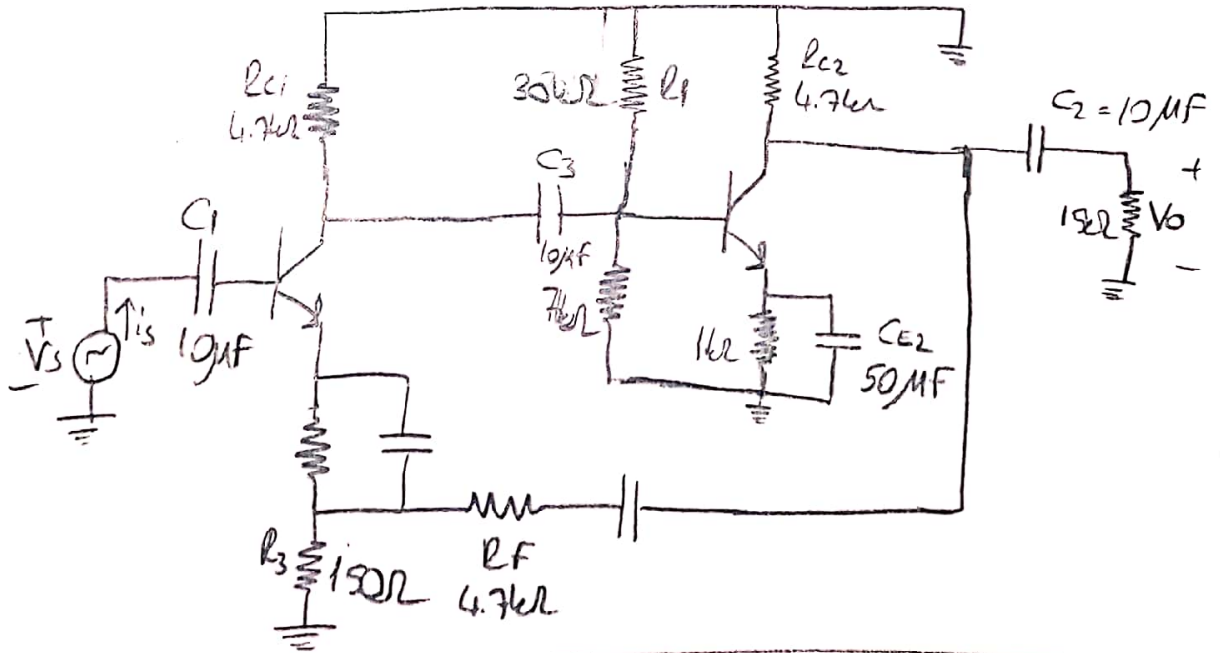
Q3: Use the techniques of feedback analysis to calculate the input resistance R_{in} , the output resistance R_{out} , and the closed loop voltage gain A_f of the amplifier in Fig P 10.19. The transistor parameters are $h_{fe} = h_{fe1} = h_{fe2} = 104$, $r_{\pi1} = r_{\pi2} = 2.5 \text{ k}\Omega$, $r_o = 1.5 \text{ k}\Omega$, $\beta = +\infty$



→ Voltage amplifier için feedback network modelle
 → direct amplifier parametrelerinin feedback loaded karşılıklarını bulmak için $A_{v,f}$ kur.
 → Kurulan $A_{v,f}$ 'yi analiz etmek. $A_{v,f}$, $r_{in,v,f}$ ve $r_{out,v,f}$ bul.

→ Devrenin tamamını analiz et $A_f = \frac{A_{v,f}}{1 + \beta A_{v,f}}$, $r_{in,f} = r_{in,v,f} \parallel (1 + \beta A_{v,f})$
 $r_{out,f} = \frac{r_{out,v,f}}{1 + \beta A_{v,f}}$

7

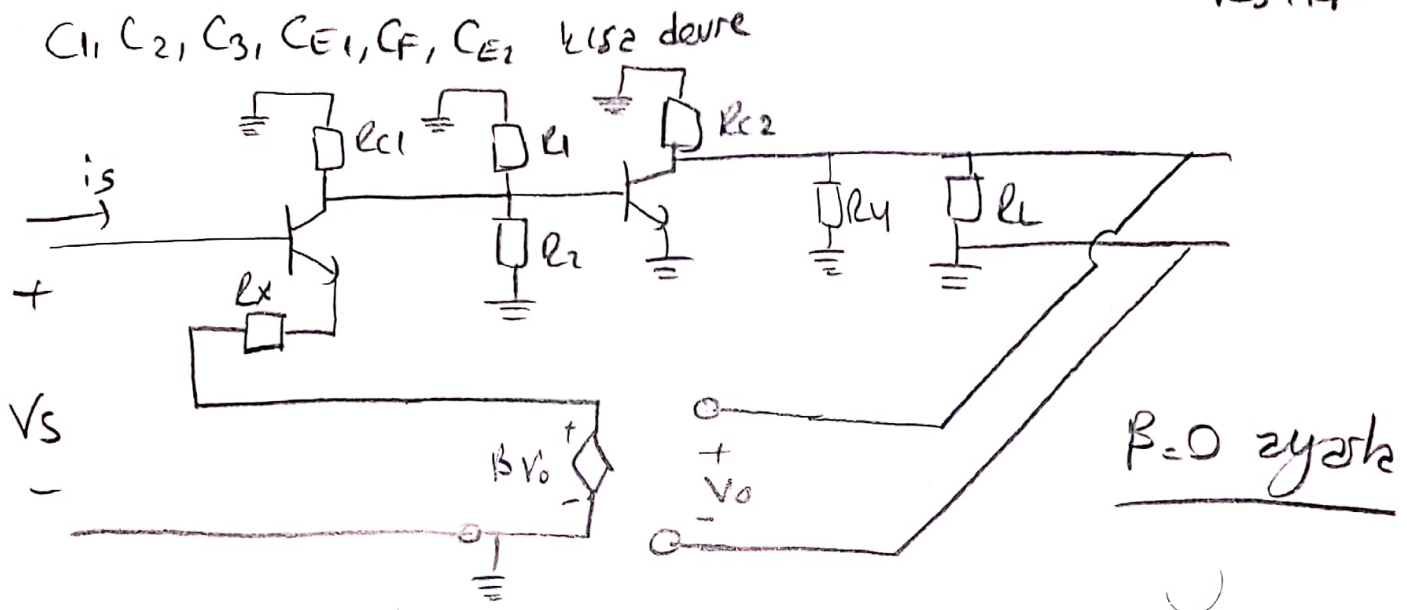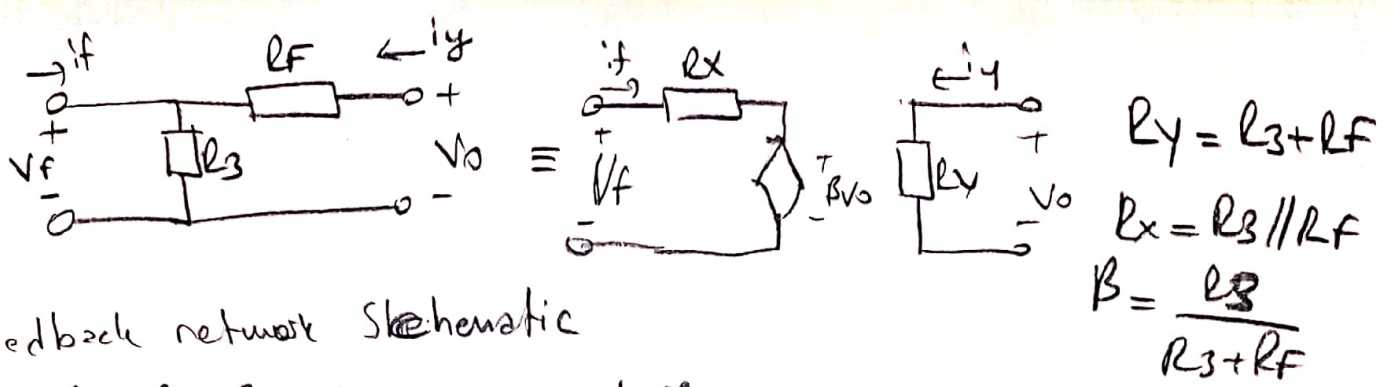

$$r_{in, VA, fl} = \frac{V_S}{i_S} \Big|_{i_O=0} = r_{\pi 1} (1 + g_{m1} R_X)$$

$$A_{VA, fl} = \frac{v_O}{V_S} \Big|_{i_O=0} = \left[\frac{-g_{m1}}{1 + g_{m1} R_X} \right] \left[R_{C1} \parallel R_{E1} \parallel R_{E2} \parallel r_{\pi 2} \parallel [r_{O1} (1 + g_{m1} R_X)] \right] \cdot [-g_{m2}] [R_{C2} \parallel r_{O2} \parallel R_L \parallel R_E]$$

$$R_{in, C1} = (r_{\pi 1} \parallel R_X) (1 + g_{m1} R_O)$$

$$R_{out, b2} = R_{E1} \parallel R_{E2} \parallel R_{C1} \parallel R_{in, C1}$$

$$r_{out, VA, fl} = R_{C2} \parallel R_{E4} \parallel R_{L1} \parallel R_O$$



feedback network is analize.

$$\beta = \frac{R_3}{R_3 + R_F} \quad A_F = \frac{A_{VA, fl}}{1 + \beta A_{VA, fl}} \quad , \quad r_{in, f} = r_{in, VA, fl} (1 + \beta A_{VA, fl})$$

$$r_{out, f} = \frac{r_{out, VA, fl}}{1 + \beta A_{VA, fl}}$$

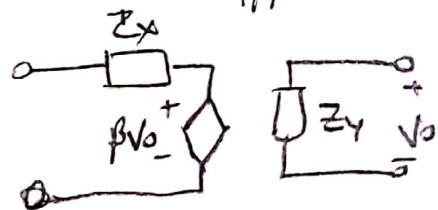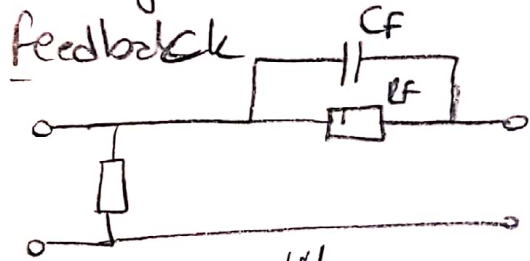Q4. The MOS Amplifier shown in fig P10.22 is biased to have the following small-signal MOS parameters: $g_{m1} = 1.2 \text{ mA/V}$, $r_{o1} = 25 \text{ k}\Omega$, $g_{m2} = 1.6 \text{ mA/V}$, and $r_{o2} = 25 \text{ k}\Omega$. If $R_{D1} = 1.5 \text{ k}\Omega$, then $R_{D2} = 1 \text{ k}\Omega$, $R_{SE} = 500 \Omega$, $R_F = 5 \text{ k}\Omega$ and $C_F = 20 \text{ pF}$. Determine (a) the voltage gain without feedback $A = V_o/V_s$, (b) the voltage gain with feedback A_f and (c) the feedback capacitor C_F to limit the high frequency $f_H = 50 \text{ kHz}$.

Voltage zup. i.e. voltage-series feedback



$$Z_x = \text{Parallel RC} \quad R_{SE} \parallel R_F \parallel C_F$$


$$Z_y = \parallel \quad R_{SE} + (R_F \parallel C_F)$$

$$B_S = \frac{R_{SE}}{R_{SE} + \frac{R_F \cdot \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}}} = \frac{R_{SE}}{R_{SE} + \frac{R_F}{1 + sR_FC_F}} = \frac{R_{SE}(1 + sR_FC_F)}{R_F + R_{SE} + sR_FC_F R_{SE}}$$

$$B_S = B_o \left(\frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \right)$$

$$= \frac{R_{SE}}{R_F + R_{SE}} \cdot \left[\frac{1 + \frac{s}{\frac{1}{R_FC_F} \rightarrow \omega_z}}{1 + \frac{s}{\frac{1}{C_F R_{SE}} \cdot \frac{R_{SE}}{R_F + R_{SE}} \rightarrow \omega_p}} \right]$$

(9)

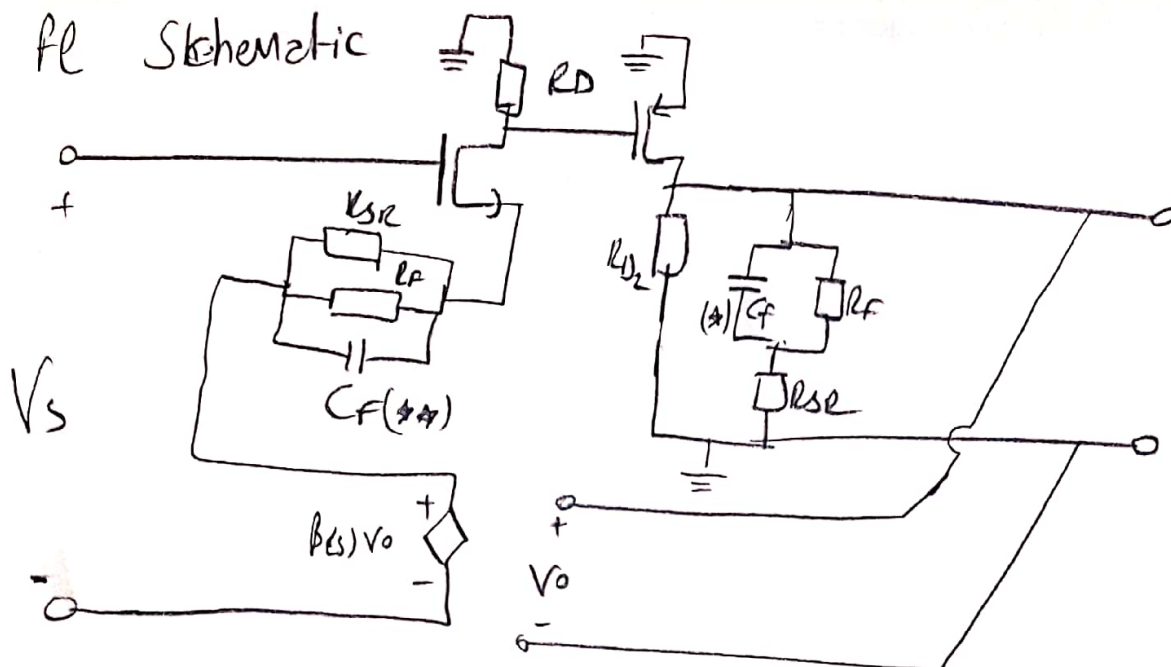

(**) $C_F = C_1$

$$R_1 = R_{sr} \parallel R_F \parallel \left[\frac{R_{D1} + r_{o1}}{1 + g_{m1} R_{D1}} \right]$$

$r_{o1} \gg R_{D1}$
 $g_{m1} R_{D1} \gg 1$

$$R_1 = \frac{r_{o1}}{g_{m1} R_{D1}} = \frac{1}{g_{m1}}$$

$$\tau_1 = R_1 \cdot C_1$$

$$\tau_1 = \left(\frac{1}{g_{m1}} \parallel R_{sr} \parallel R_F \right) \cdot C_1$$

$R_{sr} \ll R_F$

$$\tau_1 = 71.43 \cdot 20 \times 10^{-12} = 1.428 \times 10^{-9}$$

$$\tau_1 = 1.428 \times 10^{-9}$$

$$\omega_H = \frac{1}{\tau_1 + \tau_2} = 40.935 \times 10^6$$

(*) $C_2 = C_F$

$$R_2 = R_F \parallel [R_{sr} + r_{o2} \parallel R_{D2}]$$

$r_{o2} \gg R_{D2}$

$$R_2 = R_F \parallel [R_{sr} + R_{D2}]$$

$$\tau_2 = R_2 \cdot C_2$$

$$R_2 = 5k \parallel [500 + 1k]$$

$$R_2 = 1153.84 \Omega$$

$$\tau_2 = 1153.84 \cdot 20 \times 10^{-12}$$

$C_2 = C_F$

$$\tau_2 = 2.307 \times 10^{-8}$$

$R_F = 5k$

$R_{D2} = 1k$

$R_{sr} = 500 \Omega$

$$\tau_2 \gg \tau_1$$

$$23.07 \gg 1.428$$

(10)

$$\beta(s) = 0 : \text{win} \quad R_x = R_{SR} \parallel R_F \text{ and } R_y = R_F + R_{SR}$$

$$A_{VA,fl} = \left[\frac{-g_{m1}}{1+g_{m1}R_x} \right] \cdot \left[R_{D1} \parallel [(1+g_{m1}R_x) \cdot r_{o1}] \right] \cdot [-g_{m2}] \cdot [R_{D2} \parallel R_y \parallel r_{o2}]$$

$$r_{in,VA,fl} = +\infty$$

$$r_{out,VA,fl} = R_{D2} \parallel R_y \parallel r_{o2} = R_{D2} \parallel R_y$$

$$r_{in,f} = r_{in,VA,fl} \cdot (1 + A_{VA,fl} \beta) = +\infty$$

$$r_{out,f} = \frac{r_{out,VA,fl}}{1 + A_{VA,fl} \beta} = \frac{R_{D2} \parallel R_y}{1 + A_{VA,fl} \beta}$$

$$A_{VA,fl}(j\omega) = \frac{A_{VA,fl}}{1 + \frac{j\omega}{\omega_H}}, \quad \omega_H = 40.93 \times 10^6$$

$$\beta(j\omega) = \beta_0 \left[\frac{1 + \frac{j\omega}{\omega_z}}{1 + \frac{j\omega}{\omega_p}} \right]$$

$$A_f(j\omega) = \frac{A_{VA,fl}(j\omega)}{1 + \beta(j\omega) \cdot A_{VA,fl}(j\omega)} = \frac{\frac{A_{VA,fl}}{1 + \frac{j\omega}{\omega_H}}}{1 + \frac{A_{VA,fl}}{1 + \frac{j\omega}{\omega_H}} \cdot \beta_0 \frac{1 + \frac{j\omega}{\omega_z}}{1 + \frac{j\omega}{\omega_p}}}$$

$$= A_{VA,fl} \left(1 + \frac{j\omega}{\omega_p} \right)$$

$$\frac{1 + \frac{j\omega}{\omega_H} + \frac{j\omega}{\omega_p} + \beta A_{VA,fl} + \frac{j\omega}{\omega_z}}{\beta A_{VA,fl}}$$

$$A_f(j\omega) = \frac{A_{VA,fl}}{1 + \beta A_{VA,fl}} \cdot \frac{1 + \frac{j\omega}{\omega_p}}{1 + \frac{j\omega}{(\omega_H \parallel \omega_p \parallel \frac{\omega_z}{A_{VA,fl} \cdot \beta})} (1 + A_{VA,fl} \beta)}$$

$A_f(j\omega)$ has a zero and a pole approximately

$$W_p = \frac{1}{C_F R_F \frac{R_{SE}}{R_{SE} + R_F}} \quad \frac{R_{SE}}{R_F} = \frac{1}{10} \quad W_p = \frac{11}{C_F R_F} = 11 W_z$$

$$A_{VA, fl} = \left[\frac{-1.2 \text{ mS}}{1 + (1.2 \text{ mS}) \cdot (0.5 \text{ k} // 15 \text{ k})} \right] \cdot \left[1.5 \text{ k} // \left[25 \text{ k} (1 + (1.2 \text{ mS}) \cdot (0.5 \text{ k} // 15 \text{ k})) \right] \right] \cdot \left[-1.6 \text{ mS} \right] \cdot \left[1 \text{ k} // 5.5 \text{ k} // +\infty \right]$$

$A_{VA, fl} \beta > 0$
 $\approx 1.5 \text{ k}$

$\approx 0.9 \text{ k}$

$$A_{VA, fl} = (-0.75 \text{ mS}) \cdot (1.5 \text{ k}) \cdot (-1.6 \text{ mS}) \cdot 0.5 \text{ k} = 1.620$$

$$A_{VA, fl} \cdot \beta = 0.15$$

$$\frac{0.15}{\beta} = 1.620 \quad \beta = 0.092 \approx \frac{1}{11}$$

$$\frac{W_z}{A_{VA, fl} \beta} = \frac{W_z}{0.15} = \frac{W_p}{11 \cdot (0.15)} = \frac{W_p}{1.65}$$


$$W_p = \frac{1}{C_F \cdot 5 \text{ k} \cdot \frac{1}{11}} = \frac{1}{454.5 \times C_F} = \frac{1}{110.01 \times 10^6 \times C_F}$$

$$\frac{W_z}{A_{VA, fl} \beta} = \frac{W_p}{1.65} = 66.673 \times 10^6 = \frac{W_z}{A_{VA, fl} \beta}$$




$$A_f(j\omega) = \frac{1.62}{1.5} \cdot \frac{1 + \frac{j\omega}{1}}{C_F (454.5)} \cdot \frac{1}{1 + \left[\frac{1}{(C_F \cdot 1154.5)} // \frac{1}{C_F \cdot 454.5} // \frac{1}{C_F \cdot 720} \right]}$$

$$W_{H, fl} = \frac{0.15}{C_F \cdot (2.62)} = \frac{1}{C_F \cdot 22.8 \text{ k}} = 2\pi (50 \text{ kHz})$$

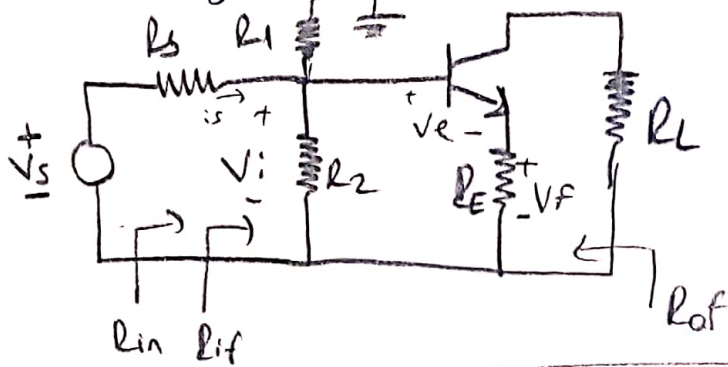Q5. Use the techniques of feedback analysis to determine the input and output resistance of the CE transistor amplifier in Fig P10.26. The circuit parameters are $R_S = 500\Omega$, $R_E = 250\Omega$, $R_2 = 15k\Omega$, $R_1 = 5k\Omega$, $R_C = 5k\Omega$ and $R_L = 10k\Omega$. The π model parameters are $r_o = 25k\Omega$, $h_{fe} = 150$, $r_{\pi} = 250\Omega$, $g_m = 0.3876 A/V$, $r_m = \infty$.



Feedback network schematic

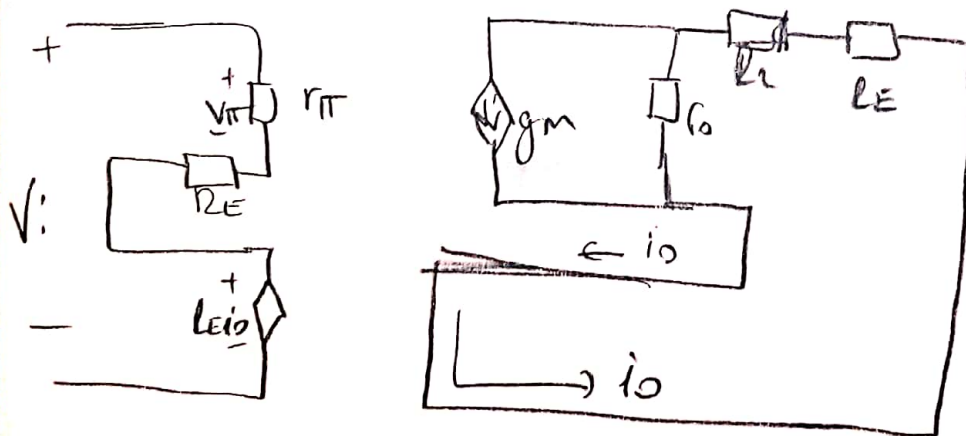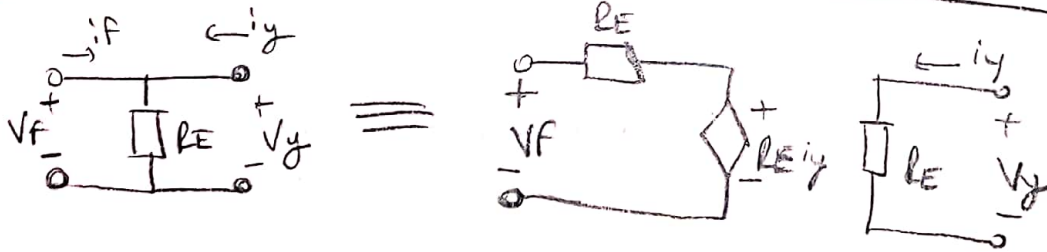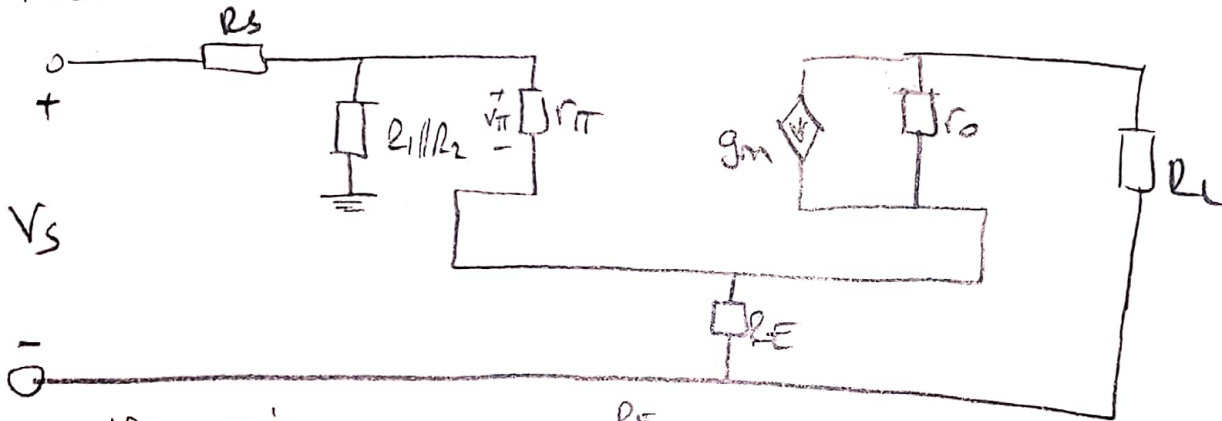

$$\beta = 0$$

$$r_{in, TCA, FL} = r_{\pi} + R_E$$

~~AP~~

(13)

$$A_{TCA,fl} = \frac{1\pi}{\pi + R_E} \cdot g_m \cdot \frac{r_o}{r_o + R_L + R_E}$$

$$r_{out, TCA, fl} = r_o + R_L + R_E$$


$$r_{in, TCA} = \pi + R_E$$

Time dense analysis:

$$r_{in, f} = r_{in, TCA, fl} (1 + \beta A_{TCA, fl})$$

$$r_{out, f} = r_{out, TCA, fl} (1 + \beta A_{TCA, fl})$$
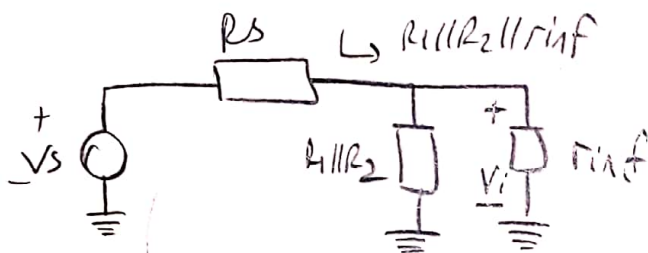
$$A_f = \frac{A_{TCA, fl}}{1 + \beta A_{TCA, fl}}$$



$$\frac{V_o}{V_s} = \frac{R_L \parallel R_2 \parallel r_{in, f}}{R_L \parallel R_2 \parallel r_{in, f} + R_s} \cdot [-A_f] r_{out, f}$$

$$\frac{V_o}{V_s} = \frac{5k \parallel 15k \parallel 17.803k}{5k \parallel 15k \parallel 17.803k + 500} \cdot [-3.94 \times 10^{-3}] \cdot (1225k)$$

$$\frac{V_o}{V_s} = \frac{3.09k}{3590} \cdot (-3.94 \times 10^{-3}) \cdot 1225k$$

$$\frac{V_o}{V_s} = -4154.285$$

$$r_{in, TCA} = 250\Omega + 250 = 0.5k\Omega$$

$$r_{out, TCA} = r_o + R_L + R_E = 25k + 10k + 350$$

$$r_{out, TCA} = 35k\Omega$$

$$A_{TCA} = \frac{250}{250 + 250} \cdot 0.3876 \cdot \frac{25k}{25k + 10k}$$

$$A_{TCA} = 0.1384$$

$$\beta = R_E = 250$$

$$r_{in, f} = 500 \cdot (1 + 34.6)$$

$$r_{in, f} = 17.803k\Omega$$


$$r_{out, f} = 35k\Omega \cdot 35 =$$

$$r_{out, f} = 1225k\Omega$$


$$A_f = \frac{0.138}{1 + 34.6}$$

$$A_f = 3.94 \times 10^{-3}$$

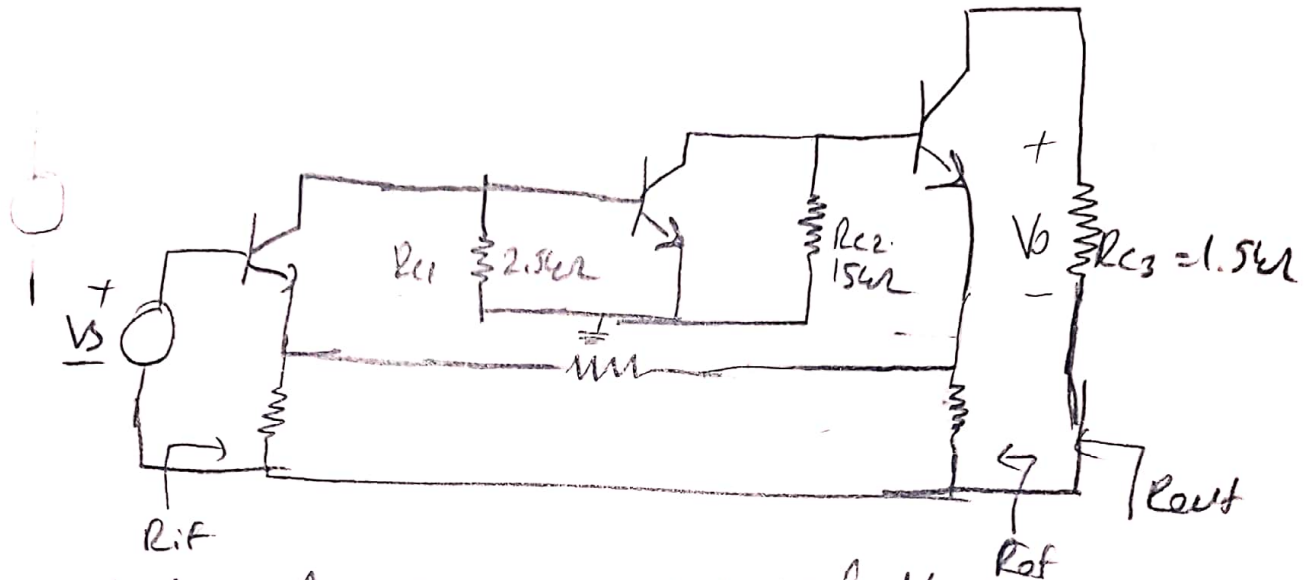Q6. The AC equivalent circuit of a feedback amplifier is shown in fig P.10.28. The circuit values $R_{C1} = 2.5k\Omega$, $R_{C2} = 5k\Omega$, $R_{C3} = 1.5k\Omega$, $R_{E1} = 100\Omega$, $R_{E2} = 100\Omega$, $R_F = 750\Omega$, $R_S = 0$. The transistor parameters are $h_{fe} = 100$, $r_{\pi} = 2.5k\Omega$, $r_o = 25k\Omega$ and $r_{\mu} = \infty$. Use techniques of feedback analysis to calculate (a) the input resistance R_{if} , (b) the output resistance R_{of} , the closed-loop voltage gain A_f .



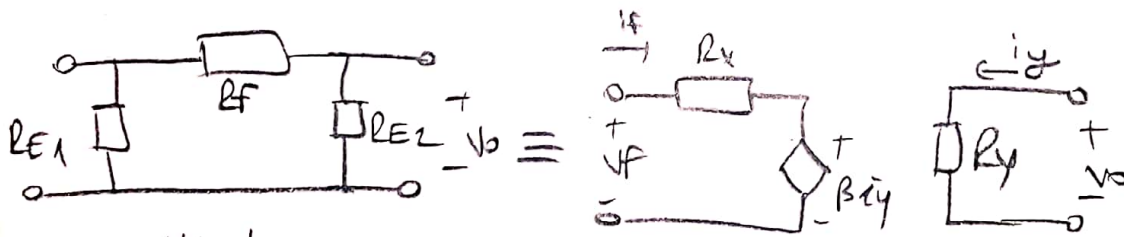
Transconductance Amp. in current series feedback form.



$$R_x = \frac{V_x}{i_x} \Big|_{i_y=0} = R_{E1} \parallel [R_F + R_{E2}]$$

$$R_y = \frac{V_y}{i_y} \Big|_{i_x=0} = R_{E2} \parallel [R_{E1} + R_F]$$

$$\beta = \frac{V_x}{i_y} \Big|_{i_x=0} = \frac{R_F}{R_{E2} + R_{E1} + R_F} \cdot R_{E1}$$

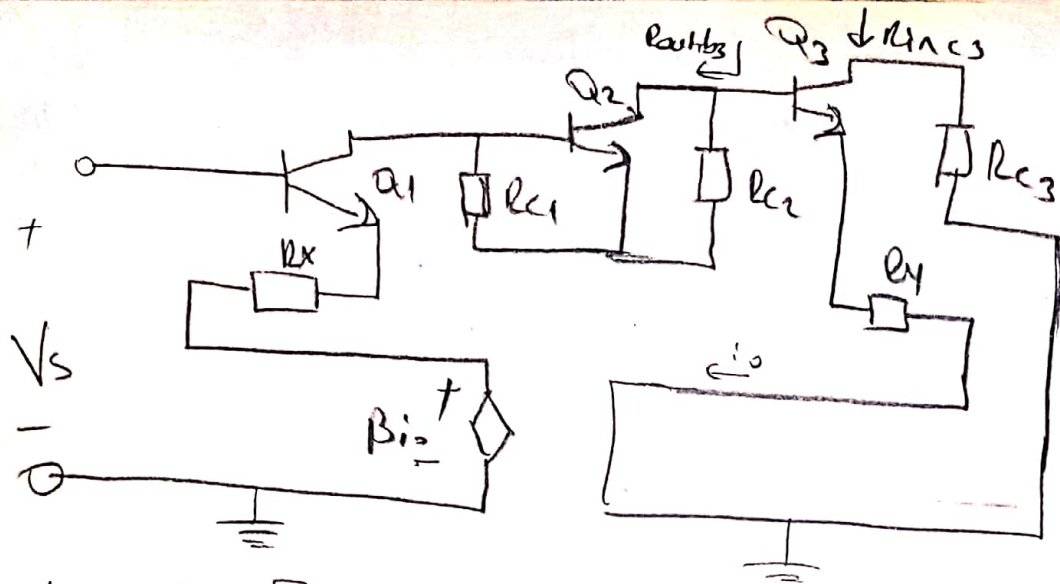

$$A_{TCA,fl} = \left[\frac{-g_{m1}}{1+g_{m1}R_x} \right] \left[[(1+g_{m1}R_{be1}) R_{c1}] \parallel R_{c1} \parallel R_{be2} \right] \cdot [-g_{m2}] \cdot$$

$$[R_{c2} \parallel R_{c2} \parallel [R_{be3} (1+g_{m3}R_{e4})]] \cdot \left[\frac{g_{m3}}{1+g_{m3}R_{e4}} \right]$$

$$R_{in,TCA,fl} = R_x (1+g_{m1}R_x)$$

$$R_{out,TCA,fl} = R_{c3} + R_{be3} \quad R_{out,b3} = R_{c2} \parallel R_{be2}$$

$$R_{in,b3} = (1+g_{m3}R_{e4}) \left[\frac{R_{e4}R_{be3}}{R_{e4}R_{be3} + R_{out,b3}} + \frac{R_{be3} + R_{e4}R_{out,b3}}{R_{e4}R_{be3} + R_{out,b3}} \right]$$

$$\approx (1+g_{m3}R_{e4}) \left[\frac{R_{e4}R_{be3}}{R_{e4}R_{be3} + R_{out,b3}} \right]$$

For overall analysis

$$A_f = \frac{A_{TCA,fl}}{1+\beta A_{TCA,fl}}$$

$$R_{in,f} = R_{in,TCA,fl} (1+\beta A_{TCA,fl})$$

$$R_{out,f} = R_{out,TCA,fl} (1+\beta A_{TCA,fl})$$

