


HW-13

Abdullah MEMİÇOĞLU

171024001

Amu

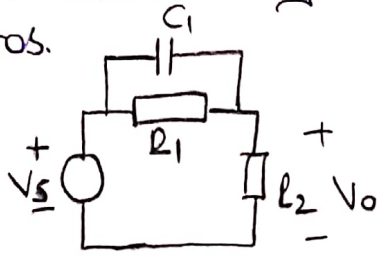Q1. Determine (a) the transfer function of the network shown in fig P12.2 and (b) its pole and zeros.



$$\frac{V_o}{V_{ss}} = \frac{R_2}{R_2 + R_1 \parallel \frac{1}{sC_1}} = \frac{R_2}{R_2 + \frac{R_1 \frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}}}$$


$$= \frac{R_2}{R_2 + \frac{R_1}{1 + sC_1 R_1}} = \frac{R_2(1 + sR_1 C_1)}{R_1 + R_2 + R_1 R_2 C_1 s} = \frac{R_2}{R_1 + R_2} \cdot \frac{1 + \frac{s}{1/R_1 C_1}}{1 + \frac{s}{1/C_1(R_1 \parallel R_2)}}$$

low freq.  
gain

$1/R_1 C_1 \rightarrow \text{zero}$

$1/C_1(R_1 \parallel R_2) \rightarrow \text{pole}$

Bode plot

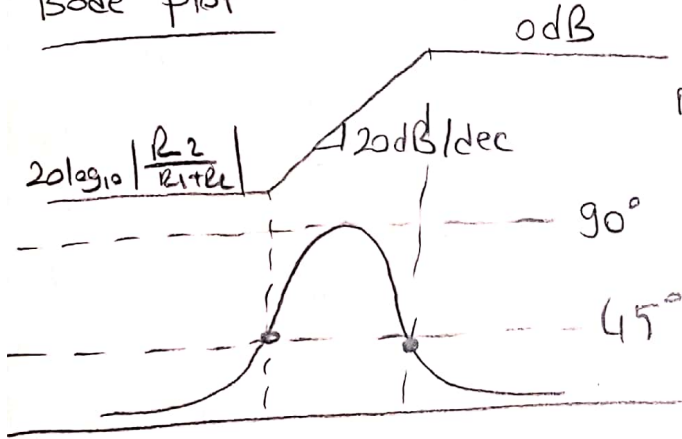

$$\frac{R_2}{R_1 + R_2} \cdot \frac{R_1 C_1}{(R_1 \parallel R_2) C_1} = \frac{R_2}{R_1 + R_2} \cdot \frac{R_1}{R_1 R_2 / (R_1 + R_2)}$$

$$= \frac{R_2 R_1}{R_1 + R_2} \cdot \frac{R_1 + R_2}{R_1 R_2} = 1 //$$

(1)

Q2. Determine (a) the pole and zero quality factors  $Q_p$  and  $Q_z$ , (b) the pole and zero resonant frequencies  $\omega_p$  and  $\omega_z$ , (c) the pole factor  $\beta_p$ , and (d) the pole angle  $\phi_p$ . The transfer function has the general form as given by  $H(s) = \frac{5s^2 + 15s + 100}{s^2 + 20s + 200}$

$$H(s) = A \cdot \frac{s^2 + 2\delta_z \omega_{0,z} s + \omega_{0,z}^2}{s^2 + 2\delta_p \omega_{0,p} s + \omega_{0,p}^2}$$

$$\boxed{B_{w,p} = 20}$$

$$B_{w,p} = 2\delta_p \omega_{0,p} \rightarrow Q_p = \frac{\omega_{0,p}}{2\delta_p \omega_{0,p}} = \frac{\sqrt{200}}{20} = \frac{\sqrt{2}}{2} = Q_p$$

$$B_{w,z} = 2\delta_z \omega_{0,z} \Rightarrow Q_z = \frac{\omega_{0,z}}{2\delta_z \omega_{0,z}} = \frac{\sqrt{20}}{3} = \frac{2\sqrt{5}}{3} = Q_z$$

$$\boxed{B_{w,z} = 3}$$

$$s^2 + 20s + 200 = (s + \alpha_p + j\beta_p)(s + \alpha_p - j\beta_p) \\ = s^2 + 2\delta_p \omega_{0,p} s + \omega_{0,p}^2$$

$$\alpha_p^2 + \beta_p^2 = \omega_{0,p}^2 = 200$$

$$2\alpha_p = 2\delta_p \omega_{0,p} = 20 \quad \boxed{\alpha_p = 10}$$

$$\beta_p = \sqrt{200 - 10^2} = \boxed{10 = \beta_p}$$


$$\boxed{P_1 = -\alpha_p - j\beta_p = -10 - 10j}$$

$$\boxed{P_2 = -\alpha_p + j\beta_p = -10 + 10j}$$

$$\phi_p = \cos^{-1} \left( \frac{\alpha_p}{\sqrt{\alpha_p^2 + \beta_p^2}} \right) = \cos^{-1} \left( \frac{10}{\sqrt{200}} \right) = \cos^{-1} \left( \frac{1}{\sqrt{2}} \right) = 45^\circ$$

(2)

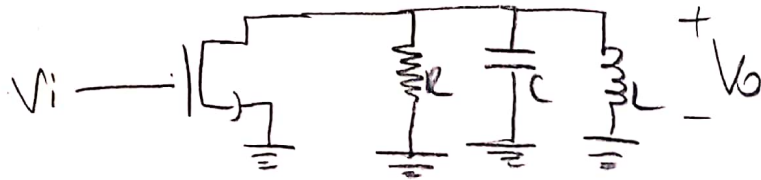Q3 A coil having an inductance of 10mH is intended for applications around 1-MHz frequency. Its Q is specified to be 200. Find the equivalent parallel resistance  $R_p$ . What is the value of the capacitor required to produce resonance at 1MHz? What additional parallel resistance is required to produce a 3dB bandwidth of 10kHz



$$\frac{V_o}{V_i} \approx -g_m \left[ R \parallel \frac{1}{sC} \parallel sL \right] = -g_m \frac{1}{\frac{1}{R} + sC + \frac{1}{sL}}$$

$$= \frac{-g_m s L}{s \frac{L}{R} + s^2 LC + 1} = \frac{-g_m s}{\frac{s}{R} + s^2 C + \frac{1}{L}} \approx -\frac{g_m s}{C} \cdot \frac{1}{s^2 \frac{s}{RC} + \frac{1}{LC}}$$

$$(\text{res. freq.})^2 = \omega_0^2 = \frac{1}{LC} \quad 2\delta\omega_0 = \frac{1}{RC} \quad 2\delta \frac{1}{\sqrt{LC}} = \frac{1}{RC}$$

$$\frac{V_o}{V_i} = -\frac{g_m}{C} \cdot \frac{1}{2\delta\omega_0} = -\frac{g_m}{C} \cdot RC = -g_m R$$

$$\delta = \sqrt{\frac{L}{C}} \cdot \frac{1}{2R}$$

$$G(\omega) = \frac{2\delta\omega_0 \cdot \omega}{(\omega_0^2 - \omega^2)^2 + (2\delta\omega_0\omega)^2} \Rightarrow \left| G(\omega_{3dB}) \right| = \frac{(2\delta\omega_0)^2 \omega_{-3dB}^2}{(\omega_0^2 - \omega_{-3dB}^2)^2 + (2\delta\omega_0 \omega_{-3dB})^2} = \frac{1}{2}$$

$$\omega_L = \omega_0 \left[ -\delta + \sqrt{1 + \delta^2} \right]$$


$$\omega_H = \omega_0 \left[ \delta + \sqrt{1 + \delta^2} \right]$$

$$BW = \omega_H - \omega_L = 2\delta\omega_0 = \frac{1}{RC}$$

3


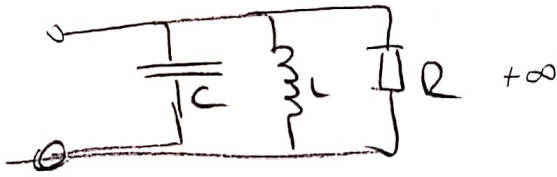
$$R \rightarrow +\infty \quad \underline{BW = 0}$$



$$Q = \frac{\omega_0}{BW} = \frac{1/\sqrt{LC}}{1/RC} = R\sqrt{\frac{C}{L}}$$

$$R \rightarrow +\infty \quad Q \rightarrow +\infty$$

~~Q~~  $R \rightarrow +\infty$  Q için ideal değer olsa da bu durumda  $BW = 0$  olduğundan kullanılamamaktadır. Trade-off



$$L = 10 \mu H$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi \cdot 1 \text{ MHz}$$

$$= 2\pi \times 10^6$$

$$2\pi \times 10^6 = \frac{1}{\sqrt{LC}} \quad \sqrt{C} = \frac{1}{2\pi \times 10^6 \cdot \sqrt{L}} \rightarrow C = \frac{1}{4\pi^2 \cdot 10^{12} \cdot L} \quad L = 10 \times 10^{-6}$$

$$Q = R_p \sqrt{\frac{C}{L}} = 200$$

$$C = \frac{1}{4\pi^2 \cdot 10^{12} \cdot 10 \cdot 10^{-6}} = \frac{10^{-7}}{4\pi^2}$$

$$R_p = \sqrt{\frac{2.533 \times 10^{-9}}{10 \cdot 10^{-6}}} = 200$$


$$C = 2.533 \text{ nF}$$

$$0.0159$$

$$R_p = 6000\pi = 12.566 \text{ k}\Omega$$

(4)

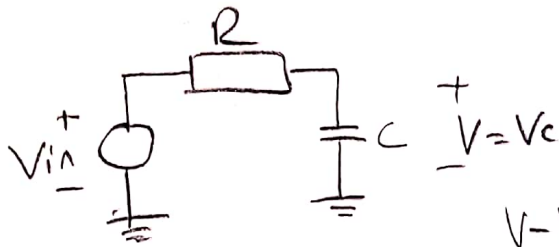Q4. Derive the response of an RC low-pass filter to a sinusoidal wave form



$$V_{in}(t) = A \sin(\omega t)$$

$$\frac{V - V_{in}}{R} + C \frac{dV}{dt} = 0$$

$$\frac{V - V_{in}}{RC} + \frac{dV}{dt} = 0$$

$$sV(s) - V(0^-) + \frac{1}{RC} V(s) = \frac{1}{RC} V_{in}(s) \quad \frac{dV}{dt} + \frac{1}{RC} V = \frac{1}{RC} V_{in}(t)$$

$$= \frac{A}{RC} \frac{\omega}{s^2 + \omega^2} \rightarrow \left(s + \frac{1}{RC}\right) V(s) = V(0) + \frac{A}{RC} \frac{\omega}{s^2 + \omega^2}$$

$$V(s) = \frac{V(0)}{s + \frac{1}{RC}} + \frac{A}{RC} \cdot \frac{\omega}{(s^2 + \omega^2)(s + \frac{1}{RC})}$$

$$\frac{1}{(s^2 + \omega^2)(s + \frac{1}{RC})} = \frac{Fs + G}{s^2 + \omega^2} + \frac{H}{s + \frac{1}{RC}} \rightarrow (Fs + G) \cdot (s + \frac{1}{RC}) + H(s^2 + \omega^2) = 1$$

$$Fs^2 + \frac{G}{RC} + Gs + \frac{F}{RC} s + Hs^2 + H\omega^2 = 1$$

$$F + H = 0 \quad G + \frac{F}{RC} = 0$$

$$G = \frac{H}{RC} \quad H = -F$$

$$\frac{G}{RC} + H\omega^2 = 1 \rightarrow \frac{H}{(RC)^2} + H\omega^2 = 1$$

$$H [1 + (RC\omega)^2] = (RC)^2$$

$$H = \frac{(RC)^2}{1 + (RC\omega)^2}$$

$$G = \frac{H}{RC} = \frac{RC}{1 + (RC\omega)^2}$$

$$F = -\frac{(RC)^2}{1 + (RC\omega)^2}$$

$$V_{per}(s) = \frac{AW}{RC} \left[ \frac{FS+G}{s^2+w^2} \right] = \frac{AFw}{RC} \cdot \frac{s}{s^2+w^2} + \frac{AG}{RC} \cdot \frac{w}{s^2+w^2}$$

$$v_{per}(t) = \frac{AFw}{RC} \cdot \cos(wt) + \frac{AG}{RC} \sin(wt)$$

$$K \cos \phi = \frac{AG}{RC} \quad K \sin \phi = \frac{AFw}{RC}$$

$$\tan \theta = \frac{K \sin \theta}{K \cos \theta} = \frac{F \cdot w}{G} = -RCw$$

$$(K \cos \theta)^2 + (K \sin \theta)^2 = K^2 (\sin^2 \theta + \cos^2 \theta) = K^2 = \left( \frac{AG}{RC} \right)^2 + \left( \frac{AFw}{RC} \right)^2$$

$$K^2 = \left( \frac{A}{RC} \right)^2 \cdot (G^2 + (Fw)^2) = \left( \frac{A}{RC} \right)^2 \cdot \left[ \frac{(RC)^4 w^2}{[1+(RCw)^2]^2} + \frac{(RC)^2}{[1+(RCw)^2]^2} \right]$$

$$K^2 = \left( \frac{A}{RC} \right)^2 \cdot (RC)^2 \cdot \left[ \frac{(RCw)^2 + 1}{[1+(RCw)^2]^2} \right] = A^2 \cdot \frac{1}{1+(RCw)^2} \rightarrow \boxed{K = \frac{A}{\sqrt{1+(RCw)^2}}}$$

$$s_{per}(t) = K \sin(wt + \phi) = \frac{A}{\sqrt{1+(RCw)^2}} \sin(wt + \arctan(-RCw))$$

$$w = w_0 = \frac{1}{RC}$$

$$K = \frac{A}{\sqrt{1+(RC \cdot \frac{1}{RC})^2}} = \boxed{\frac{A}{\sqrt{2}} = K}$$

$$\phi = \arctan(-RC \cdot \frac{1}{RC}) = \arctan(-1) = \left( -\frac{\pi}{4} \right)$$

(6)