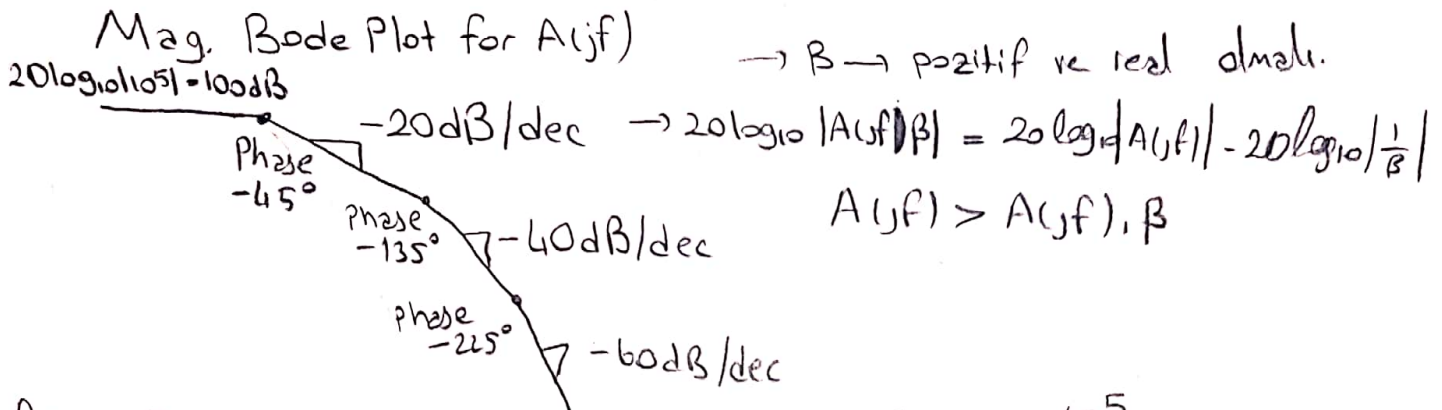


Q1. An amplifier has a dc gain of 10^5 and poles at 10^5 Hz, 3.16×10^5 Hz, and 10^6 Hz. Find the value of β , and the corresponding closed-loop gain, for which a phase margin of 45° is obtained.



Bazı 5 common terms değerleri verilmiş. $A(f) = \frac{10^5}{(1 + \frac{jf}{10^5})(1 + \frac{jf}{3.16 \times 10^5})(1 + \frac{jf}{10^6})}$ olarak yazılabilir.

$|A(f) \cdot \beta| = 1$ olduğu bilindiğinden β için çözümler.

$$\left| \frac{10^5 \cdot \beta}{(1 + \frac{jf_u}{10^5}) \cdot (1 + \frac{jf_u}{3.16 \times 10^5}) \cdot (1 + \frac{jf_u}{10^6})} \right| = 1 \quad \rightarrow \text{closed loop gain for phase marg. } 45^\circ$$

dermisi 45° için $f_u = 3.16 \times 10^5$ Hz





$$1 = \frac{10^5 \cdot \beta}{\sqrt{1+(3.16)^2} \cdot \sqrt{2} \cdot \sqrt{1+(0.316)^2}} \Rightarrow 4.915 = 10^5 \cdot \beta \quad \boxed{\beta = 4.915 \times 10^{-5}} \quad \text{second pole}$$

$\frac{1}{\beta} = 2.0342 \times 10^4$


$$20 \log_{10} \left| \frac{1}{\beta} \right| = 86.168 \text{ dB}$$

$$A_f = \frac{A}{1 + A \cdot \beta} = \frac{10^5}{1 + 10^5 \cdot (4.915 \times 10^{-5})} = \underline{\underline{1.6906 \times 10^4}}$$

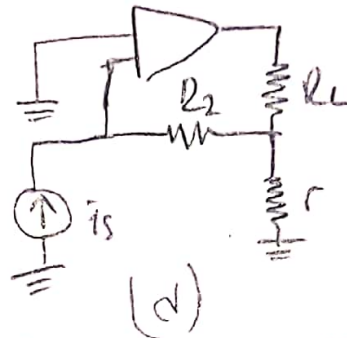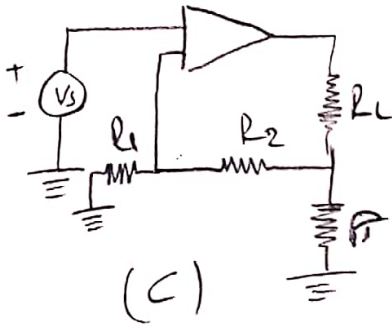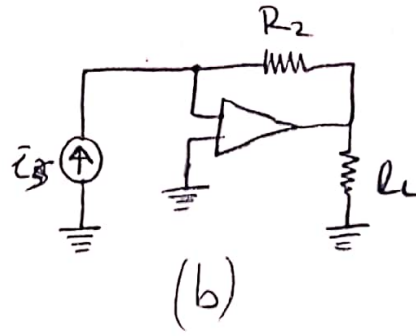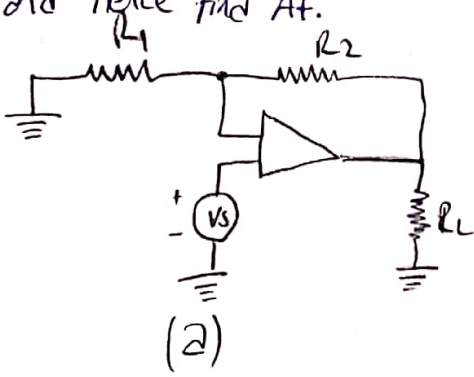Q2. For each of the opamp circuits shown in Fig. P.8.2b, identify the feedback topology and indicate the output variable being sampled and the feedback signal. In each case, assuming the opamp to be ideal, find an expression for β , and hence find A_f .




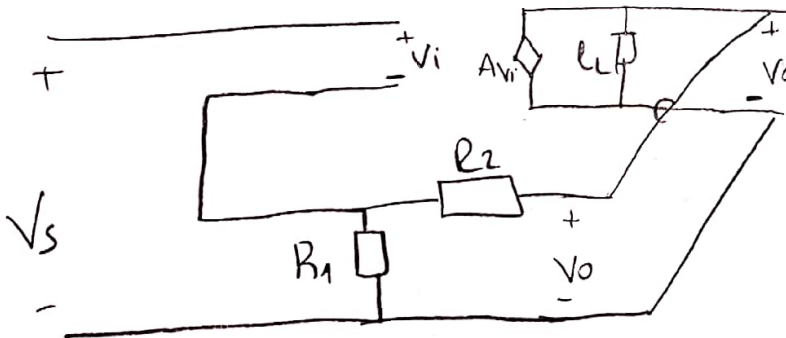OPAMP'lar voltage amplifier'lerdir. Aslında diff. amp gibi bir davranıır. Her girişteki iki kolun farkını yükselterek dışarı çıkarıyor. İyi bir voltage amp. olması için yüksek giriş empedansı olmalı (ss equ. empedansı). OPAMP'in basit bir modellenmesi aşağıdaki gibidir.



Burada giriş empedansı sonsuza gelmiştir. İdeale yaklaşılmıştır. Çıkış empedansı sıfır \rightarrow ideal değeri.

Feedback Network

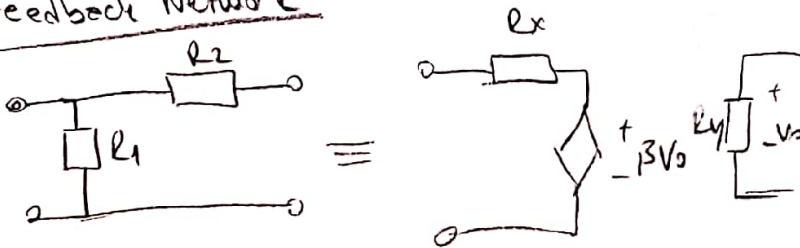



$$\beta = \frac{R_1}{R_1 + R_2}$$

$$R_x = R_1 \parallel R_2$$

$$R_y = R_1 + R_2$$

(2)

Voltage Amp. with feedback network.

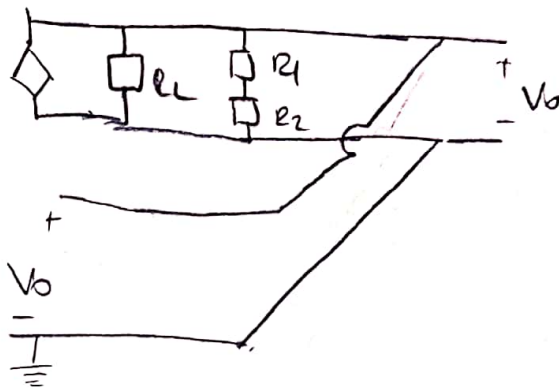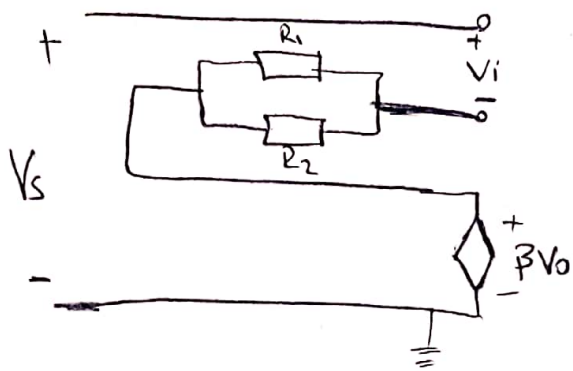

$$\beta = 0$$

$$r_{in,VA,f} = +\infty \quad (r_{in} = +\infty \text{ denistik Ideal olmayan opamp olsaydı}) \rightarrow r_{in} + R_1 \parallel R_2 \rightarrow \text{ideale yaklaşıyor.}$$

$$r_{out,VA,f} = 0 \quad (r_{out} = 0 \text{ denistik Ideal olmayan opamp olsaydı}) \rightarrow r_{out} \parallel R_L \parallel (R_1 + R_2) \rightarrow \text{düşürerek ideale yaklaşıyor.}$$

$$A_{VA,f} = A \left(\text{ideal olmasaydı} \rightarrow A_{VA,f} = \frac{r_{in}}{r_{in} + R_1 \parallel R_2} \cdot A \cdot \frac{R_L \parallel (R_1 + R_2)}{(R_L \parallel (R_1 + R_2)) + r_{out}} \right)$$

Feed back Amp. Analizi

$$r_{in,f} = r_{in,VA,f} (1 + \beta A_{VA,f}) = +\infty$$


$$r_{out,f} = \frac{r_{out,VA,f}}{1 + \beta A_{VA,f}} = 0$$

Improving factor ile giriş empedansı yükselttiyor çıkış empedansı düşürüyor. Böylece voltage amp. idealize ediliyor.

$$A_f = \frac{A_{VA,f}}{1 + \beta A_{VA,f}} = \frac{A}{1 + \frac{R_1}{R_1 + R_2} A} \approx \frac{R_1 + R_2}{R_1} \quad A \gg 1$$

(b)

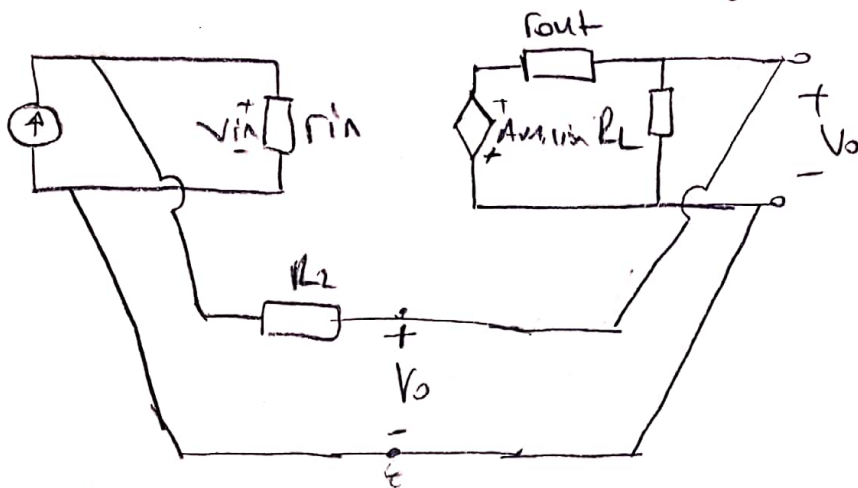Trans Resistance Amp. (voltage-shunt feedback.)




Feedback Network



$$B = \frac{v_f}{V_o} \Big|_{v_f=0} \equiv \frac{-i_y}{i_o} = \frac{-1}{R_2} \quad \left\{ \begin{array}{l} R_y = \frac{V_o}{i_y} \Big|_{v_f=0} = R_2 \\ R_x = \frac{V_f}{i_f} \Big|_{V_o=0} = R_2 \end{array} \right.$$

$$R_x = \frac{V_f}{i_f} \Big|_{V_o=0} = R_2$$

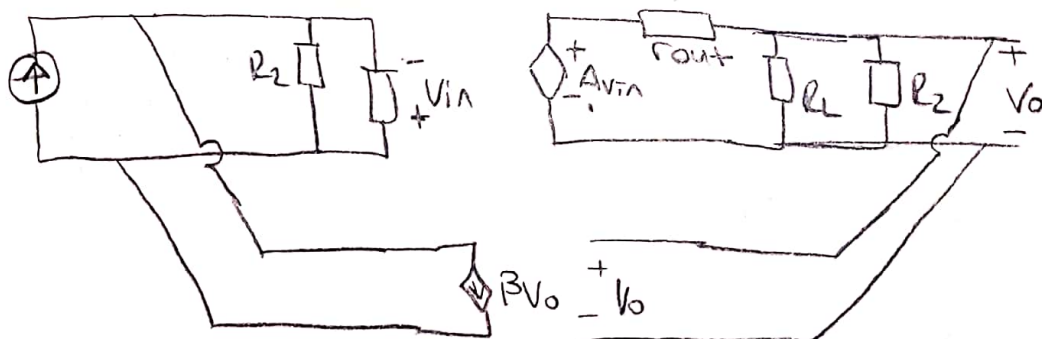Transresistance Amp. with feedback network



$$B=0$$

$$r_{in, TCA, fl} = R_2 \parallel r_{in} \quad r_{in, TCA, f} < r_{in}$$

$$r_{out, TCA, fl} = R_2 \parallel R_L \parallel r_{out} \quad r_{out, TCA, f} < r_{out}$$

feedback network
burada giriş ve
çıkış empedansların

$$A_{TRA, f} = [-R_2 \parallel r_{in}] \cdot A \cdot \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}} \right]$$

$$r_{in, TRA, f} = R_2 \leftarrow R_2 \ll r_{in}$$

$$r_{out, TRA, fl} \approx 0$$

$$A_{TRA, fl} = [-R_2] \cdot A \cdot [1] = A \cdot R_2 = A_{TRA, f}$$

$$\hookrightarrow R_2 \ll r_{in} \quad \hookrightarrow r_{out} \ll R_L \parallel R_2$$

(4)

Feedback Amp. Analysis

$$r_{in,f} = \frac{r_{in,TRA,f}}{1 + \beta \cdot A_{TRA,f}} = \frac{R_2 \parallel r_{in}}{1 + \left(-\frac{1}{R_2}\right) \cdot (-R_2 \parallel r_{in}) \cdot A \left(\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right)}$$


$$\left. \begin{matrix} r_{in} \rightarrow +\infty \\ r_{out} \rightarrow 0 \end{matrix} \right\} \frac{R_2}{1 + \left(-\frac{1}{R_2}\right) \cdot (-R_2) \cdot A} = \frac{R_2}{1+A} \quad A \gg 1 \rightarrow \boxed{\frac{R_2}{A}}$$

$$r_{out,f} = \frac{r_{out,TRA,f}}{1 + \beta A_{TRA,f}} = \frac{0}{\dots} = 0 \quad \text{if } A \gg R_2 \rightarrow r_{in,f} = 0$$


$$A_f = \frac{A_{TRA,f}}{1 + \beta A_{TRA,f}} = \frac{[-R_2 \parallel r_{in}] \cdot A \cdot \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right]}{1 + \left(-\frac{1}{R_2}\right) \cdot [-R_2 \parallel r_{in}] \cdot A \cdot \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right]}$$

$$A_f = \frac{-R_2 \cdot A}{1 + \left(-\frac{1}{R_2}\right) \cdot (-R_2) \cdot A} = \frac{-R_2 \cdot A}{A+1} \xrightarrow{A \gg 1} \boxed{-R_2} \rightarrow r_{in} \rightarrow +\infty, r_{out} \rightarrow 0 //$$

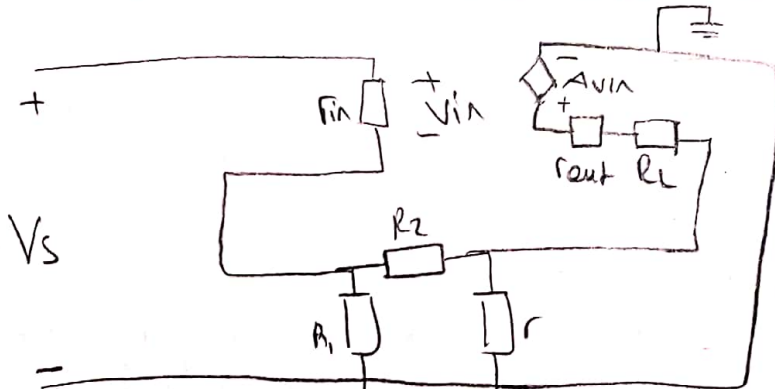Transconductance amp. with current-series feedback




Feedback Network Analysis

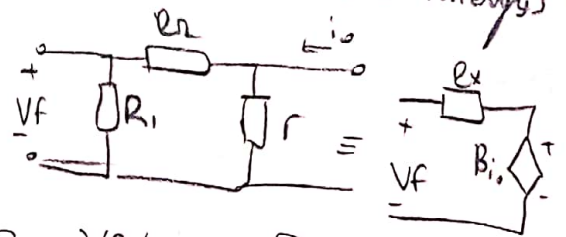

$$\beta = \frac{V_f}{i_o} \Big|_{V_x=0} = \frac{r}{r + R_1 + R_2} \cdot R_1$$

$$R_x = \frac{V_f}{i_f} \Big|_{i_o=0} = R_1 \parallel (R_2 + r)$$

$$R_y = \frac{V_x}{i_o} \Big|_{V_f=0} = r \parallel (R_1 + R_2)$$

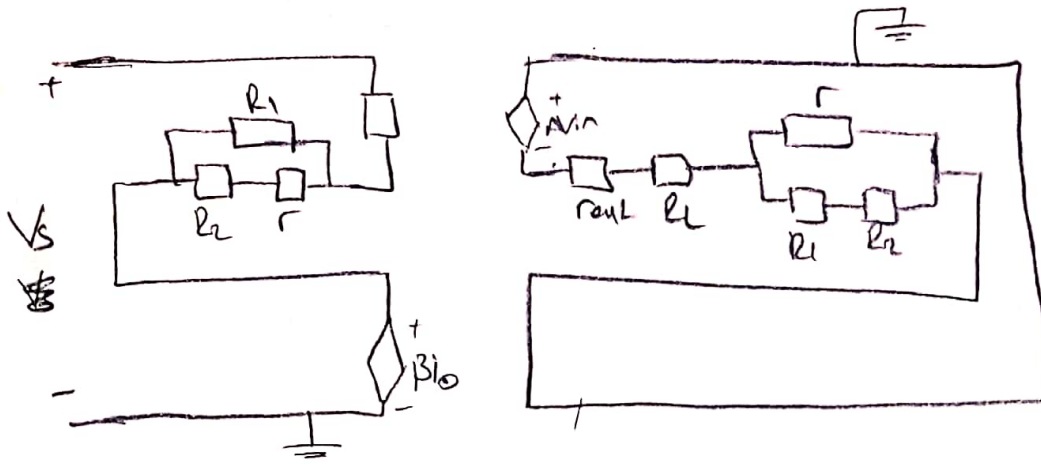

$$\beta = 0$$

$$r_{in, TCA, fl} = r_{in} + R_1 \parallel (R_2 + r) \rightarrow r_{in, TCA, f} > r_{in}$$

$$r_{out, TCA, f} = r_{out} + R_L + r \parallel (R_1 + R_2) \rightarrow r_{out, TCA, f} > r_{out}$$

$$A_{TCA, fl} = \frac{r_{in}}{r_{in} + R_1 \parallel (R_2 + r)} = A \cdot \frac{1}{r_{out} + R_L + r \parallel (R_1 + R_2)}$$

$$r_{in} = \infty \text{ old. den } r_{in, TCA, f} = \infty$$

$$r_{out, TCA, f} \approx R_L + r \parallel (R_1 + R_2) \rightarrow r_{out} = 0$$

$$A_{TCA, fl} = A \cdot \frac{1}{R_L + r \parallel (R_1 + R_2)}$$

feedback amp. Analysis

$$\begin{aligned} r_{in, f} &= (1 + \beta A_{TCA, fl}) r_{in, TCA, fl} \\ r_{out, f} &= (1 + \beta A_{TCA, fl}) r_{out, TCA, f} \end{aligned} \quad \left. \begin{array}{l} \text{current-series bağlandı tipi} \\ \text{giris ve çıkış portları feedback} \\ \text{fazlıdır orantısız zıttır. Bu} \\ \text{de transconductance amp.'i} \\ \text{idealize eder.} \end{array} \right\}$$


$$r_{out, f} = \left(1 + \frac{r R_1}{r + R_1 + R_2} \cdot A \cdot \frac{1}{R_L + r \parallel (R_1 + R_2)} \right) \cdot (R_L + r \parallel (R_1 + R_2))$$

$$A \gg 1 \rightarrow r_{out, f} = \left(\frac{R_1 \cdot r \cdot A}{r + R_1 + R_2} \right)$$


(6)

$$A_F \approx \frac{A \cdot \frac{R_L + r \parallel (R_1 + R_2)}{1 + \frac{r R_L}{r + R_1 + R_2}}}{\frac{A \cdot \frac{1}{R_L + r \parallel (R_1 + R_2)}}{1}} \xrightarrow{A \gg 1} \frac{r + R_1 + R_2}{r R_1} = A_F$$


Current Amp. with current-shunt feedback

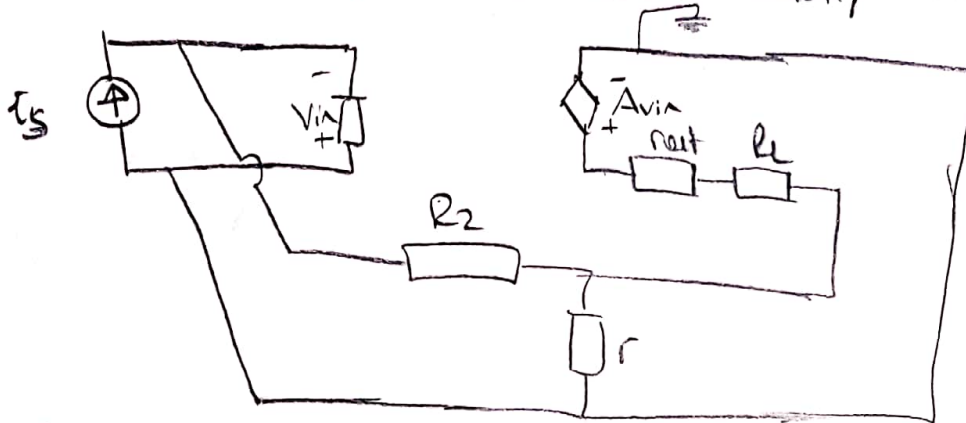

Feedback network Analysis

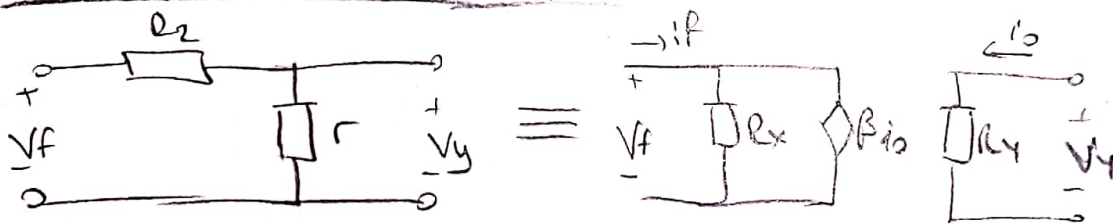

$$R_x = \frac{V_f}{i_o} \Big|_{V_f=0} = R_2 + r \quad R_y = \frac{V_y}{i_o} \Big|_{V_f=0} = R_L \parallel r \quad \beta = \frac{i_f}{i_o} \Big|_{V_f=0} = \frac{r}{r + R_2}$$

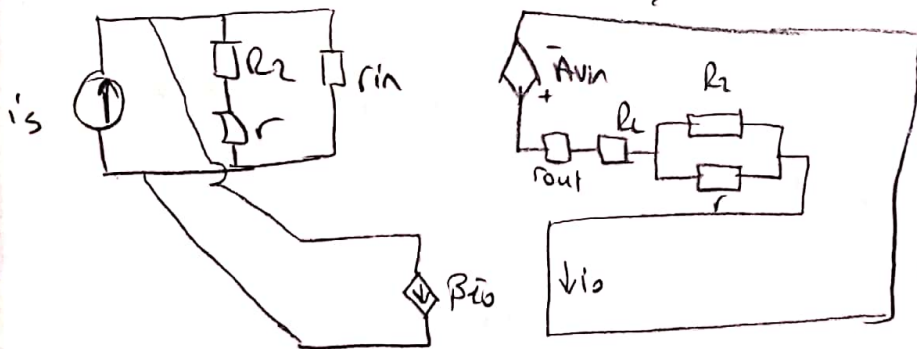

$\beta = 0$ Current Amp. with feedback

$$r_{in, A, fl} = r_{in} \parallel (R_2 + r) \\ r_{out, A, fl} = r_{out} + R_L + R_2 \parallel r$$

$$A_{CA, fl} = \frac{-R_2 + r}{R_2 + r + r_{in}} A \cdot \frac{1}{r_{out} + R_L + R_2 \parallel r}$$

$$r_{in} \rightarrow \infty \quad r_{out} \rightarrow 0 \\ r_{in, A, fl} = (R_2 + r) \\ r_{out, A, fl} = R_L + R_2 \parallel r \\ A_{CA, fl} = -A \frac{(R_2 + r)}{R_L + (R_2 \parallel r)}$$

Current Amp with feedback amp

$$r_{in,f} = \frac{r_{in,CA,fl}}{1 + B A_{CA,fl}} \approx \frac{R_2 + r}{1 + \left(\frac{-r}{r + R_2} \right) (-A) \cdot \left(\frac{R_L r}{R_L + R_2 || r} \right)}$$

$$A \gg 1 \rightarrow \frac{R_2 + r}{r.A. \frac{1}{R_L + R_2 || r}} = \frac{(R_2 + r) \cdot (R_L + R_2 || r)}{r.A.} = \frac{(R_2 + r) \cdot R_L}{r.A.}$$



$$r_{out,f} = (1 + B A_{CA,fl}) r_{out,CA,fl} = \frac{R_L (R_2 + r)}{r.A.}$$

$$= \left[1 + \left(\frac{-r}{r + R_2} \right) (-A) \cdot \left(\frac{R_L r}{R_L + R_2 || r} \right) \right] \cdot (R_L + R_2 || r)$$




$$\left. \begin{matrix} r_{in} \rightarrow +\infty \\ r_{out} \rightarrow 0 \end{matrix} \right\} A \gg 1 \rightarrow A \cdot r = r_{out,f} = r.A$$

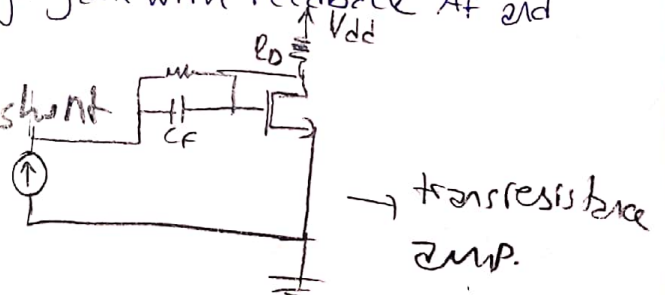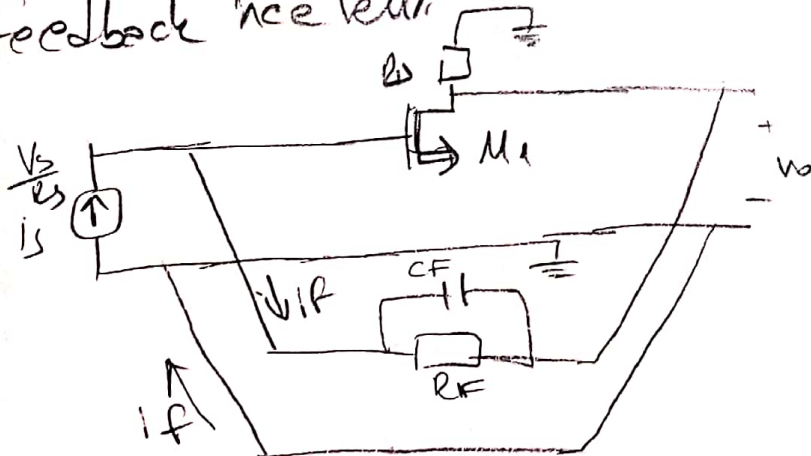Q3. The Mos amplifier shown in fig. P10.42 is biased to have the following small-signal MOS parameters: $g_{m1} = 1.2 \text{ mA/V}$ and $r_{o1} = 25 \text{ k}\Omega$. If $R_F = 100 \text{ k}\Omega$ then $R_D = 2 \text{ k}\Omega$ and $C_F = 10 \text{ nF}$. Determine (a) the voltage gain without feedback $A = v_o / v_s$, (b) the voltage gain with feedback A_f and (c) the high cutoff frequency f_H

Transresistance amp. depends on voltage-shunt feedback network




8

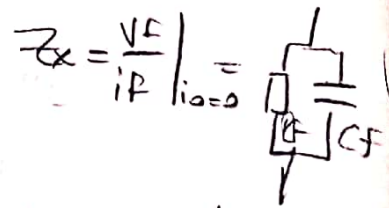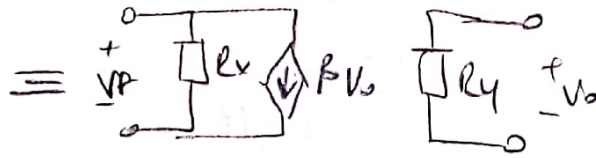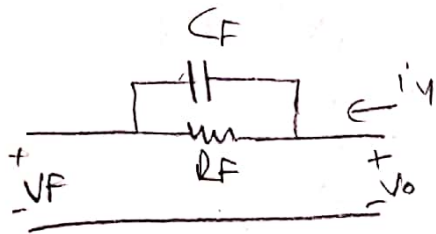

$$\beta(s) = \frac{-1}{R_F \frac{1}{sC_F}} = -R_F + \frac{1}{sC_F} = -\frac{1 + sC_F R_F}{R_F \frac{1}{sC_F}}$$

$$\beta(s) = -\frac{1}{R_F} \left[1 + \frac{s}{1/C_F R_F} \right] \quad \frac{-1}{R_F} = \beta \quad C_F \cdot R_F = \frac{1}{\omega_Z}$$

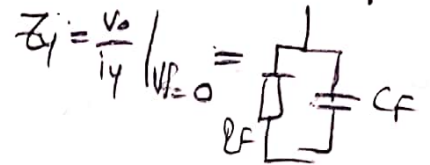
$$\beta(s) = \beta \cdot [1 + s\omega_Z]$$



$$\beta(s) = \frac{1}{V_0} \Big|_{V_F=0} = \frac{-i_Y}{V_0} \Big|_{V_F=0}$$

$$\beta(s) = \frac{-1}{R_F \parallel \frac{1}{sC_F}}$$

feedback network Analysis.

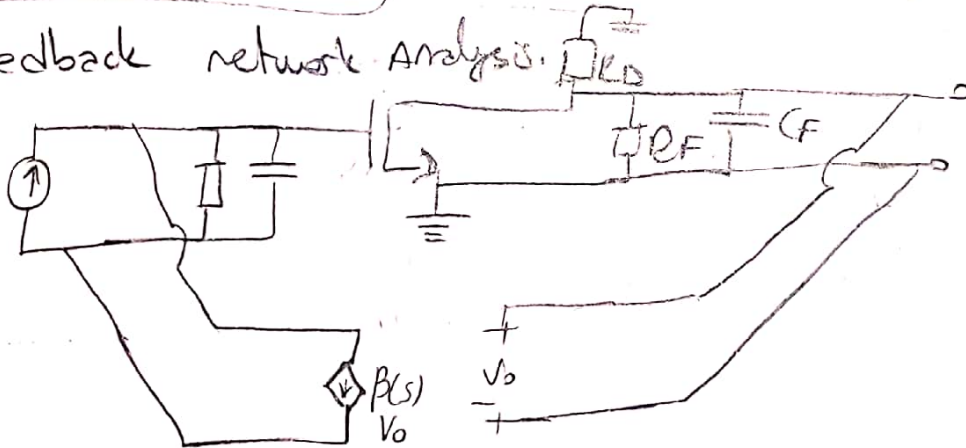

$$\beta = \infty$$

$$A_{TRA,f} = \frac{V_0}{V_F} = R_F (-g_{m1}) [R_D \parallel R_F \parallel r_{o1}] = -2.4 \times 10^6$$

$$r_{in, TRA, f} = R_F = 100k\Omega, \quad r_{out, TRA, f} = R_D \parallel R_F \parallel r_{o1} = 2k\Omega$$

$$\gamma_1 = R_F \cdot C_F \quad \gamma_2 = C_F (R_D \parallel R_F \parallel r_{o1})$$

$$\gamma_1 = 100k\Omega \cdot 10nF = 10^{-3}s$$

$$\gamma_2 = 10 \cdot 10^{-9} \cdot (2k\Omega \parallel 100k\Omega \parallel 12.5k\Omega)$$

$$\gamma_2 = 2 \times 10^{-5}s$$

$$\omega_{H, TRA} = \frac{1}{\gamma_1 + \gamma_2} = \frac{1}{100 \times 10^{-5} + 2 \times 10^{-5}} \approx \frac{1}{2 \times 10^{-5}} = \frac{100000}{2} = 5 \times 10^4 \text{ rad/s}$$

$$\omega_{H, TRA} = 5 \times 10^4 \text{ rad/s}$$

(9)

$$A_{TRA,fl}(j\omega) = \frac{A_{TRA,fl}}{1 + \frac{j\omega}{\omega_{H,TRA,fl}}} = \frac{-2.4 \times 10^6}{1 + \frac{j\omega}{5 \times 10^4}}$$

$$r_{in,f} = \frac{r_{in,TRA,f}}{1 + \beta \cdot A_{TRA,fl}} = \frac{100k\Omega}{1 + (-10^{-5}) \cdot (-2.4 \times 10^6)} \quad r_{in,TRA,f} = 100k\Omega$$

$\beta = -\frac{1}{R_F} = -\frac{1}{100k\Omega} = -10^{-5}$

$r_{out,TRA,f} = 2k\Omega$
 $A_{TRA,f} = -2.4 \times 10^6$

$$r_{in,f} = \frac{10^5}{25} = \frac{100.000}{25} = 4000 = 4k\Omega$$

$$r_{out,f} = \frac{R_{D1} || R_F || r_{out}}{1 + g_m [R_{D1} || R_F || r_{out}]} = \frac{2000}{1 + 1.2 \times 10^{-3} \cdot 2000} = \frac{2000}{2.5} = 800\Omega$$

$$A_f(j\omega) = \frac{A_{TRA,fl}(j\omega)}{1 + \beta(j\omega) \cdot A_{TRA,fl}(j\omega)} = \frac{-2.4 \times 10^6}{1 + \frac{j\omega}{5 \times 10^4}}$$

$$= \frac{A_{TRA,fl}}{1 + \beta \cdot \left[1 + \frac{j\omega}{\omega_2} \right] \frac{-2.4 \times 10^6}{1 + \frac{j\omega}{5 \times 10^4}}}$$

$$= \frac{A_{TRA,fl}}{1 + \frac{j\omega}{\omega_{H,TRA,f}} + A_{TRA,fl} \cdot \beta + \frac{j\omega}{\omega_2} \frac{A_{TRA,fl} \cdot \beta}{A_{TRA,fl} \cdot \beta}}$$

$$= \frac{A_{TRA,fl}}{1 + A_{TRA,fl} \cdot \beta} \cdot \frac{1}{1 + \frac{j\omega}{(1 + A_{TRA,fl} \cdot \beta) \cdot \left[\omega_{H,TRA,f} || \frac{\omega_2}{A_{TRA,fl} \cdot \beta} \right]}}$$

$$\omega_{H,f} = (1 + A_{TRA,fl} \cdot \beta) \left[\omega_{H,TRA,f} || \frac{\omega_2}{A_{TRA,fl} \cdot \beta} \right]$$

(10)

Compute the voltage gain

$$\frac{V_o}{V_s} = \frac{r_o}{R_s \frac{V_s}{R_s}} = \frac{1}{R_s} \cdot \frac{r_o}{r_s} = \frac{1}{R_s} \cdot A_f = \frac{1}{R_s} \cdot \frac{A_{TRA, fl}}{1 + \beta \cdot A_{TRA, fl}}$$

$$\text{Midband} = \frac{1}{R_s} \cdot \frac{-2.4 \times 10^6}{1 + 24} = \frac{-9.6 \times 10^4}{R_s}$$

$$\beta = -10^{-5}$$

$$A_{TRA, fl} = -2.4 \times 10^6$$




$$W_2 = \frac{1}{C_{RF}} = \frac{1}{1nF \cdot 100k} = 1000 rad/s$$

$$\frac{W_2}{A_{TRA,fp.\beta}} = \frac{1000}{-2.4 \times 10^6 \cdot 10^{-5}} = \frac{1000}{24} = 41.7 \text{ rad/s}$$

Q4. The MOS amplifier shown in Fig. P10.50 is biased to have the following small signal MOS parameters: $g_{m1} = 1.2 \text{ mA/V}$, $r_{o1} = 25 \text{ k}\Omega$, $g_{m2} = 1.6 \text{ mA/V}$, and $r_{o2} = 25 \text{ k}\Omega$. If $R_D = 1.5 \text{ k}\Omega$ then $R_{S1} = 500 \text{ k}\Omega$, $R_{S2} = 2 \text{ k}\Omega$ & $R_F = 8 \text{ k}\Omega$

(a) voltage gain without feedback $A = v_o/v_s$ (b) the voltage gain with feedback A_f ; (c) the feedback capacitor C_F to limit the high frequency $f_H = 50 \text{ kHz}$.

Current Amp. with Current Short

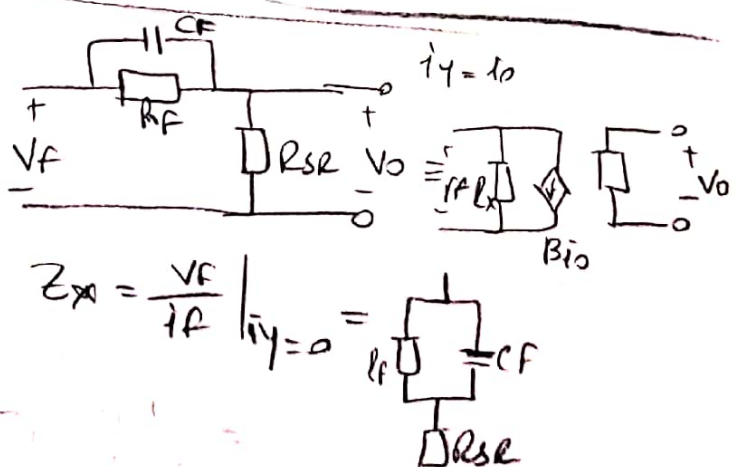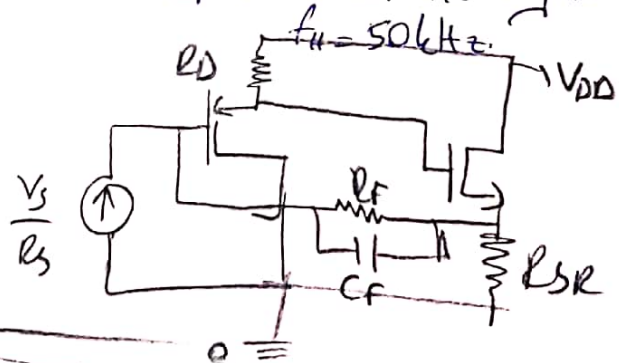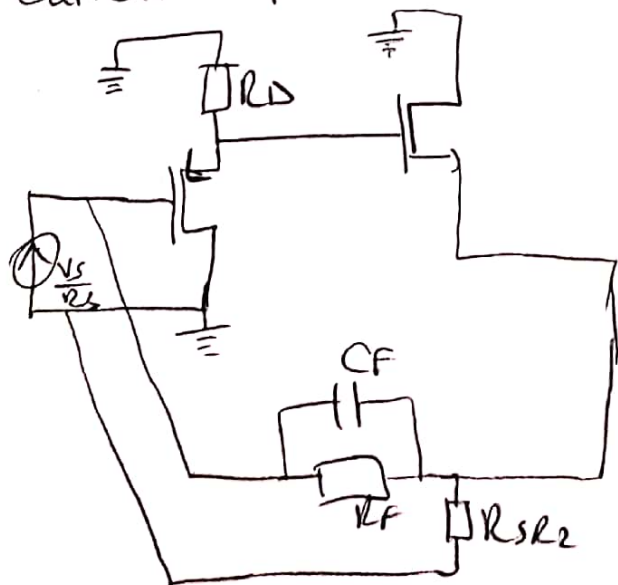

11


$$Z_y = \frac{V_o}{I_y} \Big|_{V_A=0} = \frac{R_{SR}}{1 + sC_F R_F} \parallel R_{SR}$$

$$\beta(s) = \frac{I_F}{I_y} \Big|_{V_A=0} = - \frac{R_{SR}}{R_{SR} + R_F \parallel \frac{1}{sC_F}}$$

$$\beta(s) = \frac{-R_{SR}}{R_{SR} + \frac{R_F \cdot \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}}} = - \frac{R_{SR}}{R_{SR} + \frac{R_F}{1+sC_F R_F}} = - \frac{R_{SR}(1+sC_F R_F)}{R_{SR} + R_F + sC_F R_F R_{SR}}$$

$$= - \underbrace{\frac{R_{SR}}{R_{SR} + R_F}}_{\beta} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \rightarrow \omega_z \rightarrow \beta \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \rightarrow \text{pole}$$

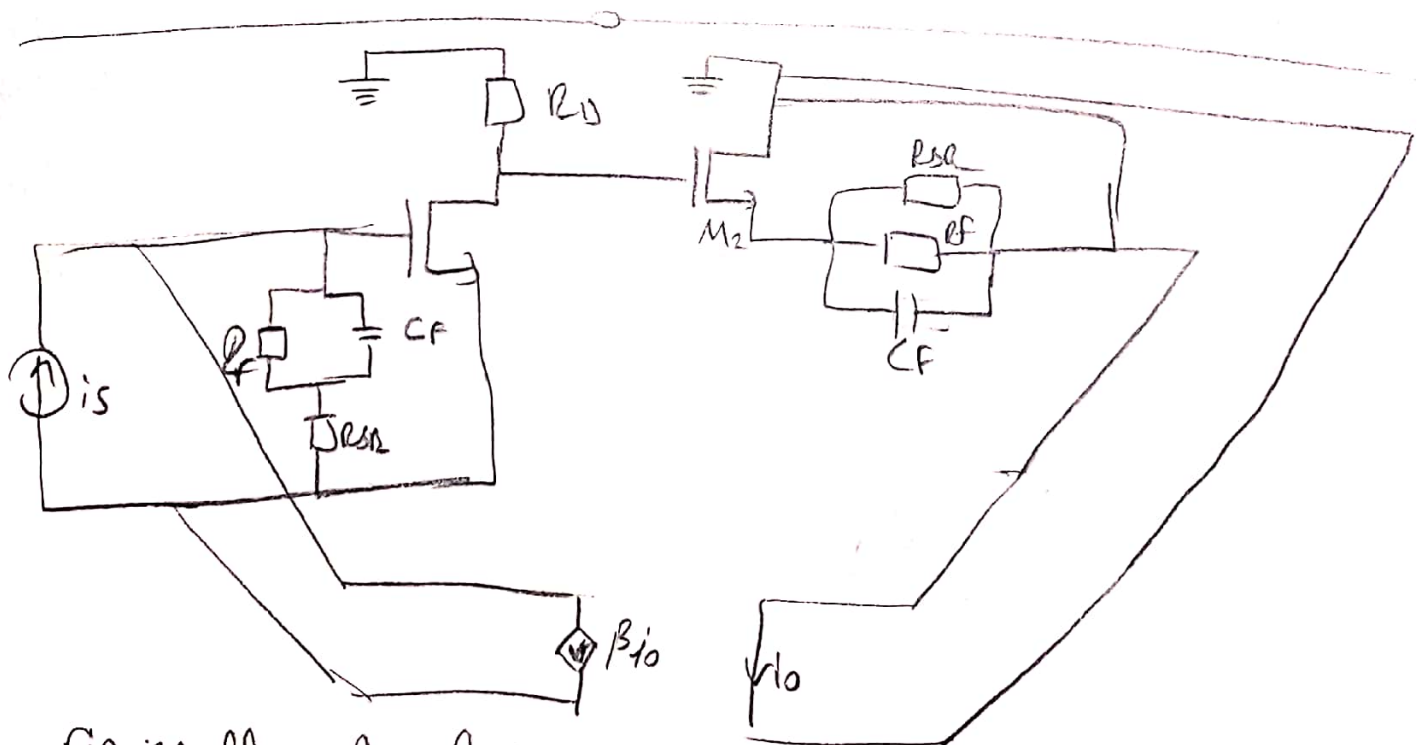$\frac{1}{C_F(R_F \parallel R_{SR})} \rightarrow \omega_p$




$$r_{in, CA, RL} = R_F + R_{SR}$$

$$r_{out, CA, RL} = r_{o2} (1 + g_{m2} (R_{SR} \parallel R_F))$$

$$A_{CA, RL} \approx (-g_{m1}) (R_D) \left[\frac{g_{m2}}{1 + g_{m2} (R_{SR} \parallel R_F)} \right] \cdot (R_F + R_{SR})$$

$W_{H,CA,fl}$, OCTC

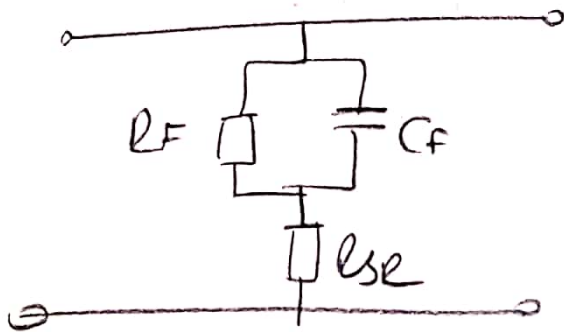


$$Y_1 = \frac{1}{R_F} \quad C_1 = C_F \quad R_1 = R_F$$

$$Y_1 = R_F C_F =$$

$$Y_1 = 800 \cdot C_F$$
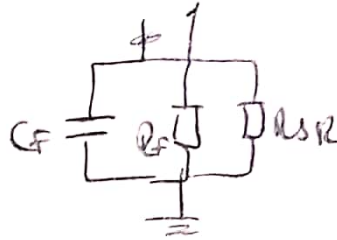
$$W_{H,CA,fl} \approx \frac{1}{625 \cdot C_F}$$



$$Y_2 = C_2 R_2 = 625 \cdot C_F$$

$$C_2 = C_F$$

$$R_2 = R_F \parallel R_{SR} \parallel \frac{1}{g_{m2}}$$

$800 \quad \ll 1400$

$$R_2 \approx \frac{1}{g_{m2}} = 625 \Omega$$

$$A_{CA,fl}(j\omega) = \frac{A_{CA,fl}}{1 + \frac{j\omega}{W_{H,CA,fl}}}$$

$$r_{in,fl} = \frac{r_{in,CA,fl}}{1 + \beta A_{CA,fl}} \rightarrow \text{giris por tunda yukseltici}$$

$$r_{out,fl} = r_{out,CA,fl} (1 + \beta A_{CA,fl}) \rightarrow \text{cikis por tunda zikeltici}$$

$$A(j\omega) = \frac{A_{CA,fl}(j\omega)}{1 + \beta(j\omega) A_{CA,fl}(j\omega)} = \frac{A_{CA,fl}}{1 + \frac{j\omega}{W_{H,CA,fl}}}$$

$$\approx \frac{A_{CA,fl} \left(1 + \frac{j\omega}{W_p} \right)}{1 + \frac{j\omega}{W_{H,CA,fl}} + \frac{j\omega}{W_p} + \frac{A_{CA,fl} \beta + \frac{j\omega}{W_z}}{A_{CA,fl} \beta}}$$

$$= \frac{A_{CA,fl}}{1 + \beta A_{CA,fl}} \cdot \frac{1 + \frac{j\omega}{W_p}}{1 + \frac{j\omega}{(1 + A_{CA,fl} \beta) [W_{H,CA,fl} \parallel W_p \parallel \frac{W_z}{A_{CA,fl} \beta}]}}$$

(13)