


HW.2

Q1. The circuit of fig 10.68 must provide a gain of 50 with $R_1 = R_2 = 5k\Omega$
 If $V_{A,N} = 5V$ and $V_{A,P} = 4V$ calculate the required tail current

ABDULLAH
 MEMİŞOĞLU
 171024001

P, X = Virtual ground node'lu için

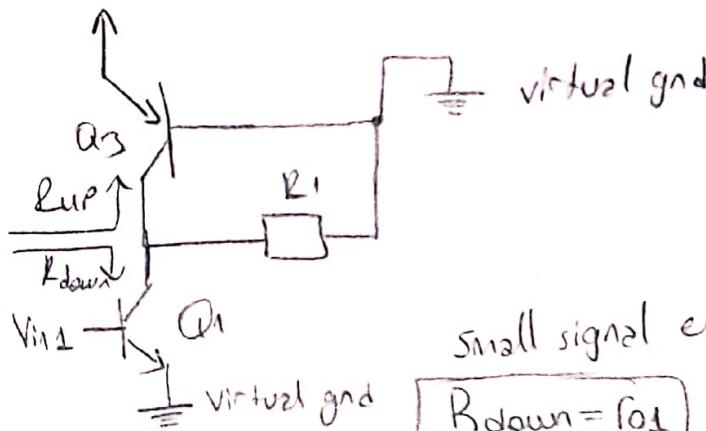
Differential mode half circuit çizilecek olursa;



Small signal esdeğer devresinde R_{up} ve R_{down} görülür.

$$R_{down} = r_{o1}$$

R_{up} elde etmek için:

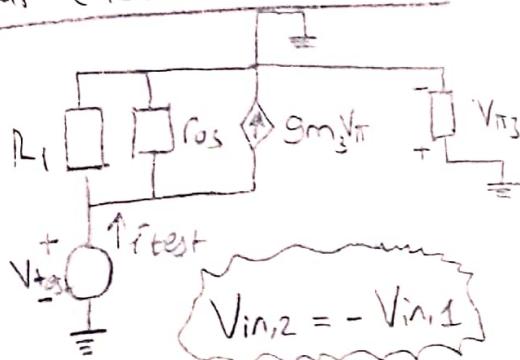

$$R_{up} = \frac{V_{test}}{I_{test}} = R_1 // r_{o3}$$

$$V_{t3} = 0$$


$$\frac{V_{out1}}{V_{in1}} = -g_{m1} [R_1 // r_{o3} // r_{o1}]$$

Common emitter configuration

$$\frac{V_{out2}}{V_{in2}} = \frac{V_{out}}{V_{in1} - V_{in2}} = -\frac{V_{out2} - V_{out1}}{V_{in2} - V_{in1}} = -g_{m1} [R_1 // r_{o3} // r_{o1}]$$

(1)


Common mode half circuit model oluştur

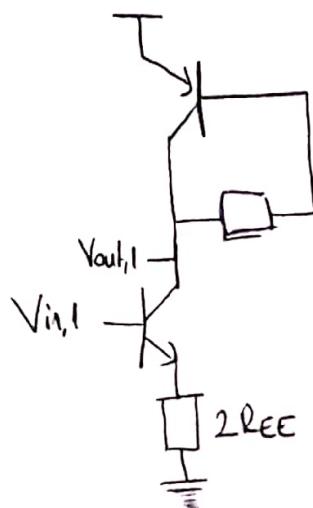

REE: Akım kaynağı için çıkış impedansı



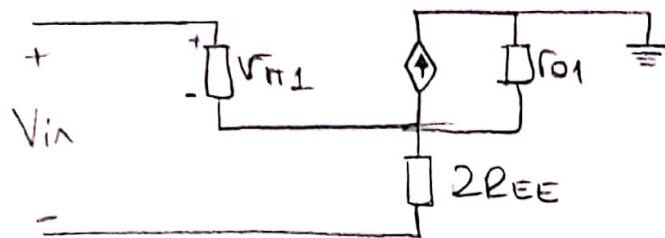short the output, compute $\frac{I_{out}}{V_{in}}$



$$-\frac{V_{\pi,1}}{R_{\pi,1}} + \frac{V_{in} - V_{\pi,1}}{R_E} - g_m V_{\pi,1} + \frac{V_{in} - V_{\pi,1}}{R_{O1}} = 0$$

$$I_{out} - \frac{V_{in} - V_{\pi,1}}{R_{O1}} + g_m V_{\pi,1} = 0$$

$$\frac{V_{\pi,1}}{R_E \parallel R_{O1}} = \frac{V_{\pi}}{R_{\pi} \parallel R_E \parallel \frac{1}{g_m} \parallel R_{O1}}$$

$$I_{out} + \frac{V_{\pi,1}}{R_{O1} \parallel \frac{1}{g_m}} = \frac{V_{in}}{R_{O1}} \rightarrow V_{\pi,1} = V_{in} \frac{\frac{1}{g_m} \parallel R_E}{R_E} \rightarrow V_{in} = \frac{V_{\pi,1}}{\frac{1}{g_m} \parallel R_E}$$


$$I_{out} + \frac{V_{\pi,1}}{\frac{1}{g_m} \parallel R_E} = 0 \rightarrow I_{out} = -\frac{V_{\pi,1}}{\frac{1}{g_m} \parallel R_E}$$

$$A_{TCA} = \frac{I_{out}}{V_{in}} = \frac{-\frac{V_{\pi,1}}{\frac{1}{g_m} \parallel R_E}}{\frac{V_{\pi,1}}{\frac{1}{g_m} \parallel R_E}} = -\frac{R_E}{\frac{1}{g_m} \cdot \frac{1}{g_m} \parallel R_E} = -\frac{g_m \cdot R_E}{\frac{1}{g_m} + R_E}$$

$$A_{TCA} = \frac{-g_m}{\frac{1}{g_m} \parallel R_E} = \frac{-g_m}{1 + g_m R_E} - A_{TCA} \quad \star$$

(2)

$r_{out, TCA}$ bulma için :

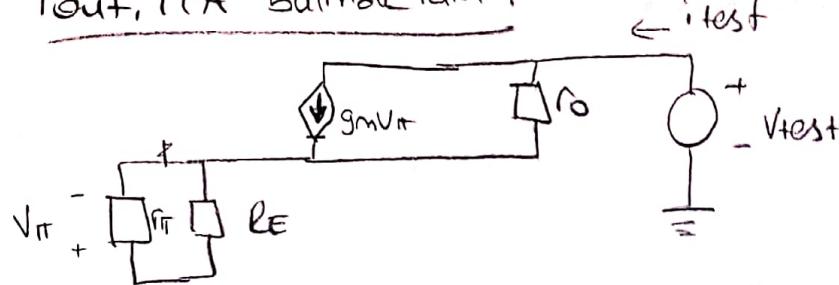


$$(\bar{i}_{test} g_m V_{\pi 1}) R_o + \bar{i}_{test} (r_{\pi 1} || R_E) = V_{test}$$

$$\bar{i}_{test} [R_o (1 + g_m (r_{\pi 1} || R_E)) + (r_{\pi 1} || R_E)] = V_{test}$$

$$\frac{V_{test}}{\bar{i}_{test}} \approx \boxed{R_o (1 + g_m R_E)} = r_{out, TCA}$$

eq. 3
 $r_{\pi 1} \gg R_E$
 $r_{\pi 1} || R_E \ll R_o (1 + g_m R_E)$

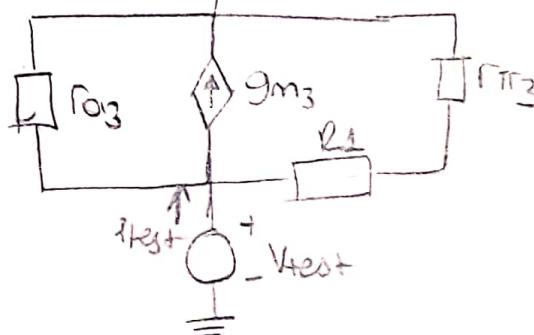R_{up} için devrenin üst kismı
small signal esdevri devresi çizilirse.



$$-\bar{i}_{test} + \frac{V_{test}}{R_o3} + g_m3 V_{\pi 3} + \frac{V_{test}}{R_1 + r_{\pi 3}} = 0$$

$$\boxed{V_{\pi 3} = V_{test} + \frac{r_{\pi 3}}{R_1 + r_{\pi 3}}}$$

$$-\bar{i}_{test} + \frac{V_{test}}{R_o3 || \frac{R_1 + r_{\pi 3}}{1 + \beta_3}} = 0$$

$$\boxed{R_{up} = \frac{V_{test}}{\bar{i}_{test}}}$$

$$\frac{V_{test}}{R_o3 || R_1 + r_{\pi 3}} = \bar{i}_{test} \rightarrow$$

$$\boxed{\frac{V_{test}}{\bar{i}_{test}} = R_o3 || \frac{R_1 + r_{\pi 3}}{1 + g_m3 r_{\pi 3}}}$$

$$\boxed{R_{up} = R_o3 || \frac{R_1 + r_{\pi 3}}{1 + g_m3 r_{\pi 3}}}$$

$$R_{UP} = R_O3 \parallel \frac{R_1 + r_{\pi 3}}{1 + g_{m3}r_{\pi 3}}$$

Common mode gain $g_{m1} = \frac{V_{out,1}}{V_{in,1}}$

$$A_{TCA} = \frac{-g_{m1}}{1 + g_{m1}R_E}$$

$$R_{out,TCA} = R_O1(1 + g_{m1}R_E)$$

$$\frac{V_{out,1}}{V_{in,1}} = A_{TCA} [R_{out,TCA} \parallel R_{UP}]$$

$$= \frac{-g_{m1}}{1 + g_{m1}R_E} \left[R_O1(1 + g_{m1}R_E) \parallel \left(R_O3 \parallel \frac{R_1 + r_{\pi 3}}{1 + g_{m3}r_{\pi 3}} \right) \right]$$

$$\frac{1}{R_O1(1 + g_{m1}R_E)} + \frac{1}{R_O3} + \frac{1}{R_1 + r_{\pi 3}} \\ 1 + g_{m1}R_E \gg \quad R_O3 \gg \quad \frac{1}{1 + g_{m3}r_{\pi 3}}$$

$$\frac{V_{out,1}}{V_{in,1}} = \frac{-g_{m1}}{1 + g_{m1}R_E} \cdot \left(\frac{\frac{1}{R_1 + r_{\pi 3}}}{\frac{1}{1 + g_{m3}r_{\pi 3}}} \right) = \frac{-g_{m1}}{1 + g_{m1}R_E} \cdot \left(\frac{1 + g_{m3}r_{\pi 3}}{R_1 + r_{\pi 3}} \right)$$

$$CMRR = \frac{\text{Differential mode gain}}{\text{Common mode gain}} = \frac{\frac{V_{out,1}}{V_{in,1}}}{\frac{V_{out,1}}{V_{in,1}}} = \frac{-g_{m1}[R_1 \parallel R_O3 \parallel R_O1]}{\frac{g_{m1}}{1 + g_{m2}R_E} \cdot \frac{1}{R_1 + r_{\pi 3}}}$$

$$R_O3 \gg R_1 \quad R_O1 \gg R_1$$

$$\left\{ \frac{-R_1 \cdot (1 + g_{m2}R_E) \cdot (R_1 + r_{\pi 3})}{(1 + g_{m3}r_{\pi 3})} \right\} = CMRR$$

4

Q_3 ve Q_4 'ün I_b 'lerini föhmal edilebilir

$$g_{m1} = \frac{I_{C1}}{V_T}$$

V_T : Termal Voltag $\rightarrow 26\text{mV}$
 I_{C1} : Q_1 'nın collector akımı

$$I_{C1} = I_{C2} = I_{C3} = I_{C4} = \frac{I_{EE}}{2}$$

$$R_L = 5\text{k}\Omega$$

$$r_{O3} = \frac{V_{A,P}}{I_{C3}} = \frac{4}{\frac{I_{EE}}{2}} = \frac{8}{I_{EE}} = r_{O3}$$

$$g_{m1} = \frac{I_{EE}}{2V_T} = \frac{I_{EE}}{52 \times 10^{-3}}$$

$$r_{O1} = \frac{V_{A,N}}{I_{C1}} = \frac{5}{\frac{I_{EE}}{2}} = \frac{10}{I_{EE}}$$

differential mode gain (düzeynden kaynaklı 50)

$$50 = g_{m1} [R_L \parallel r_{O3} \parallel r_{O1}]$$

$$50 = \frac{I_{EE}}{2V_T} \cdot \left[5k \parallel \frac{8}{I_{EE}} \parallel \frac{10}{I_{EE}} \right]$$

$$50 = \frac{I_{EE}}{2V_T} \cdot \left[\frac{1}{5000} + \frac{I_{EE}}{8} + \frac{I_{EE}}{10} \right]$$

$$50 = \frac{I_{EE}}{52 \times 10^{-3}} \cdot \left[\frac{8 + 9000 I_{EE}}{8500} \right]$$

$$50 = \frac{I_{EE}}{52 \times 10^{-3}} \cdot \left[\frac{9000 I_{EE} + 8}{40000} \right] = \frac{9000 I_{EE}^2 + 8 I_{EE}}{208} = 50$$

$$9000 I_{EE}^2 + 8 I_{EE} = 10400$$


$$I_{EE}^2 + \frac{8}{9000} I_{EE} - \frac{10400}{9000} = 0$$

$$-\frac{b \mp \sqrt{b^2 - 4ac}}{2a} = \frac{-8}{9000} \mp \sqrt{\frac{64}{81000000} + 4 \cdot 1 \cdot \frac{10400}{9000}} = \frac{-8}{9000} \mp \frac{2.169}{2} = 2.169$$

$$I_{EE} = 1.074 \text{ A}$$

$I_{EE} < 0$ olamaz
 bu yüzden ikinci kök gelmez. (5)

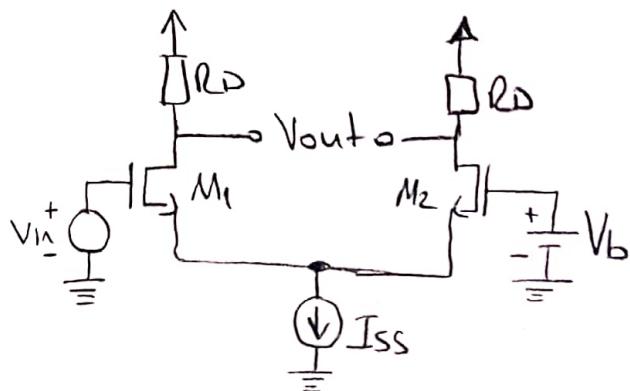Q2. A student has a single-ended voltage source constructs the circuits shown in Fig 10.75, hoping to obtain differential outputs. Assume perfect symmetry but $\lambda=0$ for simplicity.



- (a) Viewing M_1 as a common-source stage degenerated by the impedance seen at the source of M_2 , calculate V_x in terms of V_{in} .
- (b) Viewing M_1 as a source follower and M_2 as a common gate stage, calculate V_y in terms of V_{in} .
- (c) Add the result obtained in (a) and (b) with proper polarities. If the voltage gain is defined as $(V_x - V_y)/V_{in}$, how does it compare with the gain of differentially-driven pairs?

(a) Small signal equivalent

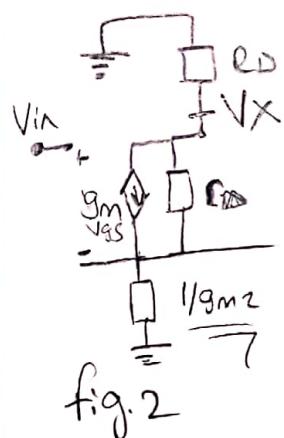


fig.2

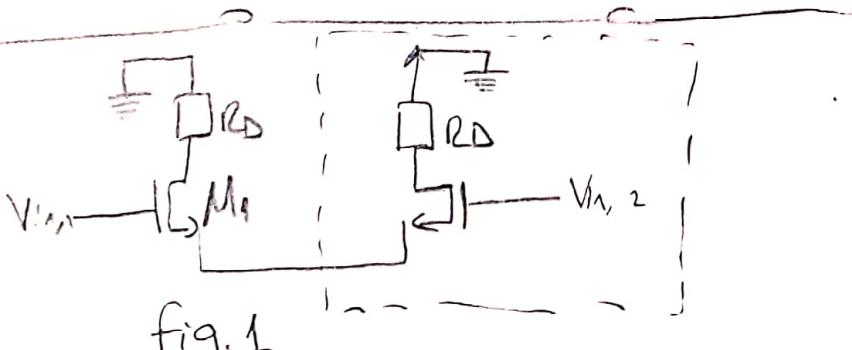


fig.1

$1/g_{m2}$ esdeger degerdir Devre önce fig 1'deki gibi incelenir sonrasında fig.2 elde edilir. fig.1'de farklı bölgelerin small signal esdeger impedansı $\frac{1}{g_{m2}}$ 'dur. fig 2'de fig 1 devresini small signal esdegerinin M_1 yarı devresi alınarak ve M_2 kismi için source'a $\frac{1}{g_{m1}}$ esdeger impedansı entegre edileseli oluşturulmuştur.

⑥

Q2.2.2 V_x : V_{in} cinsinden yazılabilmesi için $\frac{R_d \cdot R_s}{R_d + R_s}$

$\frac{V_x}{V_{in}} = t$ t bir sbt olmak üzere + degeri bulunmalıdır.

$$\frac{V_x}{V_{in}} = t = -g_{m1} \cdot \frac{1}{1 + g_{m1} \frac{1}{g_{m2}}} \cdot \left[R_D \parallel \text{r}_{out}, TCA \right]$$

hesaplamalı

$$r_{out, TCA} = \left(1 + g_{m1} r_{o1} \right) \underbrace{\frac{1}{g_{m2}}}_{\beta_1} + r_{o1} \quad \lambda = 0 \text{ verilmiştir} \quad \text{ve} \quad r_{o1} = +\infty$$

Simetriinin korunması için $g_m = g_{m1} = g_{m2}$

$$\frac{V_x}{V_{in}} = -g_m \cdot \frac{g_m}{2g_m} \cdot \left[\underbrace{\frac{R_D \cdot r_{out, TCA}}{R_D + r_{out, TCA}}}_{\frac{R_D}{2}} \right] \quad r_{o1} \rightarrow +\infty \quad r_{out, TCA} \rightarrow +\infty$$

$$\boxed{\frac{V_x}{V_{in}} = -g_m \cdot \frac{1}{2} \cdot R_D} \rightarrow \boxed{V_x = \left(-g_m \cdot \frac{1}{2} \cdot R_D \right) V_{in}}$$


(b) V_y 'yi V_{in} cinsinden bulabilmesi için;

$$\frac{V_y}{V_{in}} = t_2, \quad t_2 \text{ sbt} \quad t_2 = \alpha_1 + \alpha_2 \quad \text{Cascade yapısı.}$$

$\alpha_1 \rightarrow$ common drain'de gelen
 $\alpha_2 \rightarrow$ common gate'de gelen

$$\frac{V_y}{V_{in}} = \alpha_1 \cdot \alpha_2$$

α_1 için

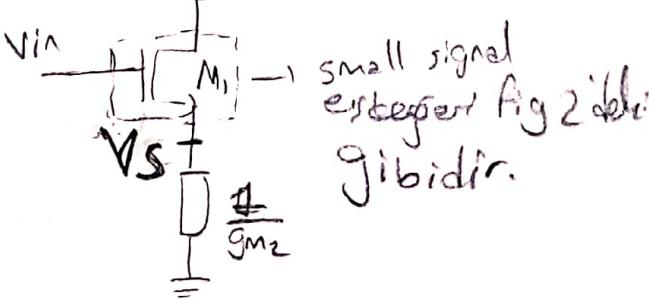


$$\frac{V_s}{V_{in}} = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} = \frac{\frac{1}{g_m}}{\frac{2}{g_m}} = \frac{1}{2} \parallel$$

(7)

Q:

(b.2)

Q2 (Common gate gain)

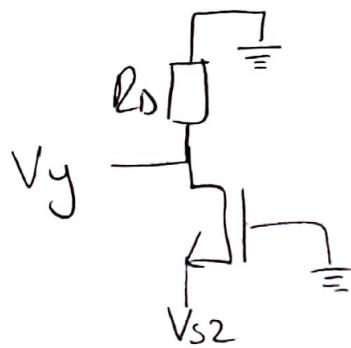In
H)

$$\frac{V_y}{V_{s2}} = g_m R_D = \underline{\underline{g_m R_D}}$$


$$\frac{V_y}{V_{in}} = \frac{V_y}{V_s} \cdot \frac{V_s}{V_{in}} = \frac{g_m R_D}{2}$$

$\underbrace{g_m R_D}_{\frac{1}{2}}$

$$\textcircled{c} \quad \frac{V_x}{V_{in}} = -\frac{g_m R_D}{2} \quad \frac{V_y}{V_{in}} = \frac{g_m R_D}{2}$$

Voltage gain = $\frac{V_x - V_y}{V_{in}} = -\underline{\underline{g_m R_D}}$

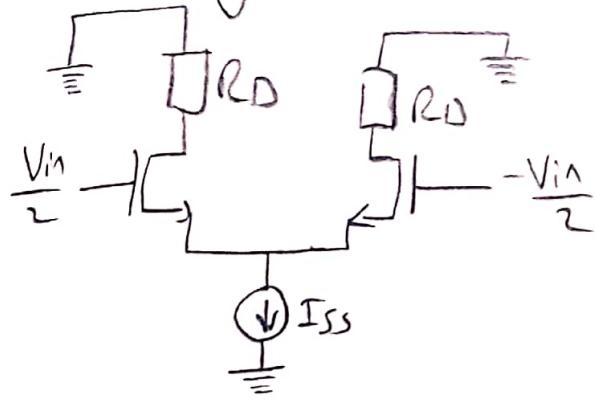V_x Differentially driven pairs ile de aynı voltage gain'i elde edip edemeysenizizi kontrol edelim



diff. mode half circuit

$$V_x = \left(\frac{V_{in}}{2} \right) \left[-g_{m1} (R_D || R_{D1}) \right]$$

$\lambda = 0$

$$V_x = -g_m R_D \frac{V_{in}}{2}$$

Virtual Gnd

$$V_y = \left(-\frac{V_{in}}{2} \right) \left[-g_{m2} (R_D || R_{D2}) \right]$$


$$V_y = \frac{g_m R_D \cdot V_{in}}{2}$$

$$\frac{V_x - V_y}{V_{in}} = -g_m R_D \frac{V_{in}}{2} - g_m R_D \frac{V_{in}}{2}$$


$$= g_m R_D //$$

(8)

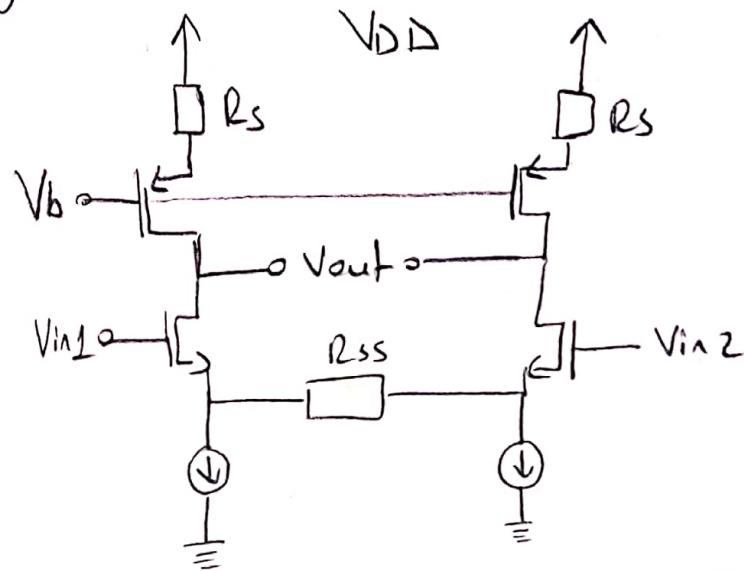
Q3. Calculate the differential voltage gain of the circuits depicted in Fig 10.77. Assume perfect symmetry and $\lambda > 0$. You may need to compute the gain as $A_v = -G_m R_{out}$ in some cases.



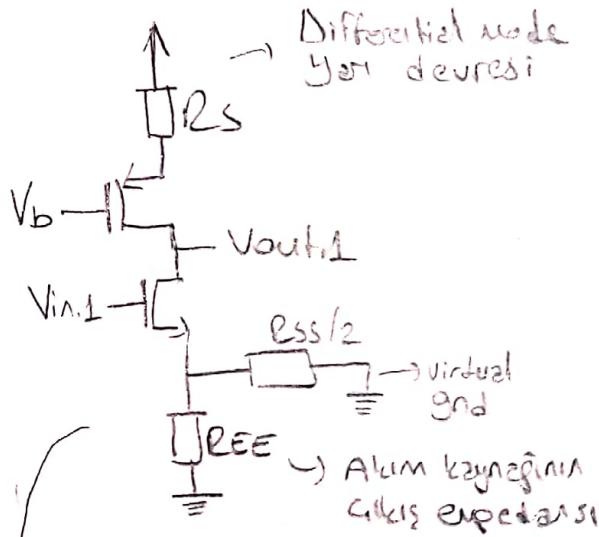Öncelikle Differential ve Common mode yan devreleri çizilmelidir:



Common Mode yan devresi

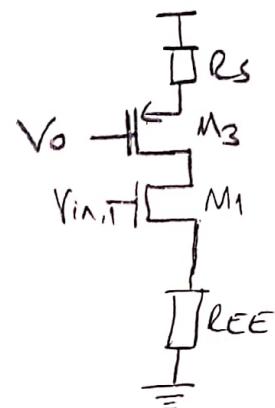

$$A_{TCA} = \frac{V_{out}}{V_{in}} = \frac{\frac{-V_F}{1/g_m}}{\frac{V_F}{1/g_m R_E}} = \frac{-g_m 1}{1 + g_m 1 R_E}$$

$$R_{out,TCA} = R_O (1 + g_m R_E)$$

syf 3 eq.3

$$R_E = R_{EE} \parallel \frac{R_{ss}}{2}$$

$$R_{up} = (1 + g_m 3 R_3) R_s + R_3$$

$\tilde{\beta}_3$

(9)

Differential Mode h.c

$$A_{TCA_1} = - \frac{g_{m_1}}{1 + g_{m_1} R_{E_1}}$$

$$R_{E_1} = R_{EE} \parallel \frac{R_{SS}}{2}$$

$$f_{out, TCA} = f_{o_1} (1 + g_{m_1} R_{E_1})$$

$$R_{up} = (1 + g_{m_3} f_{o_3}) R_S + f_{o_3}$$

$\underbrace{\qquad\qquad\qquad}_{B_3}$

Common Mode

$$A_{TCA_2} = - \frac{g_{m_2}}{1 + g_{m_2} R_{E_2}}$$

$R_{E_2} = R_{EE} \rightarrow R_{SS}$ ızdırda
züm seçim j.m.

$$f_{out, TCA} = f_{o_1} (1 + g_{m_2} R_{E_2})$$

$$R_{up} = (1 + g_{m_3} f_{o_3}) R_S + f_{o_3}$$

$\underbrace{\qquad\qquad\qquad}_{B_3}$

Differential Mode

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m_1}}{1 + g_{m_1} R_{E_1}} \cdot \left[f_{o_1} (1 + g_{m_1} R_{E_1}) \parallel (1 + g_{m_3} f_{o_3}) R_S + f_{o_3} \right]$$

$$R_{E_1} = R_{EE} \parallel \frac{R_{SS}}{2}$$

$R_{SS} \ll R_{EE}$ ise

$$R_{E_1} = \frac{R_{SS}}{2} \quad A_1$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m_2}}{1 + g_{m_1} \frac{R_{SS}}{2}} \cdot \left[f_{o_1} \left(1 + g_{m_1} \frac{R_{SS}}{2} \right) \parallel (1 + g_{m_3} f_{o_3}) R_S + f_{o_3} \right]$$

Common mode

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m_1}}{1 + g_{m_2} R_{E_2}} \cdot \left[f_{o_1} (1 + g_{m_2} R_{E_2}) \parallel (1 + g_{m_3} f_{o_3}) R_S + f_{o_3} \right]$$

$$R_{SS} \ll R_{EE} \text{ olduguunda}$$

$$A_2$$

$$\frac{-g_{m_1}}{1 + g_{m_1} \frac{R_{SS}}{2}}$$

$$\frac{A_1}{A_2} \text{ 21 olur.}$$

$$\frac{-g_{m_1}}{1 + g_{m_1} R_{EE}}$$

$$= \frac{(1 + g_{m_2} R_{EE})}{1 + g_{m_1} \frac{R_{SS}}{2}}$$

gündü $A_1 < A_2$

1 mali


$$\frac{-g_{m_1}}{1 + g_{m_2} R_{EE}}$$

$$B_1 \cdot A_1 = B_2 \cdot A_2 \text{ ise } A_1 < A_2$$

ise $B_1 > B_2$ (10)
olmali.

$$\frac{1 + g_m_2 R_{EE}}{1 + g_m_1 \frac{R_{SS}}{2 \beta_2}} > 1$$

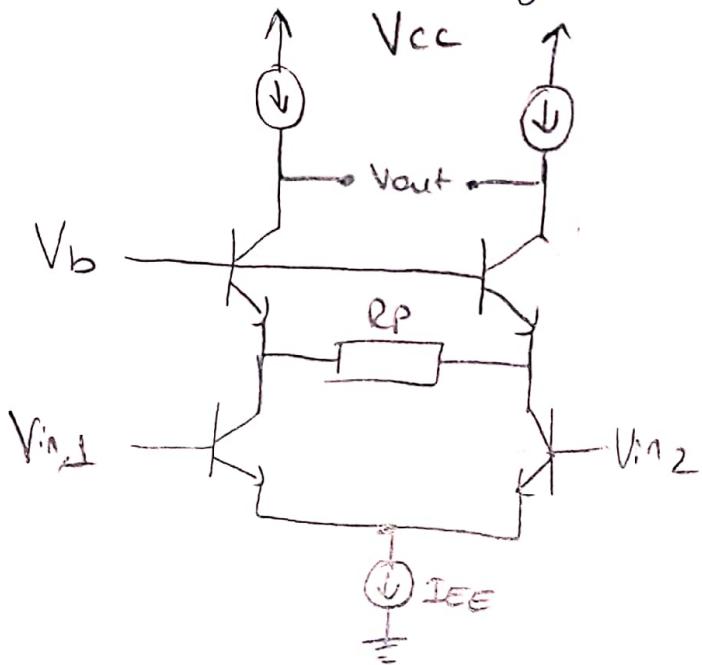Q4. Due to a manufacturing error, a parasitic resistance, R_P , has appeared in the circuit of Fig. 10.28 Calculate the voltage gain



Common base opamp small signal analysis


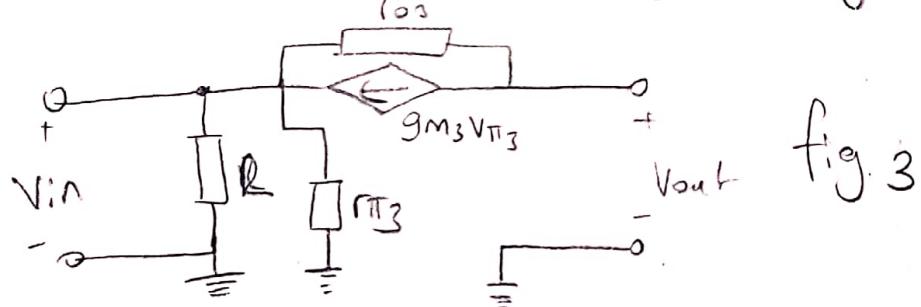


fig. 3

(11)

fig 3 devresinde girise V_{test} bajlaur kikis icin deure edilirse $r_{in,CA}$ elde edilir.

$r_{in,CA}$

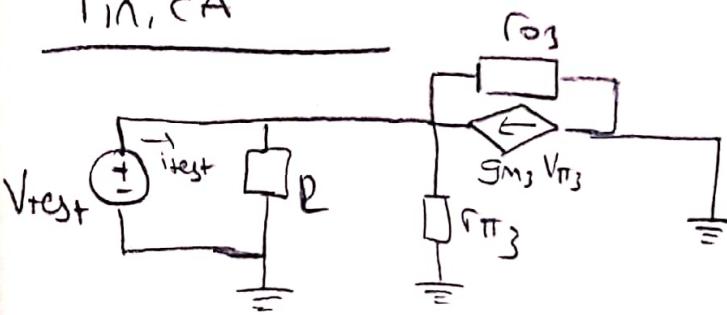

$$-i_{test+} + \frac{V_{test+}}{R} + \frac{V_{test+}}{r_{\pi_3}} + \frac{V_{test+}}{r_{o3}} - g_{m3} V_{\pi_3} = 0$$


$$V_{test+} = -V_{\pi_3}$$

$$\frac{V_{test+}}{i_{test+}} = r_{in,CA} = R \parallel r_{\pi_3} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \approx R \parallel \frac{1}{g_{m3}}$$

$$r_{in,CA} = R \parallel \frac{1}{g_{m3}}$$

$$r_{o3}, r_{\pi_3} \gg \frac{1}{g_{m3}}, R$$

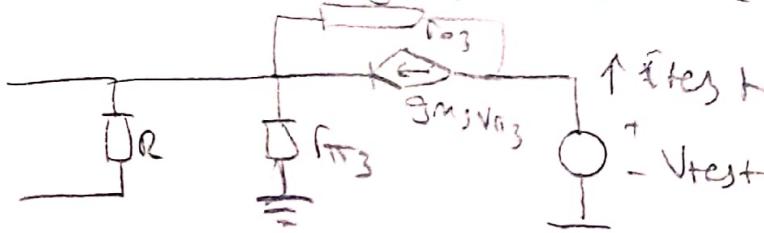$r_{out,CA}$ icin giris kicis deure gidersse V_{test}



$$i_{test+} \left[r_{o3} + \left(1 + g_{m3} r_{o3} \right) \left(r_{\pi_3} \parallel R \right) \right] = V_{test+}$$


$$\frac{V_{test+}}{i_{test+}} = r_{out,CA} = \left[r_{o3} + \left(1 + g_{m3} r_{o3} \right) \left(r_{\pi_3} \parallel R \right) \right]$$

$$r_{\pi_3} \gg R$$

$$r_{out,CA} = \left[\left(1 + g_{m3} r_{o3} \right) \cdot R + r_{o3} \right]$$

12

A_{CA} iin girisi için çıkış kisa devre

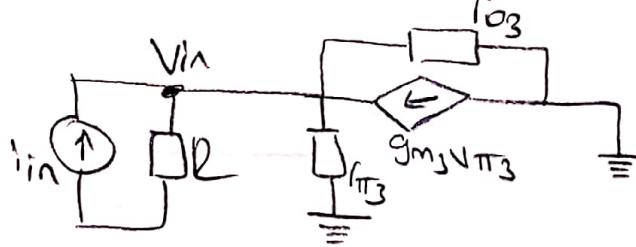

$$-i_{in} + \frac{V_{in}}{R} + \frac{V_{in}}{r_{\pi_3}} - g_m v_{\pi_3} + \frac{V_{in}}{r_{o3}} = 0 \quad v_{\pi_3} = -V_{in}$$

$$i_{out} + g_m v_{\pi_3} - \frac{V_{in}}{r_{o3}} = 0$$

$$\frac{V_{in}}{r_{in}} = R // r_{\pi_3} // r_{o3} // \frac{1}{g_m}$$

$$i_{in} = \frac{V_{in}}{R // r_{\pi_3} // r_{o3} // \frac{1}{g_m}}$$

$r_{\pi_3}, r_{\pi_3} \gg R, \frac{1}{g_m}$

$$\frac{V_{in}}{\frac{1}{g_m} // R}$$

$$i_{out} = \frac{V_{in}}{1/g_m // r_{o3}} \approx \frac{V_{in}}{1/g_m}$$

$$A_{CA} = \frac{i_{out}}{i_{in}} \approx \frac{\frac{V_{in}}{1/g_m}}{\frac{V_{in}}{1/g_m}} = \frac{1}{1/g_m // R}$$


$$A_{CA} = \frac{\frac{1}{g_m} // R}{1/g_m}$$

$$A_{CA} = \frac{\frac{1}{g_m} \cdot R}{\left(\frac{1}{g_m} + R \right) \cdot \frac{1}{g_m}} = \frac{R}{\frac{1+g_m R}{g_m}}$$

$$= \boxed{\frac{g_m \cdot R}{1+g_m \cdot R} = A_{CA}}$$

(13)

Differential mode gain denesi

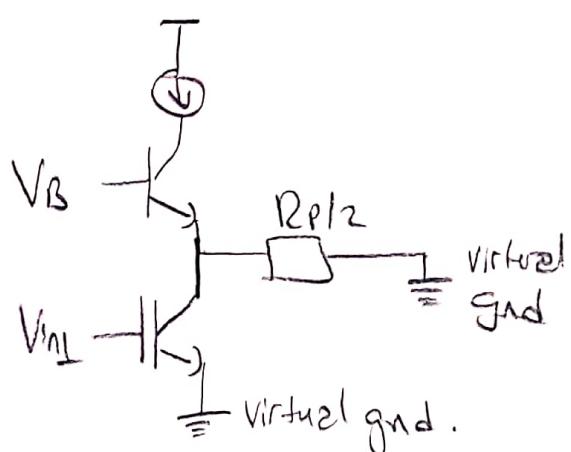

$$A_{TCA} = -g_{m1} \quad A_{CA} = \frac{g_{m3}R}{1+g_{m3}R}$$

$$R_{es} = f_{o1} \parallel R_{D1/2}$$

$$G = A_{TCA} \cdot A_{CA} \quad \left(\begin{array}{l} TCA \text{ ve CA kaskat-} \\ \text{lamaasinden delay} \end{array} \right)$$

$$R_{out} = f_{out, CA}$$


$$\text{Voltage gain} = \frac{V_{out}}{V_{in}} = G \cdot R_{out} = -g_{m1} \cdot \left(\frac{g_{m3}R}{1+g_{m3}R} \right) \cdot \left((1+g_{m3}f_{o3})R + f_{o3} \right)$$

$$f_{out, CA} = ((1+g_{m3}f_{o3})R + f_{o3})$$

$$\boxed{\text{Voltage gain} = -g_{m1} \left(\frac{g_{m3}R}{1+g_{m3}R} \right) \cdot \left((1+g_{m3}f_{o3})R + f_{o3} \right)}$$

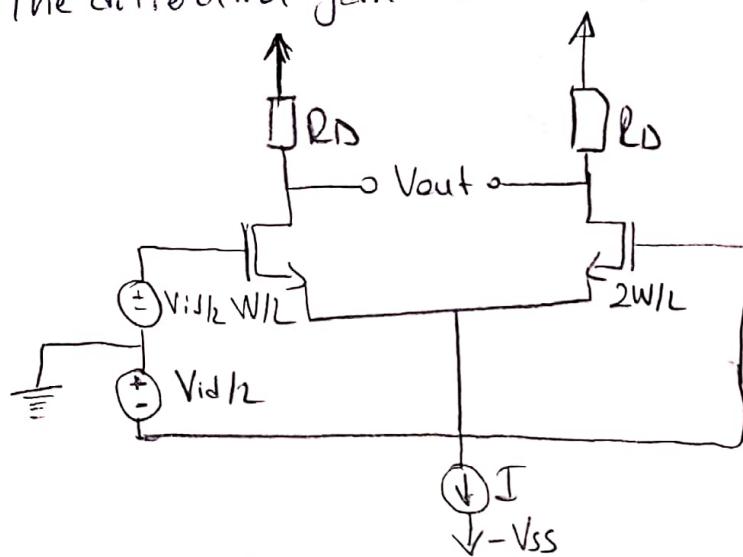Q5. A design error has resulted in a gross mismatch in the circuit of fig P7.14. Specifically, Q_2 has twice the W/L ratio of Q_1 . If V_{id} is a small sine-wave signal, find:

- I_{D1} and I_{D2}
- V_{out} for each of Q_1 and Q_2 .
- The differential gain A_d in terms of R_D , I and V_{out}



$$I_D = \frac{1}{2} M_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \quad I = I_{D1} + I_{D2}$$

$$V_{G1} = V_{G2} = 0$$

$$V_{S1} = V_{S2} = V_S \rightarrow$$

$$I_{D1} = \frac{1}{2} M_n C_{ox} \frac{W}{L} (0 - V_S - V_T)^2$$

$$I_{D2} = \frac{1}{2} M_n C_{ox} \frac{2W}{L} (0 - V_S - V_T)^2$$

$$= \frac{1}{2} M_n C_{ox} \frac{W}{L} (-V_S - V_T)^2 + \frac{1}{2} M_n C_{ox} \frac{2W}{L} (-V_S - V_T)^2 = \frac{3}{2} M_n C_{ox} \frac{W}{L} (-V_S - V_T)^2$$

$$2I_{D1} = I_{D2}$$

$$I = \frac{3}{2} M_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \rightarrow \sqrt{\frac{2I}{3M_n C_{ox} \frac{W}{L}}} = V_{GS} - V_T$$

$$g_m = \frac{2I_D}{(V_{GS} - V_T)} \rightarrow g_{m1} = \frac{2I_{D1}}{\sqrt{\frac{2I}{3M_n C_{ox} \frac{W}{L}}}}$$

$$g_{m2} = \frac{2I_{D2}}{\sqrt{\frac{2I}{3M_n C_{ox} \frac{W}{L}}}}$$

$$I_{D1} = \frac{I}{3}$$

$$I_{D2} = \frac{2I}{3}$$

$$g_{m1} = \frac{2I}{3 \cdot \sqrt{\frac{2I}{3M_n C_{ox} \frac{W}{L}}}}$$

$$g_{m2} = \frac{4I}{3 \sqrt{\frac{2I}{3M_n C_{ox} \frac{W}{L}}}}$$

(15)

$$V_{o1} = -g_{m1} \frac{V_d}{2} R_D$$

$$V_{o2} = -g_{m2} \left(-\frac{V_d}{2} \right) R_D$$

Differentiel mode gain = $\frac{V_{o2} - V_{o1}}{V_d}$

$$\frac{V_{o2} - V_{o1}}{V_d} = \frac{g_{m2} \frac{V_d}{2} R_D + g_{m1} \frac{V_d}{2} R_D}{V_d} =$$


$$= \frac{\frac{4I}{3} \sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}} \cdot \frac{R_D}{2} + \frac{2I}{3} \sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}} \cdot \frac{R_D}{2}}{V_d}$$

$$= \left(\frac{4I}{3} + \frac{2I}{3} \right) \cdot \frac{R_D}{2} \cdot \frac{1}{\sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}}}$$

$$= 2I \cdot \frac{R_D}{2} \cdot \frac{1}{\sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}}} = \boxed{\frac{I \cdot R_D}{\sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}}}} = \text{differential gain}$$

(16)

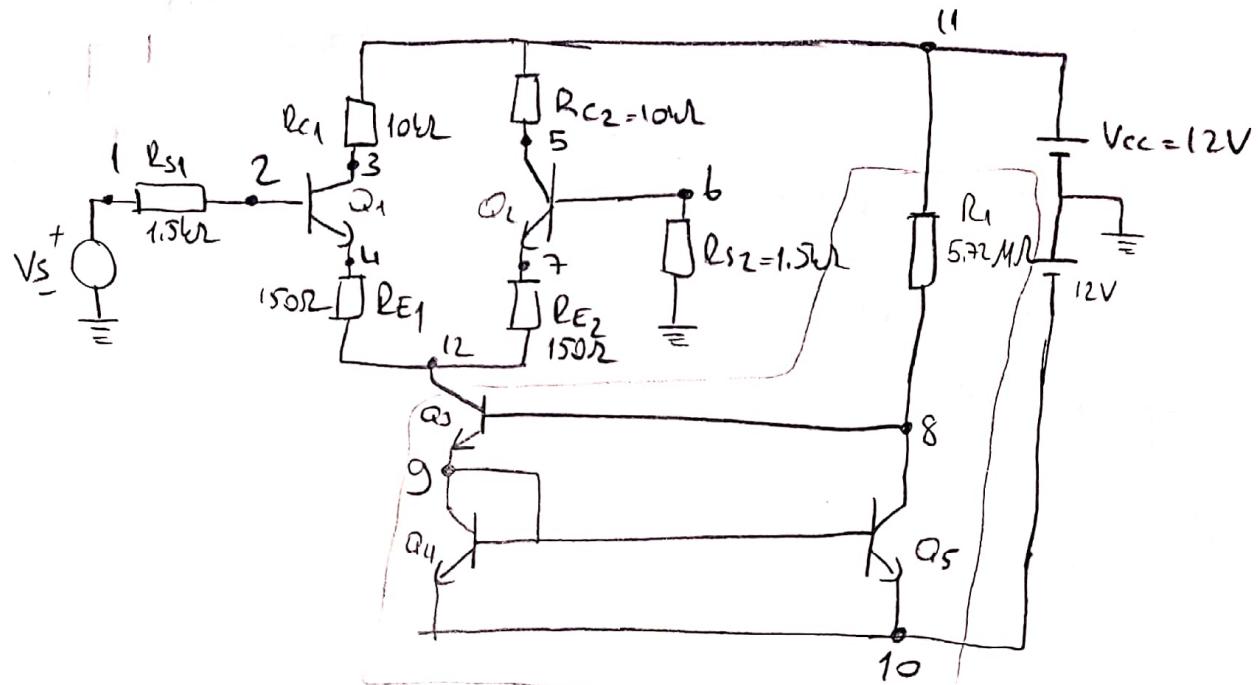Q6. A differential amplifier is shown in Fig. Pg.3g. The transistors are identical. Assume $V_{BE} = 0.7V$, $V_T = 26mV$, $\beta_F = 50$, and $V_A = 40V$. Calculate the values of A_d , R_{id} , A_c , R_{ic} and CMRR.



V_{11} = Voltage of node 11

current source

$$V_{11} = 12V \quad V_{10} = -12V \quad V_8 = -V_{10} + V_{BE4} + V_{BE3}$$

$$V_{11} = 12V, \quad V_{10} = -12V, \quad V_8 = -10.6V$$

$$I_{ref} = \frac{V_{11} - V_8}{5.72M\Omega} = 3.951MA = I_{ref}$$

$$I_{ref} \approx I_{tail}$$

$$\frac{V_A}{I_{tail}} = f_{og} \quad \frac{V_{tail}}{V_A} = \left(1 + \frac{\beta_3}{2}\right) \quad R_{tail} = \frac{V_{tail}}{I_{tail}} = \frac{V_{tail}}{V_A} \cdot \frac{V_A}{I_{tail}}$$


$$R_{tail} = f_{og} \cdot \left(1 + \frac{\beta_3}{2}\right)$$

$$\left(1 + \frac{\beta_3}{2}\right) \cdot f_{og}$$


1
17

Devrede current source devresi yerine Rtail esdeğeri eklenerek devre yeniden kurulursa.

V_C

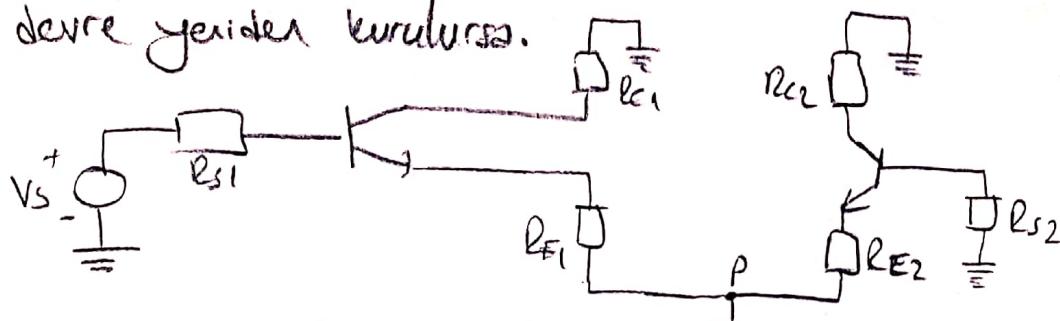

Burada simetri olduğu görülmeye.

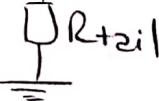

$$\left. \begin{array}{l} R_{C1} = R_{C2} \\ R_{E1} = R_{E2} \\ R_{S1} = R_{S2} \end{array} \right\} g_m_1 = g_m_2$$

$$g_m_1 = \frac{|I_{tail}|}{2} \cdot \frac{1}{V_T} = \frac{|I_{tail}|}{52mV}$$


$$I_{C1} = I_{C2}$$

$$A = R_P = R_{tail} \parallel [R_E + \frac{1}{g_m}]$$

$$R_{id} \approx [1 + g_m(R_E + R_P)] r_{pi1}$$

common base gain

C

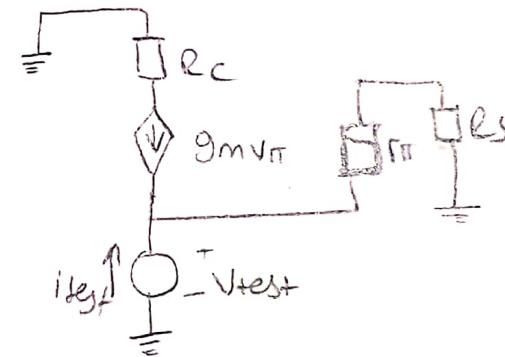

$$V_O = -g_m V_{Pi} R_C$$

$$V_O = -g_m R_C \left(-V_{test} - \frac{R_C}{R_C + R_S} V_{test} \right)$$

$$\frac{V_O}{V_{test}} = g_m R_C \cdot \frac{\frac{R_C}{R_C + R_S}}{1} \quad (R_C \gg R_S)$$

$$\frac{V_O}{V_{test}} = \underline{\underline{g_m R_C}}$$

$$\frac{V_{E1}}{V_{B1}} = \frac{R_E + R_P}{R_E + R_P + \frac{1}{g_m}}$$

$$\frac{V_{C2}}{V_S} = A_d = \frac{\frac{R_E R_P}{R_E + R_P + \frac{1}{g_m}} \cdot \frac{R_P}{R_E + R_P} \cdot \frac{R_P}{R_E} \cdot \frac{1}{g_m + R_E}}{1}$$

D

$$\frac{V_{B1}}{V_S} = \frac{R_{id}}{R_S + R_{id}}$$


$$\frac{V_P}{V_{B1}} = \frac{R_P}{R_P + R_E}$$

$$\frac{V_{E2}}{V_P} = \frac{1/g_m}{\frac{1}{g_m} + R_E}$$

Voltage
divider

18

Common mode half circuit

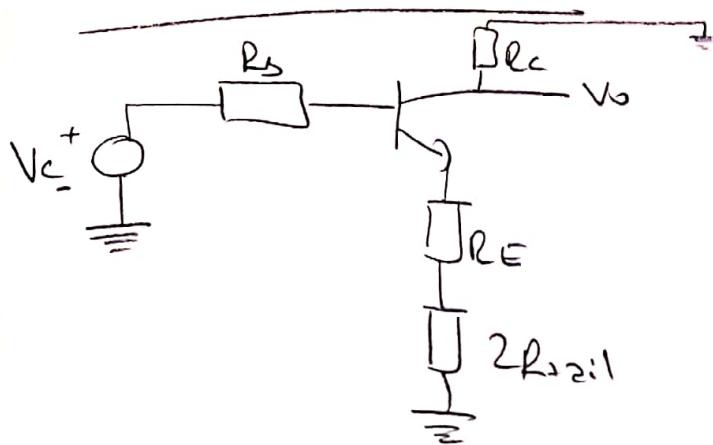

$$A_C = \frac{V_o}{V_c} = \frac{V_{B1}}{V_c} \cdot \frac{V_o}{V_{B1}} = \frac{R_{ic}}{R_{ic} + R_s} \left[-g_m \frac{1}{1 + g_m(R_E + 2R_{tail})} \right] \underbrace{(R_c || R_{out, CA})}_{R_c \ll R_{out}}$$

$$A_C = \frac{R_{ic}}{R_{ic} + R_s} \left[-g_m \frac{1}{g_m(R_E + 2R_{tail}) + 1} (R_c) \right]$$

$$CMRR_L = \left| \frac{A_d}{A_c} \right| = \frac{R_{id} \cdot R_p \cdot \frac{1}{g_m}}{\left(R_E + R_p + \frac{1}{g_m} \right) \cdot \left(R_s + R_{id} \right) \cdot \left(\frac{1}{g_m} + R_E \right)} \\ \left(\frac{R_{ic}}{R_{ic} + R_s} \right) \cdot \left(-g_m \cdot \frac{1}{g_m(R_E + 2R_{tail}) + 1} \cdot R_c \right)}$$

$$R_{ic} = [1 + g_m(R_E + 2R_{tail})] r_o$$

$$r_o = \frac{V_A}{I_{tail}} = 10.124 M\Omega$$

$$R_{id} = [1 + g_m(R_{E1} + R_p)] r_{ITL}$$

$$R_{tail} = R_o \left(1 + \frac{\beta_3}{2} \right) = 263.22 M\Omega$$

$$R_{id} = [1 + 7.598 \times 10^{-5} (150 + 6.66m\Omega)].$$

$$g_m = \frac{I_{tail}}{52mV} = 7.598 \times 10^{-5} \text{ S}^{-1}$$

$$R_{id} = 1.01 \Omega$$

$$R_{ic} = [1 + 7.59 \times 10^{-5} (2.263.22 \times 10^6 \Omega)]$$

$$R_{ic} = [1 + 19761.5] = 19.762 k\Omega$$

$$R_p = \frac{1}{R_{tail}} + \frac{1}{R_E + \frac{1}{g_m}} \\ \frac{1}{50} + \frac{1}{13k}$$

$$R_p \approx \frac{1}{150} = 6.66 m\Omega$$

19

$$\begin{aligned}
 CMRR &= \left| \frac{A_d}{A_c} \right| = \frac{\frac{R_{id} \cdot R_P \cdot \frac{1}{g_m}}{(R_E + R_P + \frac{1}{g_m}) \cdot (R_S + R_{id}) \cdot (\frac{1}{g_m} + R_C)}}{\left(\frac{R_{id} \cdot C}{R_{id} + R_S} \right) \cdot \left(\frac{-g_m \cdot R_C}{(R_E + 2R_{T21L}) \cdot g_m + 1} \right)} \\
 &= \frac{(1.01) \cdot (6.66 \times 10^{-3}) \cdot (13.161 \times 10^3)}{(150 + 6.66 \times 10^{-3} + 13.161 \text{m}\Omega) \cdot (1.5k\Omega + 1.01\Omega) \cdot (13.161 \text{m}\Omega + 150)} \quad \frac{1}{g_m} = 13.161 \text{m}\Omega \\
 &\quad \left(\frac{19.742 \text{k}\Omega}{19.742 \text{k}\Omega + 1.5 \text{k}\Omega} \right) \cdot \left(-7.598 \times 10^{-5} \cdot \left(\frac{10 \text{k}\Omega}{7.598 \times 10^{-5} (150 + 2.263.2 \text{m}\Omega) + 1} \right) \right) \\
 &= \frac{88.528}{2.598 \times 10^{11}} = \frac{(88.528) \cdot (37.128 \times 10^3)}{2.598 \times 10^{11}} \\
 &\quad (0.929) \cdot (39965) + 1
 \end{aligned}$$

$$CMRR = 1.2651 \times 10^{-5}$$

20