

```

% HW11
% Abdullah MEMİŞOĞLU
% 171024001

close all
clear classes
clear all

A1 = 2;
A2 = 3;
f1 = 10^6;
f2 = 20*10^6;
w1 = 2*pi*f1;
w2 = 2*pi*f2;
N = 2000;
t = [0:N-1] / N * 1 / f1;



Sig1 = A1*sin(w1*t);
Sig2 = A2*sin(w2*t);
Sig3 = cos( (w2-w1) * t );
Sig4 = cos( (w1+w2) * t );
Sig = Sig1.*Sig2;
Sig5 = 1/2 * A1 * A2 * ( Sig3 - Sig4 );
figure(101)
h1 = plot(t , Sig)
hold off;
hold on;
h2 = plot(t , A2*Sig1 );
hold off;
hold on;
h3 = plot(t , -A2*Sig1 );
hold off;
grid on;

xlabel('Time (s)');
ylabel('Voltage (V)');
title('Modulated Signal')

figure(102)
h4 = plot(t , Sig5 );
hold off;
grid on;

xlabel('time (s)');
ylabel('Voltage (V)');
title('Modulated Signal')

```

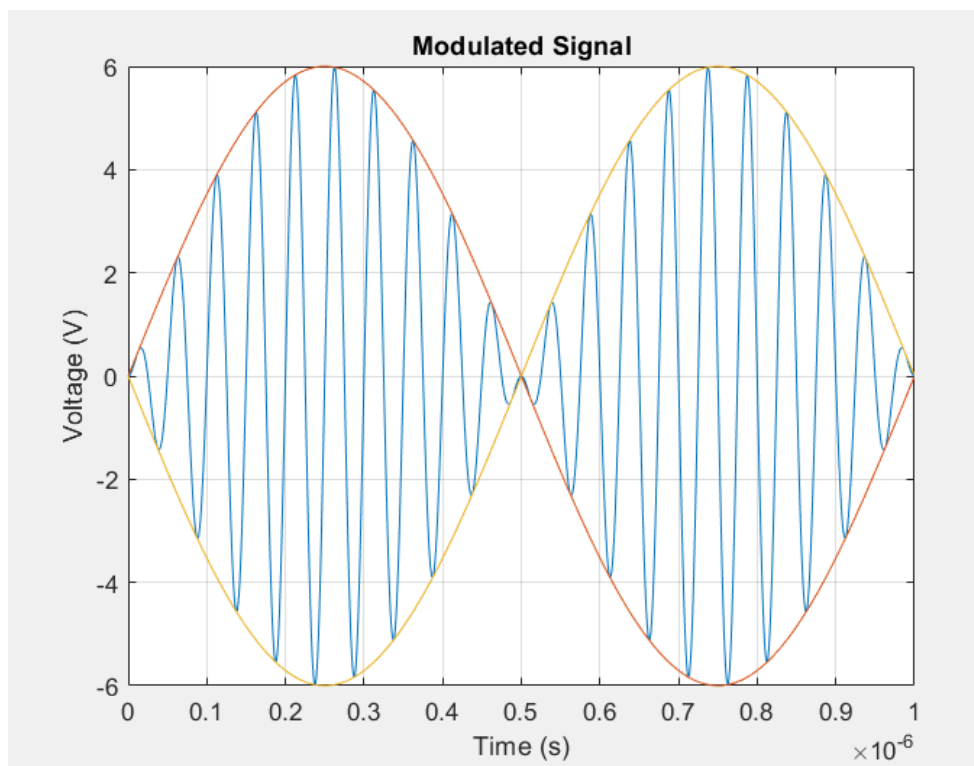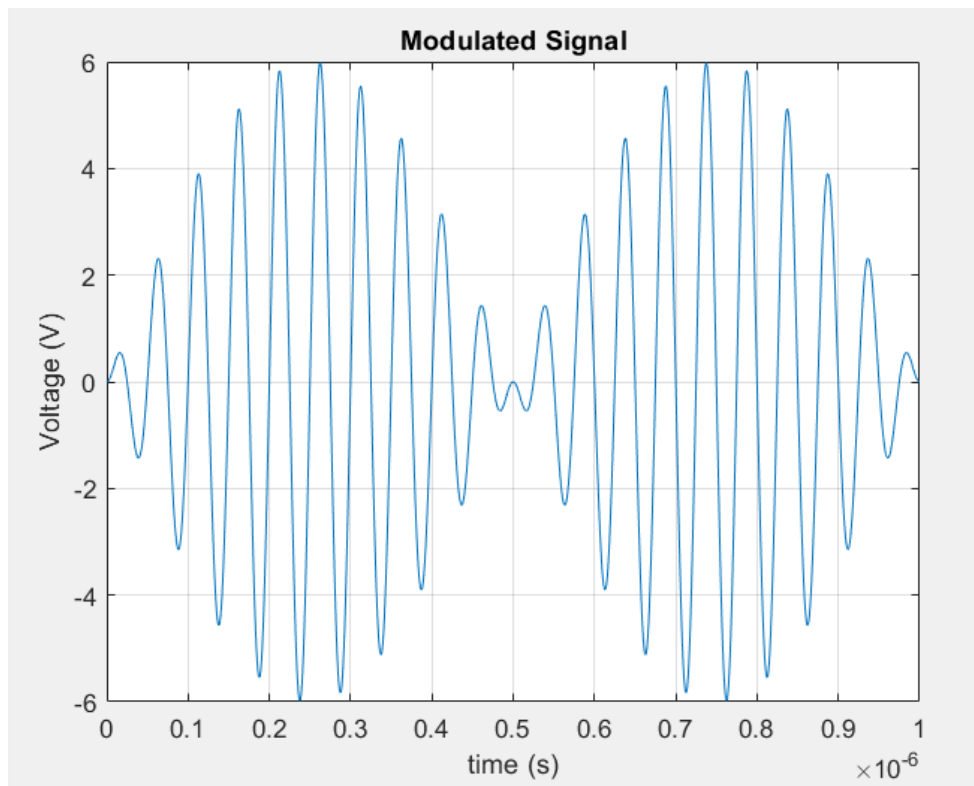

Q2

HW. 11

Abdullah Murtazogh
12124001

Q2. A large number of radio stations transmit their programs at various carrier frequencies. A radio receiver is tuned to receive an AM wave transmitted at a carrier frequency of $f_{RF} = 980 \text{ kHz}$. The LO inside the receiver is set at $f_{LO} = 1435 \text{ kHz}$.

find: (a) The frequencies coming out of the receiver's mixer:

(b) Which frequency is IF.

(c) The frequency of a radio station which would represent an image frequency to the radio station. (d) The frequency graph of the frequencies involved.

* Mixer outputs two frequencies

$$f_{RF} + f_{LO} = 980 \text{ kHz} + 1435 \text{ kHz} = 2415 \text{ kHz} //$$


$$|f_{RF} - f_{LO}| = 455 \text{ kHz} //$$

$f_{IF} \rightarrow$ intermediate frequency $\rightarrow 455 \text{ kHz} \rightarrow$ (b)

f_{IF} when mixer with the signal with f_{LO} :

$$f_{LO} - f_{IF} = 1435 \text{ kHz} - 455 \text{ kHz} = 980 \text{ kHz}$$
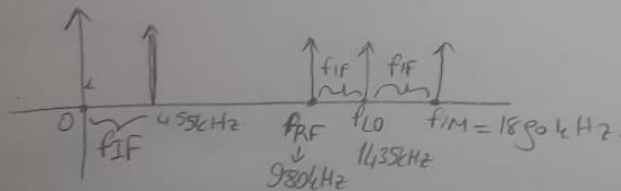
$$f_{LO} + f_{IF} = 1435 \text{ kHz} + 455 \text{ kHz} = 1890 \text{ kHz} //$$




(1)

Q3

Q3. Prepare a short report on the Q factor of LC resonators, on how it relates to bandwidth and signal attenuation

Q-factor of a series LC

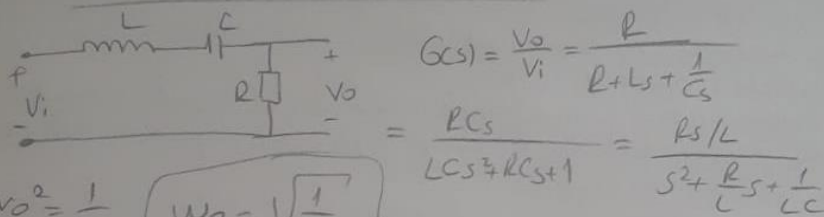

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

↳ resonant frequency

$$G(s) = \frac{2\delta\omega_0 s}{s^2 + 2\delta\omega_0 s + \omega_0^2}$$

$$2\delta\omega_0 = \frac{R}{L} \Rightarrow 2\delta \frac{1}{\sqrt{LC}} = \frac{R}{L} \quad \delta = \frac{R}{2} \sqrt{\frac{L}{C}}$$

$$G(j\omega) = \frac{2\delta\omega_0 j\omega}{(\omega_0^2 - \omega^2) + 2\delta\omega_0 j\omega} \quad G(j\omega)|_{\omega=\omega_0} = 1$$

$$|G(j\omega)|^2 = \frac{1}{2}$$

$$\frac{(2\delta\omega_0\omega)^2}{(\omega_0^2 - \omega^2)^2 + (2\delta\omega_0\omega)^2} = \frac{1}{2}$$

$$(2\delta\omega_0\omega)^2 = (\omega_0^2 - \omega^2)^2$$

$$|2\delta\omega_0\omega| = |\omega_0^2 - \omega^2|$$

$$\omega_L = -\delta\omega_0 + \omega_0\sqrt{1 + \delta^2}$$

$$\omega_H = \delta\omega_0 + \omega_0\sqrt{1 + \delta^2}$$

$$2\delta\omega_0\omega = \omega_0^2 - \omega^2 \quad \text{eq. 1} \rightarrow \text{Low freq.}$$

$$-2\delta\omega_0\omega = \omega_0^2 - \omega^2 \quad \text{eq. 2} \rightarrow \text{high freq. or first high then low}$$


$$\text{Bandwidth} = \omega_H - \omega_L = 2\delta\omega_0 = \frac{2R}{2} \sqrt{\frac{C}{L}} \cdot \frac{1}{\sqrt{LC}} = \frac{R}{L}$$

$$\boxed{BW = \frac{R}{L}} \quad Q = \frac{\omega_0}{BW} = \frac{1/\sqrt{LC}}{R/L} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q$$

2

Q4

Q4. A tuned RF amplifier has an LC tank with $Q=20$ and it is tuned at RF frequency to estimate the attenuation of the image signal, if the image frequency is 10% higher than RF signal.

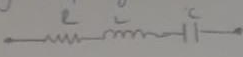Series RLC \rightarrow 

$$G(s) = \frac{R/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}, BW = \frac{R}{L}, Q = \frac{\omega_0}{BW}$$

$$G(s) = \frac{\frac{\omega_0}{Q} \cdot s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} = \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$G(j\omega) = \frac{j\omega \cdot \omega_0}{Q} \rightarrow |G(j\omega)|^2 = \frac{\omega^2 \omega_0^2}{Q^2} = \left(\frac{1}{A}\right)^2$$

$$|G(j\omega)|^2 = \frac{(k/Q)^2}{(1-k^2)^2 + \left(\frac{k}{Q}\right)^2} = \left(\frac{1}{A}\right)^2$$

$k = 1.1$ or $Q = 20$ is in

$$\left(\frac{1}{A}\right)^2 = \frac{(1.1/20)^2}{(1-1.1^2)^2 + \left(\frac{1.1}{20}\right)^2} = 0.06 \rightarrow \frac{1}{A} = 0.253 \rightarrow A = 3.946$$

$$20 \log_{10} A = 11.925 \text{ dB}$$

(3)