

HW-10

Abdullah MEMİŞOĞLU

171024001


Am

Q1. If the phase Margin of an amplifier is $PM=40^\circ$ and the Magnitude of the open loop gain is $|A(j\omega)|=50$, find the magnitude of the closed-loop gain $|A_f(j\omega)|$.

β is real and open-loop amp. is a two pole system.

$$A(j\omega) = \frac{A \rightarrow 50}{(1 + \frac{j\omega}{\omega_1})(1 + \frac{j\omega}{\omega_2})} \quad \omega_1 \ll \omega_2$$

$$\rightarrow 20 \log_{10} |\beta \cdot A(j\omega)| = 20 \log_{10} |A(j\omega)| - 20 \log_{10} \left| \frac{1}{\beta} \right|$$

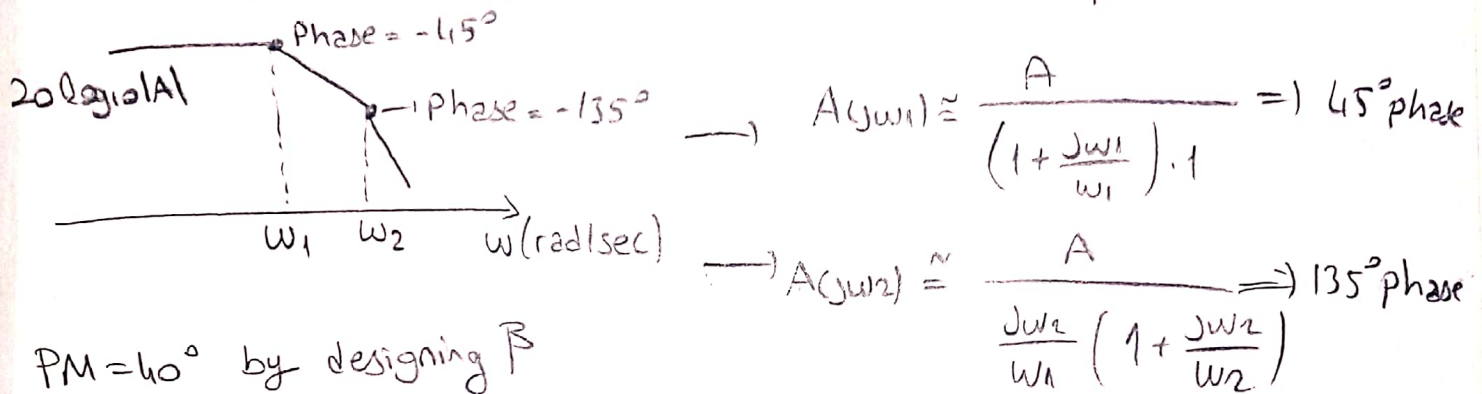


$PM=40^\circ$ by designing β

$PM = 180^\circ - |\angle A(j\omega_u)\beta|$ ω_u : unity gain frequency for loop gain

$T_L(j\omega) = A(j\omega) \cdot \beta \rightarrow \beta > 0$ and β real

$$20 \log_{10} |A(j\omega) \cdot \beta| = 20 \log_{10} |A(j\omega)| - 20 \log_{10} \left| \left(\frac{1}{\beta} \right) \right|$$

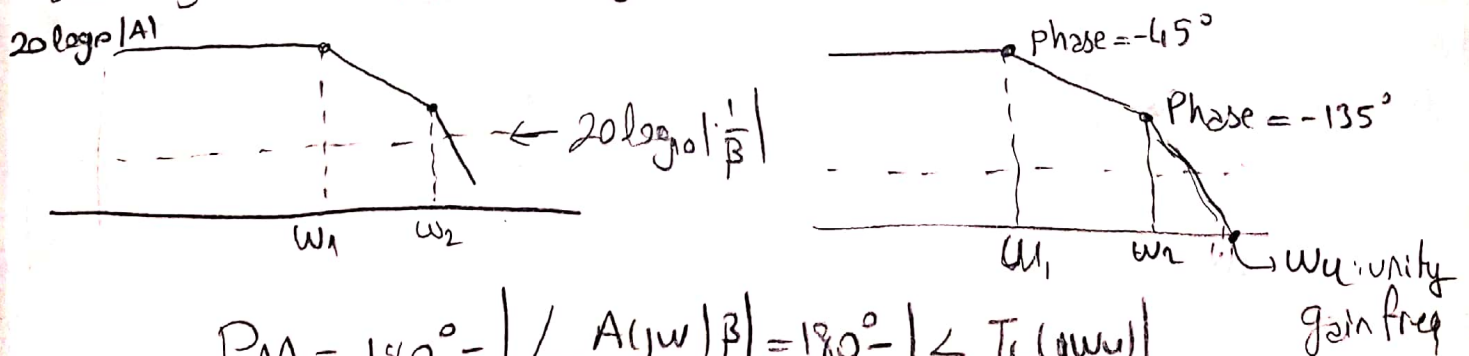

$$PM = 180^\circ - |\angle A(j\omega) \beta| = 180^\circ - |\angle T_L(j\omega_u)|$$

$$|T_L(j\omega_u)| = 140^\circ \quad \angle T_L(j\omega_u) = -140^\circ$$

1

$$T_L(j\omega_u) = \frac{A\beta}{\left(1 + \frac{j\omega_u}{\omega_1}\right) \cdot \left(1 + \frac{j\omega_u}{\omega_2}\right)} \approx \frac{A\beta}{\left(\frac{j\omega_u}{\omega_1}\right) \left(1 + \frac{j\omega_u}{\omega_2}\right)} \quad \begin{matrix} \omega_u \gg \omega_1 \\ \omega_u \gg \omega_2 \end{matrix}$$

$$\angle T_L(j\omega_u) = -90^\circ - \arctan\left(\frac{\omega_u}{\omega_2}\right) = -140^\circ$$

$$\arctan\left(\frac{\omega_u}{\omega_2}\right) = 50^\circ \rightarrow \frac{\omega_u}{\omega_2} = 1.1917 \rightarrow \omega_u = 1.1917 \omega_2$$

$$|T_L(j\omega_u)| = 1 \approx \frac{A\beta}{\left(\frac{\omega_u}{\omega_1}\right) \sqrt{1 + \frac{\omega_u^2}{\omega_2^2}}}$$

$$\frac{\omega_u}{\omega_1} \cdot \sqrt{1 + (1.1917)^2} = 50\beta$$

$$\beta = \frac{\omega_u}{\omega_1} \cdot 0.0311$$

$$\frac{\omega_u}{\omega_1} = \frac{\omega_2}{\omega_1} \cdot \frac{\omega_u}{\omega_2} = 1.1917 \cdot$$

$$\beta = \frac{\omega_2}{\omega_1} \cdot 0.0370$$

$$A_f = \frac{A}{1 + \beta A}$$

$$A_f = \frac{50}{1 + 1.853 \cdot \frac{\omega_2}{\omega_1}} \quad \star$$

Q2. The open loop gain of an amplifier has break frequencies at $f_{p1} = 10\text{kHz}$, $f_{p2} = 100\text{kHz}$, $f_{p3} = 1\text{MHz}$. The low-frequency gain is $A_0 = 250$, and the feedback factor is $\beta = 0.9$. Calculate the gain margin GM and the phase margin PM.

$$A(j\omega) = \frac{A_0}{\left(1 + \frac{jf}{f_1}\right) \cdot \left(1 + \frac{jf}{f_2}\right) \cdot \left(1 + \frac{jf}{f_3}\right)} = \frac{250}{\left(1 + \frac{jf}{10\text{kHz}}\right) \cdot \left(1 + \frac{jf}{100\text{kHz}}\right) \cdot \left(1 + \frac{jf}{1\text{MHz}}\right)}$$

$$A(jf) \cdot \beta = \frac{250 \cdot 0.9}{1} = \frac{225}{1}$$

$$|A(jf) \cdot \beta| = 1 = \frac{225}{\left|1 + \frac{jf_u}{10\text{k}}\right| \cdot \left|1 + \frac{jf_u}{100\text{k}}\right| \cdot \left|1 + \frac{jf_u}{1\text{MHz}}\right|}$$

(2)

$$|A(jf_u)\beta| = 1 = \frac{225}{\sqrt{1 + \frac{f_u^2}{(10k)^2}} \cdot \sqrt{1 + \frac{f_u^2}{(100k)^2}} \cdot \sqrt{1 + \frac{f_u^2}{(1MHz)^2}}} = 1$$

$$(225)^2 = \left(1 + \frac{f_u^2}{(10k)^2}\right) \cdot \left(1 + \frac{f_u^2}{(100k)^2}\right) \cdot \left(1 + \frac{f_u^2}{(1MHz)^2}\right)$$

$$5.062 \times 10^4 = \frac{(10^8 + f_u^2)}{10^8} \cdot \frac{(10^{10} + f_u^2)}{10^{10}} \cdot \frac{(10^{12} + f_u^2)}{10^{12}}$$

$$5.062 \times 10^{34} = (10^8 + f_u^2) \cdot (10^{10} + f_u^2) \cdot (10^{12} + f_u^2)$$

$$5.062 \times 10^{34} = 10^8 \left(1 + \frac{f_u^2}{10^8}\right) \cdot 10^{10} \left(100 + \frac{f_u^2}{10^8}\right) \cdot 10^8 \left(10000 + \frac{f_u^2}{10^8}\right)$$

$$5.062 \times 10^{10} = (2+1) \cdot (2+100) \cdot (2+10000)$$

$$= 2^3 + 100 \cdot 2^2 + 10000 \cdot 2^2 + 10^6 \cdot 2 + 2^4 + 100 \cdot 2 + 10^4 \cdot 2 + 10^6$$

$$2^3 + 10000 \cdot 2^2 + 10^6 \cdot 2 - 5.062 \times 10^{10} = 0$$

syms f(2)

$$f(2) = 2^3 + 10000 \cdot 2^2 + 10^6 \cdot 2 - 5.062 \times 10^{10}$$

$$\text{sol} = \text{vpasolve}(f) \rightarrow 2_1 = -9308.3490$$

$$2_2 = -2703.3080386$$

$$2_3 = 2011.657060$$

$$2 > 0 \text{ olacağından } 2 = \frac{f_u^2}{10^8}$$

$$2 = \frac{f_u^2}{10^8} = 2011.657 \rightarrow f_u^2 = 2011.657 \times 10^8 \rightarrow f_u = 448.51 \text{ kHz}$$



$$\angle A(jf_u)\beta \approx -190.25^\circ - 180^\circ \quad PM = -10.25^\circ$$

$$\angle A(jf_0)\beta = -180^\circ \quad (f_0 \approx 331 \text{ kHz})$$

3

$$|A(j\omega) B| = \frac{225}{\underbrace{\sqrt{1 + \left(\frac{3316 \text{ Hz}}{10^4 \text{ Hz}}\right)^2}}_{33.115} \underbrace{\sqrt{1 + \left(\frac{3316}{100^4}\right)}_{3.457} \cdot \underbrace{\sqrt{1 + \left(\frac{3316}{1M}\right)^2}}_{1.053}} \approx 1.8665$$

$$GM = 20 \log_{10} |1| - 20 \log_{10} |1.8665| = -5.420 \text{ dB}$$

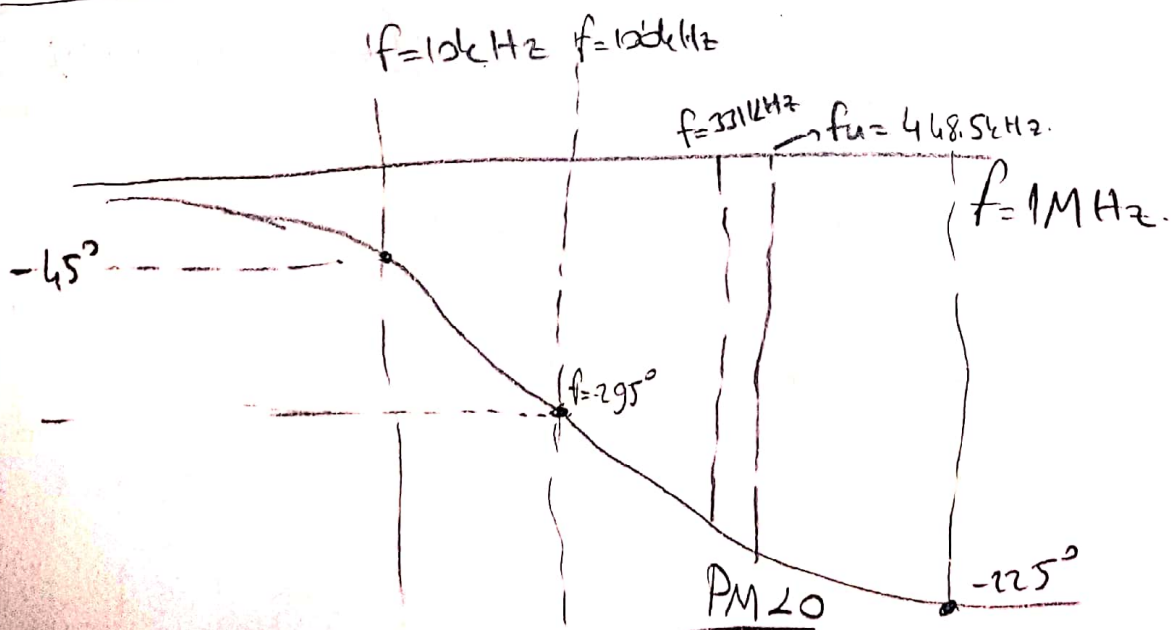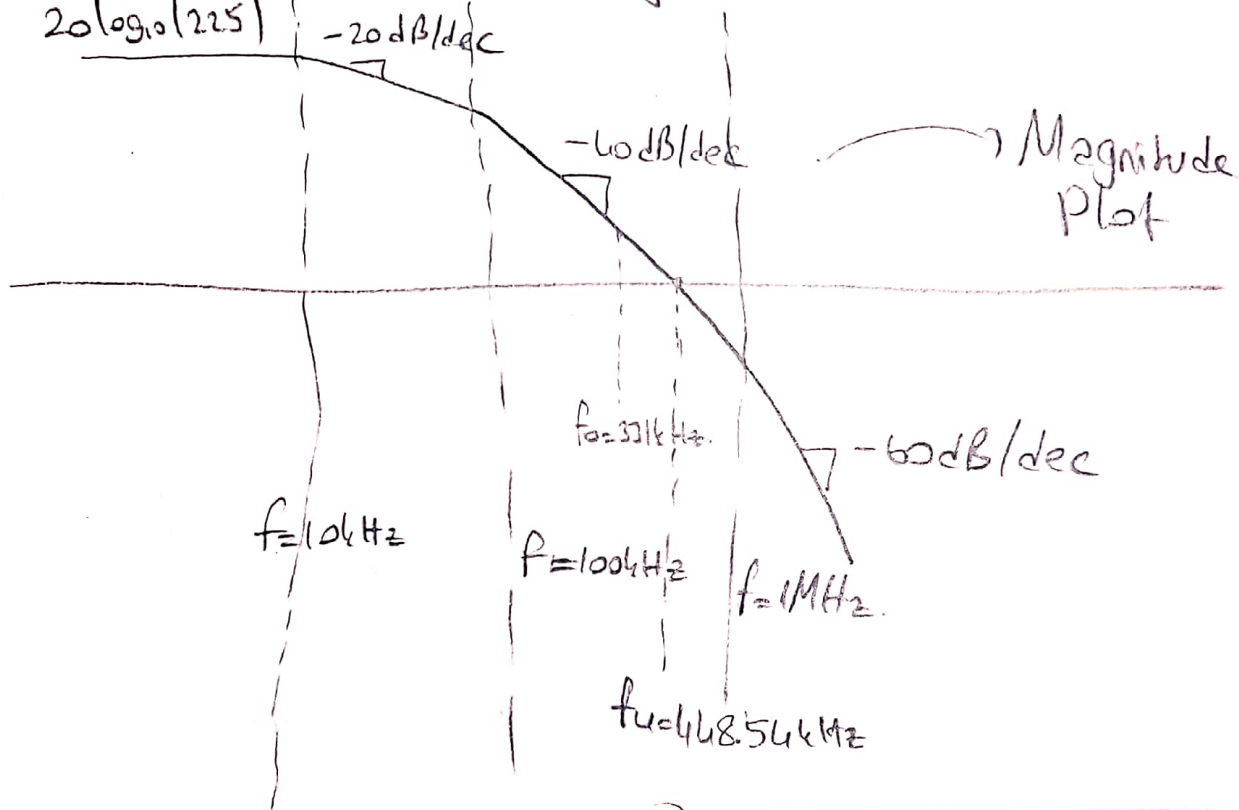


4

Q3. Find the values of R_1, R_3, C and L for the phase shift oscillator in Fig. P13.6 so that the oscillation frequency is $f_0 = 5 \text{ kHz}$.

$$h_{ie} = 1.3 \text{ k}\Omega$$

$$h_{fe} = 100$$

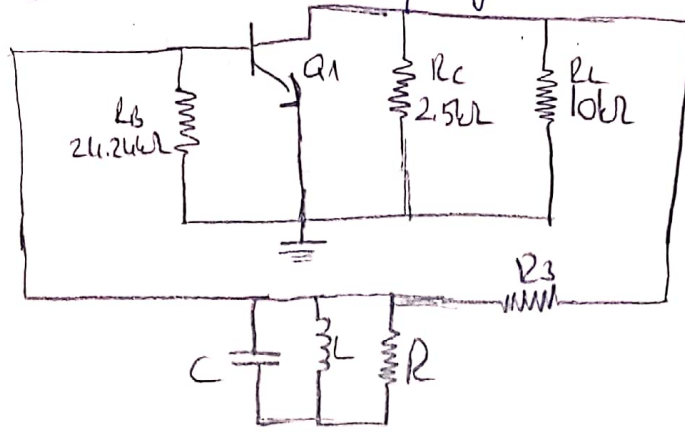


analyze the amplifier

$$r_{in,VA} = R_B \parallel r_{\pi}$$

$$r_{out,VA} = R_C \parallel R_L \parallel r_o \approx R_C \parallel R_L \quad r_o \rightarrow +\infty$$

$$r_{\pi}, \beta \text{ given} \rightarrow g_m = \frac{\beta}{r_{\pi}} = \frac{100}{1.3 \text{ k}\Omega} = 0.0769$$
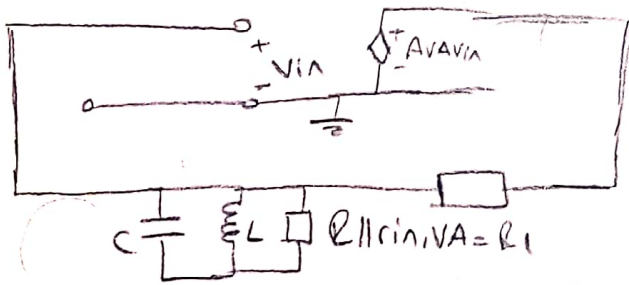
$$A_{VA} = -0.0769 (2.5 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = -153.8 = A_{VA}$$



Feedback Network

$$B(j\omega) = \frac{v_i}{v_o} = \frac{j\omega L \parallel \frac{1}{j\omega C} \parallel R_1}{j\omega L \parallel \frac{1}{j\omega C} \parallel R_1 + R_F}$$

$$\frac{j\omega L \parallel \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$B(j\omega) = \frac{j\omega L R_1}{j\omega L + (1 - \omega^2 LC) R_1} = \frac{j\omega L R_1}{j\omega L R_1 + j\omega L R_F + (1 - \omega^2 LC) R_1 R_F} \quad \text{eq. 1}$$

$$A_{VA} B(j\omega) = [-g_m (R_C \parallel R_L)] B(j\omega)$$


Phase cond. but make ω in eq. 1 to $1 - \omega^2 LC = 0$ verified.

$$\omega = \frac{1}{\sqrt{LC}}$$

5

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow A_{VA} B(j\omega) \big|_{\omega=\omega_0} = \frac{j\omega L (-g_m(R_C \parallel R_L))}{j\omega L (1 + \frac{R_F}{R_1})} < 0$$

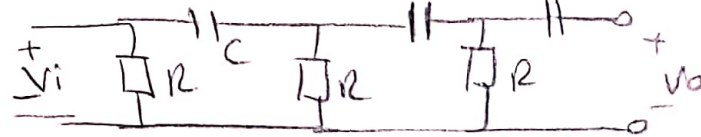$\omega = \omega_0$ için 180° phase conv.




$$B(j\omega) = \frac{V_i}{V_o} = \frac{1}{1 - j(\frac{1}{\omega RC}) - \frac{5}{\omega^2 R^2 C^2} + \frac{j}{\omega^3 R^3 C^3}}$$

$$A_{VA} B(j\omega) = [-g_m(R_C \parallel R_L)] B(j\omega)$$

$$\frac{1}{\omega^3 R^3 C^3} - \frac{5}{\omega RC} = 0 \quad 1 - 5\omega^2 R^2 C^2 = 0 \quad \omega_0 = \frac{1}{\sqrt{5} RC}$$


$$A_{VA} B(j\omega) \big|_{\omega=\omega_0} = \frac{-g_m(R_C \parallel R_L)}{1-5} = 1 \rightarrow g_m(R_C \parallel R_L) = 2g$$

Forward Imp

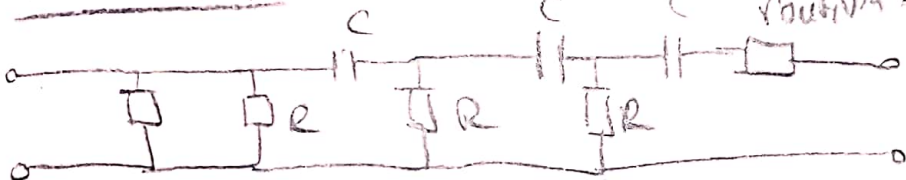


$$\left| \frac{1}{j\omega RC} \right| \geq 10 \cdot (R_C \parallel R_L) \quad \omega_0 = \frac{1}{\sqrt{5} RC} \quad r_{in,VA} = R_1 \parallel r_{\pi} \geq 10R$$

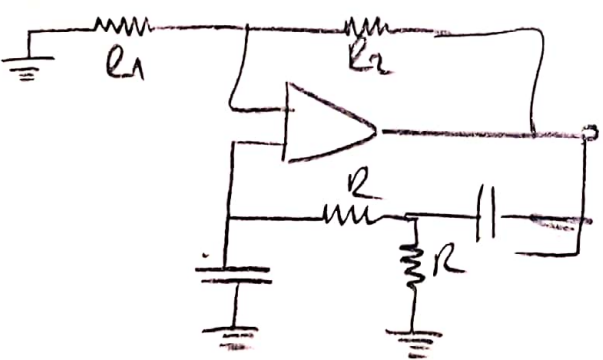Qu. for the circuit in Fig. P13.13 find $L(s)$, $L(j\omega)$ the frequency for zero loop phase, and $R_2 \parallel R_1$ for oscillation



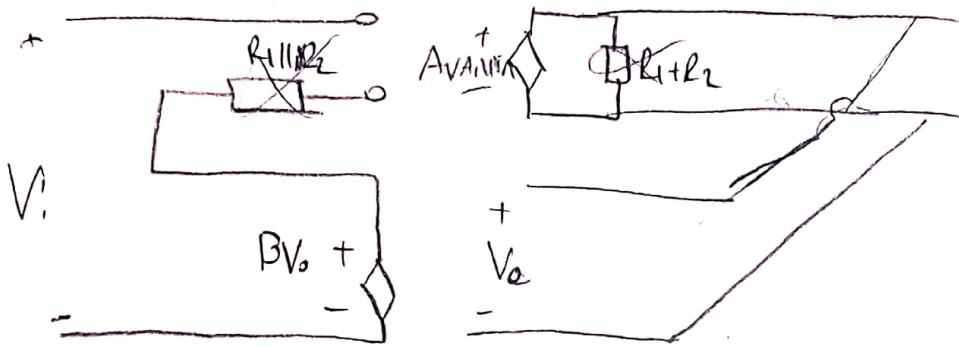
OPAMP bir voltage amp. dir. voltage-series bağlanı tipi inceleyic.



$$\frac{V_o}{V_i} = \frac{A}{1 + \frac{A R_1}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

$A \rightarrow +\infty \quad r_{in} \rightarrow +\infty \quad r_{out} \rightarrow 0$

Feedback network Analysis

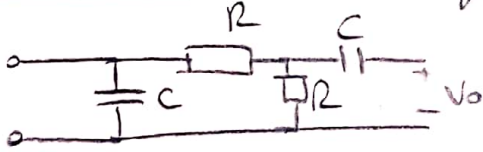

$$\frac{V_i}{V_o} = \frac{(R + \frac{1}{Cs}) \parallel R}{(R + \frac{1}{Cs}) \parallel R + \frac{1}{Cs}} \cdot \frac{1/Cs}{1/Cs + R}$$

$$\frac{V_+ - V_i}{R} = \frac{V_i}{1/Cs} = Cs V_o$$

$$V_+ = V_i + RCs V_i = (1 + RCs) V_i$$

$$V_+ + Cs V_i + Cs (V_+ - V_o) = 0 \quad V_+ (1 + RCs) + RCs V_i = RCs V_o$$

$$V_i [R^2 C^2 s^2 + 3RCs + 1] = RCs V_o$$

$$\frac{V_i}{V_o} = \frac{RCs}{R^2 C^2 s^2 + 3RCs + 1} \Rightarrow B(j\omega) = \frac{V_i(j\omega)}{V_o(j\omega)} = \frac{1}{3 + j(\omega CR - \frac{1}{\omega CR})}$$

$$A_{VA} B(j\omega) = \frac{1 + \frac{R_2}{R_1}}{3 + j(\omega CR - \frac{1}{\omega CR})}$$

$$\omega CR = \frac{1}{\omega CR} = 0$$


$$\omega_0 = \frac{1}{RC}$$

$$|A_{VA} B(j\omega_0)| = 1 \quad 1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

7

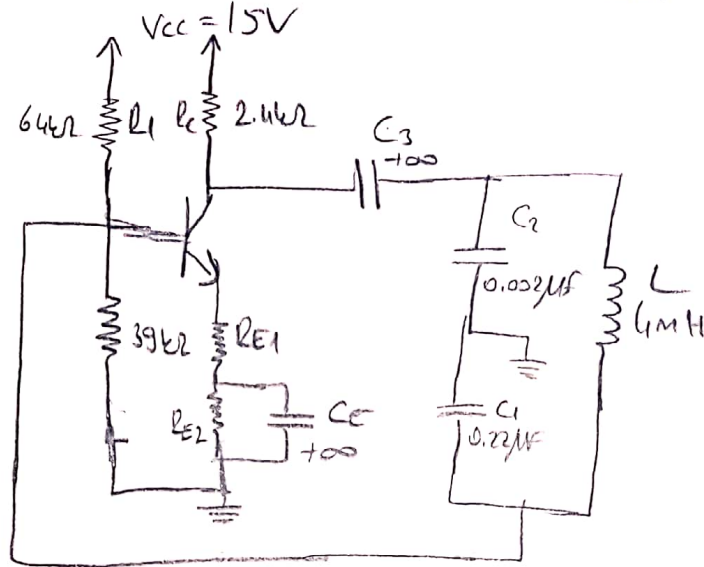Q5. A Colpitts BJT oscillator is shown in Fig. P13.17. Calculate the frequency of oscillation f_o and the value of R_{E1} required to sustain the oscillation




Model Common Emitter Amp. as Transconductance Amp.

$$r_{in,TCA} \approx R_1 \parallel R_2 \parallel [\beta r_{\pi} (1 + g_m R_{E1})]$$

$$r_{out,TCA} \approx R_c \parallel \left[(1 + g_m r_{\pi}) \cdot \frac{R_{E1} \beta r_{\pi}}{R_{E1} + r_{\pi} + R_1 \parallel R_2} \right]$$
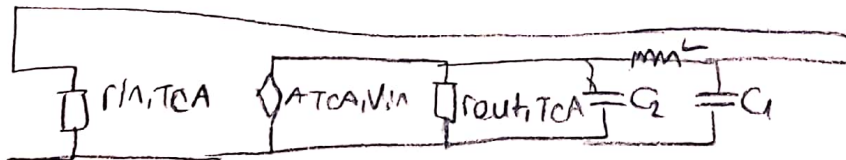
$$A_{TCA} \approx \frac{g_m}{1 + g_m R_{E1}}$$





$$\omega_o = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

$$A_{TCA}, r_{out,TCA} \geq \frac{C_1}{C_2}$$


$$\left| \frac{1}{j\omega_o C_1} \right| \ll r_{in,TCA}$$

(8)

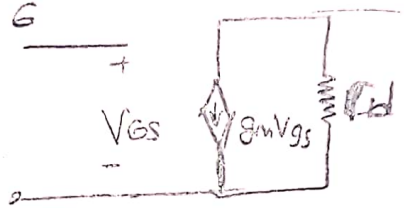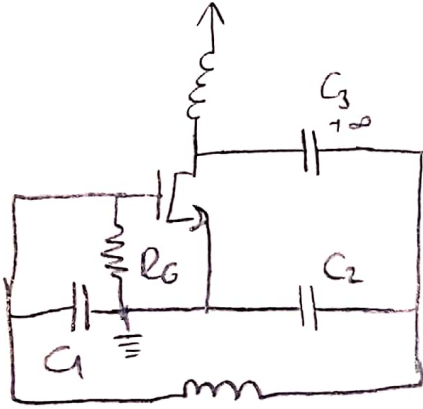Q6. Determine the frequency of oscillation for the Colpitts MOSFET oscillator in fig P.13.20 (a). The MOSFET can be replaced by its transconductance model, shown in fig P.13.20(b). The parameters are $r_d = 25k\Omega$; $g_m = 5mA/V$ $R_G = 1M\Omega$; $L = 1.5mH$, $C_1 = 10nF$, $C_2 = 10nF$. Calculate the frequency of oscillation and check to make sure the condition for oscillation is satisfied.



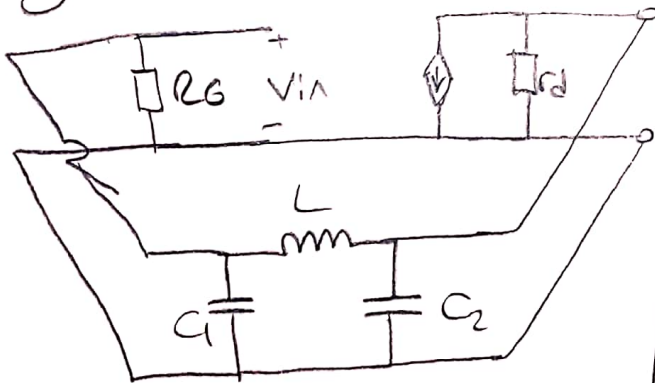RF Chocke Short cir. at DC open circuit for higher frequencies
Intrinsic gain of the MOS applies. MOS modelled as TCA



$$\omega_0 = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

$$g_m r_d \geq \frac{C_1}{C_2}$$

$$\left| \frac{1}{j\omega_0 C_1} \right| \ll R_G$$

(9)