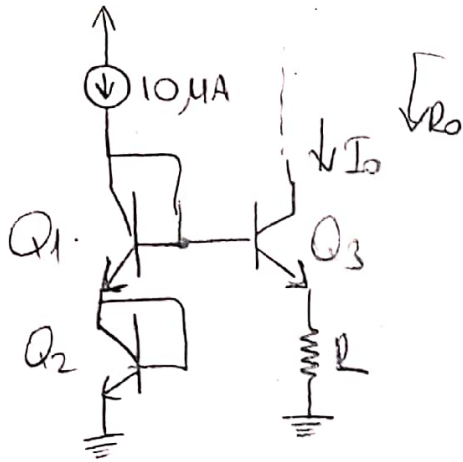


HW-14

Abdullah MEMİŞOĞLU

171024001

(a) For the circuit in Fig P6.144, Assume BJTs with high  $\beta$  and  $V_{BE} = 0.7V$  at  $1mA$ . Find the value of  $R$  that will result in  $I_0 = 10\mu A$  (b) For the design in (a), find  $R_0$  assuming  $\beta = 100$  and  $V_A = 100V$



$$I_{C1} = I_S \exp\left(\frac{V_{BE1}}{V_T}\right)$$

$$I_{C2} = I_S \exp\left(\frac{V_{BE2}}{V_T}\right)$$

$$I_{C3} = I_S \exp\left(\frac{V_{BE3}}{V_T}\right)$$

$$I_{C1} = I_{C2} = 10\mu A \quad I_{C3} = 10\mu A$$

$$I_{S1} = I_{S2} = I_{S3} \\ V_{T1} = V_{T2} = V_{T3}$$

$$V_{BE1} = V_{BE2} = V_{BE3} = V_{BE}$$

$$V_{BE} = V_T \ln \frac{I_C}{I_S} \\ \hookrightarrow 0.7V = 26mV \cdot \ln\left(\frac{1mA}{I_S}\right)$$

$$\frac{0.7}{26 \times 10^{-3}} = \ln\left(\frac{10^{-3}}{I_S}\right) \rightarrow I_S = 2.02 \times 10^{-15} A$$

$$(V_{BE}, I_C) = (0.7V, 1mA)$$


$$V_{BE2} = 26 \times 10^{-3} \cdot \ln\left(\frac{10\mu A}{2.02 \times 10^{-15}}\right) = 0.58V$$

$$R = \frac{V_{BE2}}{I_0} = \frac{0.58V}{10\mu A} = 58.039 k\Omega$$

$$V_{BE1} = V_{BE3} \\ V_{BE2} + V_{BE1} - V_{BE3} - R I_0 = 0$$

1

small sig. eq. cir.

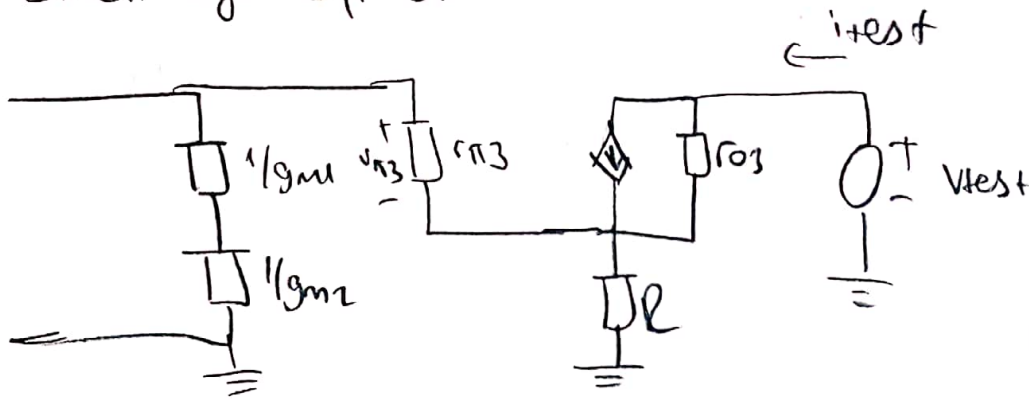

$$r_{\pi 3} \gg \frac{1}{g_{m1}} + \frac{1}{g_{m2}}$$

$$R_o \approx \frac{v_{test}}{i_{test}} = (1 + g_{m3} r_{o3})(R \parallel r_{\pi 3}) + r_{o3}$$

$$r_{o3} = \frac{V_A}{I_{C3}} = \frac{100V}{10\mu A} = 10 M\Omega$$

$$g_{m3} = \frac{I_{C3}}{V_T} = \frac{10\mu A}{25mV} = \frac{10 \times 10^{-6}}{25} = 4 \times 10^{-4} S$$

$$r_{\pi 3} = \frac{\beta}{g_{m3}} = \frac{100}{4 \times 10^{-4}} = \frac{100 \times 10^4}{4} = 25 \times 10^4 \Omega$$


$$R_o = (1 + 4 \times 10^{-4} \cdot 10 \times 10^6) (58.039 \Omega \parallel 25 \times 10^4 \Omega) + 10 \times 10^6 \Omega$$

$$R_o = (4001) \cdot (47.106 \Omega) + 10^7 \Omega$$

$$R_o = 10.188 M\Omega$$

(2)

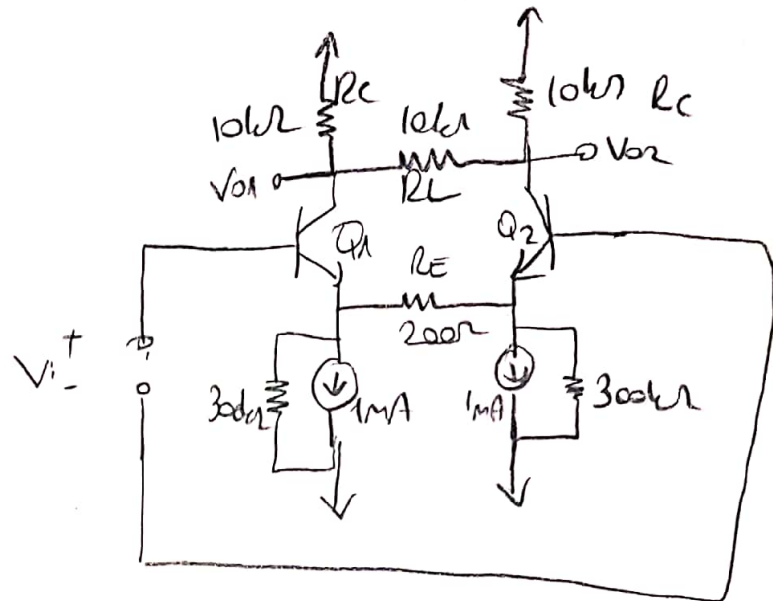Q2. For the differential amplifier shown in Fig. P7.41, identify and sketch the differential half circuit and the common mode half circuit. Find the differential gain, the differential input resistance, the common mode input resistance, for the transistors  $\beta = 100$  and  $V_A = 100V$



### DC analysis

when  $v_i = 0 \rightarrow I_{EL} = I_{EE} = 0 \quad I_{C1} = I_{C2} \approx 1mA$


$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 40mS$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{40mS} = 2.5k\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100V}{1mA} = 100k\Omega$$
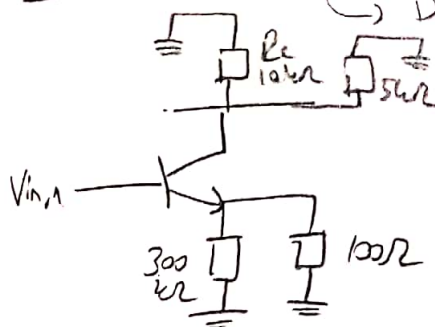
### S.S. analysis

Diff. mode - half. circ  $\Rightarrow$  virtual gnd  $R_L$  &  $R_E$




Common Emul. config.

$$A_d = \frac{V_{o1}}{V_{in1}} = \left[ - \frac{g_m}{1 + g_m(R_{CS} \parallel \frac{R_E}{2})} \right] \left[ R_C \parallel \frac{R_L}{2} \parallel \left[ 1 + g_m \left( R_{CS} \parallel \frac{R_E}{2} \right) r_o \right] \right]$$

$$R_{i,d} \approx r_{\pi1} \left[ 1 + g_m(R_{CS} \parallel \frac{R_E}{2}) \right]$$

(3)

## Common Mode Half Cir

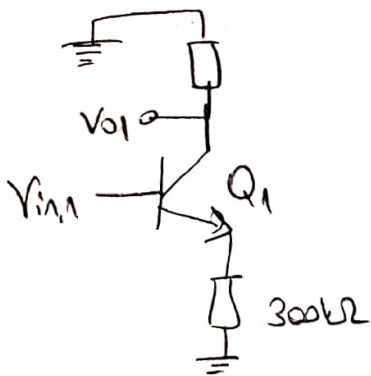

$$A_c = \frac{v_{o1}}{v_{in,1}} \approx \left[ -\frac{g_m}{1+g_m R_{es}} \right] \cdot \left[ R_c \parallel [1+g_m R_{es}] r_o \right]$$

$$R_{i,c} = r_{\pi} [1+g_m R_{es}]$$


$$CMRR = \left| \frac{A_d}{A_c} \right|$$

$$V_{b1} = V_c + \frac{V_d}{2} \rightarrow V_c = \frac{V_{B1} + V_{B2}}{2} = 0.1 \sin(2\pi 60t) \text{ V}$$


$$V_{b2} = V_c - \frac{V_d}{2} \rightarrow V_d = \underline{V_{B1} - V_{B2}} = 0.01 \sin(2\pi 1000t) \text{ V}$$

superposition

diff mode

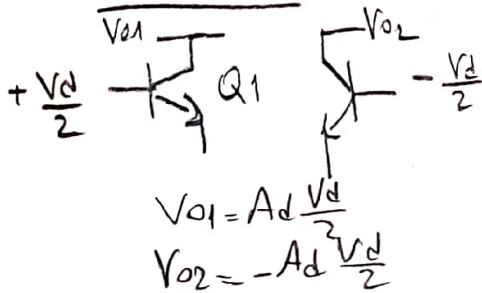

common mode only

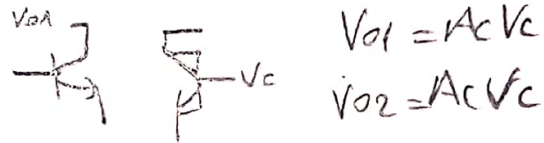


superposition  $V_{o1} = A_d \frac{V_d}{2} + A_c V_c$ ,  $V_{o2} = -A_d \frac{V_d}{2} + A_c V_c$


(4)



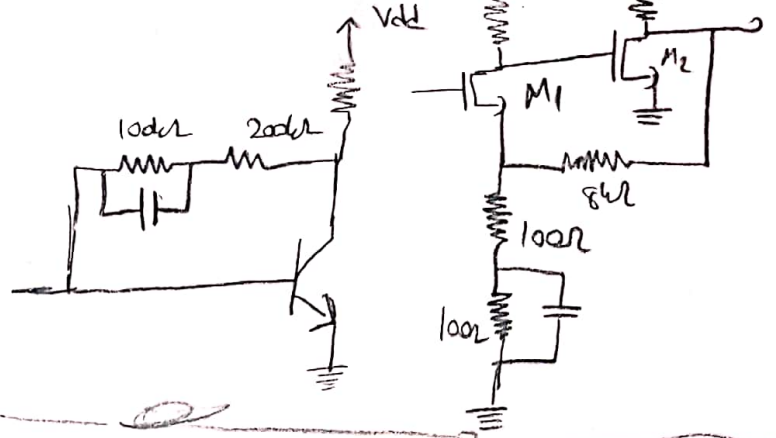
Q3. For each circuit of Fig. Pg. 29, identify the type of feedback and find the numerical value of  $\beta$  using the appropriate two port parameters of the feedback circuit. State whether the feedback is dc or ac. If both, find the two-port parameter values for both.



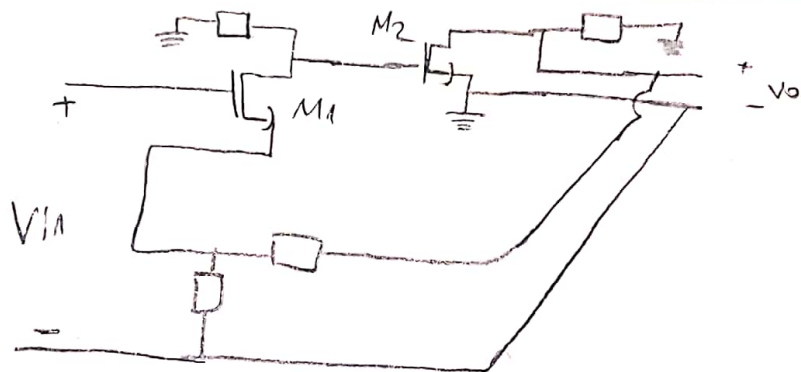Voltage-series feedback  
voltage amplifier



Two Port Parameters

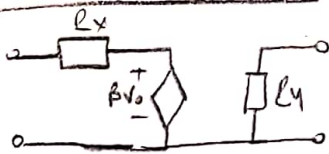



AC feedback

$$\beta = \frac{100}{8k} = \frac{1}{80}$$

$$R_x = 100k \parallel 8k = 8.7k$$

$$R_y = 8.2k$$

Voltage-Shunt  
Transres. amp.

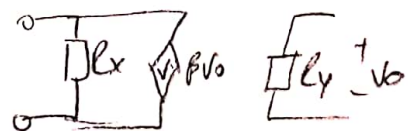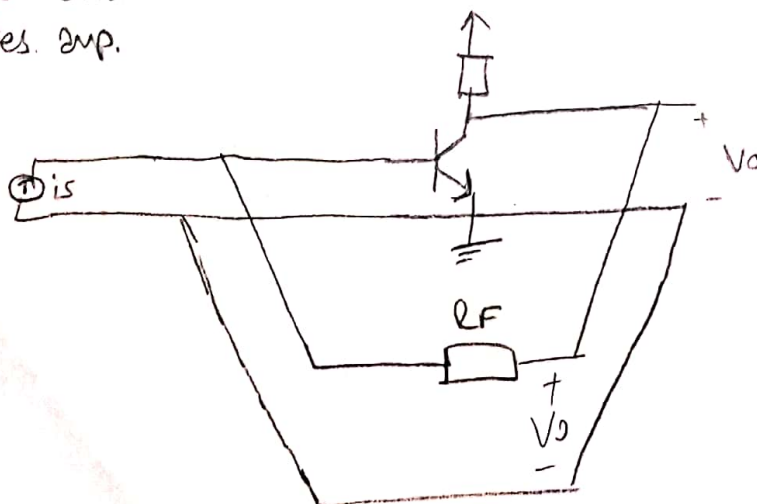


(5)

(a)

	ac feed.	dc feed
$\beta = -\frac{1}{R_F}$	$-\frac{1}{200k\Omega}$	$-\frac{1}{300k\Omega}$
$R_x = R_F$	$200k\Omega$	$300k\Omega$
$R_y = R_F$	$200k\Omega$	$300k\Omega$

Q4. The CMOS amplifier in Fig 14.20 is operated at a biasing current of  $I_Q = 50\mu A$ . The parameters of the MOSFET's are  $k_x = 10\mu A/V^2$ ,  $|V_{th}(NMOS)| = V_{th}(PMOS) = 60mV$ ,  $V_t = 1V$ ,  $W/L = 80\mu m/10\mu m$  except for  $Q_7$ , for which  $W/L = 160\mu m/10\mu m$ . Assume  $V_{DD} = V_{SS} = 5V$

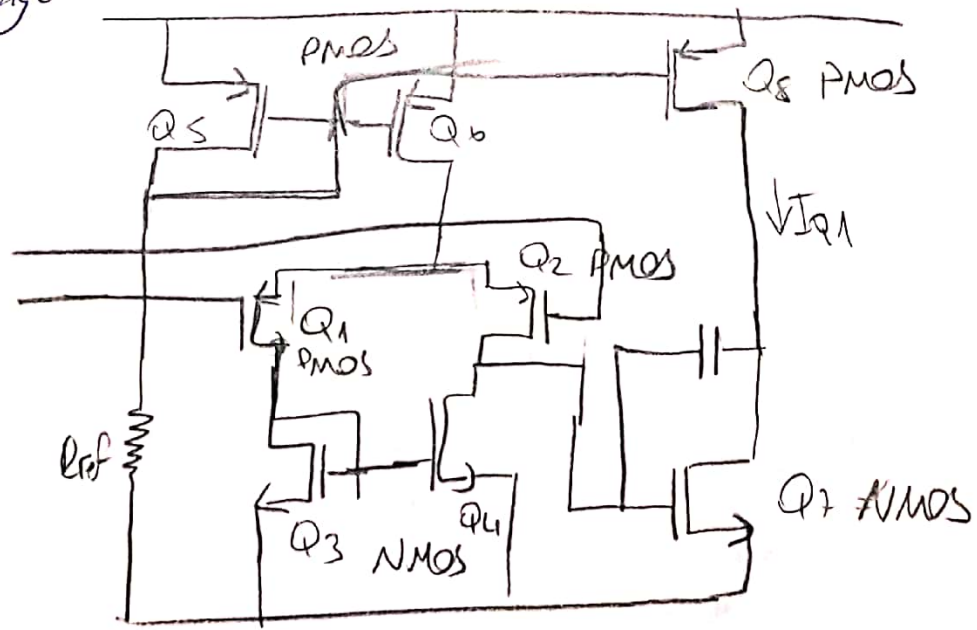- (a) Find  $V_{GS}$ ,  $g_m$  and  $r_o$  for all MOSFETs.
- (b) Find the low-frequency voltage gain of the amplifier  $A_{vo}$
- (c) Find the value of the external resistance  $R_{ref}$ .
- (d) Find the value of Compensation capacitance  $C_x$  that gives a unity-gain bandwidth of 1MHz and the corresponding slewrate.
- (e) Find the value of resistance  $R_x$  to be connected in series with  $C_x$  in order to move the zero frequency to infinity.
- (f) Find the common-mode input voltage range
- (g) Find the voltage range



(b)

## ② Systematic DC offset cancellation

$$2 \frac{\left(\frac{W}{L}\right)_8}{\left(\frac{W}{L}\right)_6} = \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_4} \quad I_{D5} = I_{D6} = I_Q = I_{ref} = 50 \mu A$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I_Q}{2} = 25 \mu A$$

$$I_{D8} = I_{D7} = I_Q = 50 \mu A$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_t|)^2$$

$$K_x = \frac{1}{2} \mu_n C_{ox} = \frac{1}{2} \mu_p C_{ox} = 10 \mu A/V^2$$

$$I_{D1} = \dots = 25 \mu A = \frac{1}{2} \cdot \underbrace{\mu_n C_{ox}}_{10 \mu A/V^2} \cdot \underbrace{\frac{W}{L}}_8 (V_{GS} - V_t)^2$$

$$\frac{W}{L} = \frac{80 \mu m}{10 \mu m} \quad \frac{Q_7}{160 \mu m / 10 \mu m}$$

$$Q_1 = Q_2 = Q_5 = Q_6 = Q_8 = \text{PMOS}$$

$$Q_3 = Q_4 = Q_7 = \text{NMOS}$$

$$25 \mu A = \frac{1}{2} \underbrace{\mu_n C_{ox}}_{10 \mu A/V^2} \cdot \underbrace{\frac{W}{L}}_8 (V_{GS} - V_t)^2$$

$$\boxed{V_{GS} - V_t = 0.790}$$

$$\hookrightarrow Q_1 = Q_3 = Q_4 = Q_2$$

$$50 \mu A = 10 \mu A/V^2 \cdot 8 \cdot (V_{GS} - V_t)^2$$

$$\hookrightarrow V_{GS} - V_t = 0.790 \rightarrow Q_5, Q_6$$

$$50 \mu A = 10 \mu A/V^2 \cdot 16 (V_{GS} - V_t)^2 = 0.559 \rightarrow Q_7$$

$$\hookrightarrow V_{GS} - V_t$$

$$\boxed{r_o = \frac{60V}{250 \mu A} = 1.2 \text{ M}\Omega}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t}$$

$$Q_1 \rightarrow \frac{1}{2} \underbrace{\mu_p C_{ox}}_{10 \mu A/V} \cdot \underbrace{\frac{W}{L}}_8 (V_{SG} - |V_t|)^2 = 25 \mu A$$

$$Q_1 \rightarrow (V_{SG} - |V_t|)^2 = \frac{25}{80}$$

$$Q_2 \rightarrow (V_{SG} - |V_t|)^2 = \frac{25}{80}$$

$$Q_3 \rightarrow (V_{GS} - V_t)^2 = \frac{25}{80}$$

$$Q_4 \rightarrow (V_{GS} - V_t)^2 = \frac{25}{80}$$

$$Q_5 \rightarrow (V_{SG} - |V_t|)^2 = \frac{50}{80}$$

$$Q_6 \rightarrow (V_{SG} - |V_t|)^2 = \frac{50}{80}$$

⑦

$$Q_7 = 10 \mu A/V \cdot 16 \cdot (V_{GS} - V_t)^2 = 50 \mu A$$

$$\hookrightarrow (V_{GS} - V_t)^2 = \frac{25}{80}$$



$$r_{o1} = \frac{|V_{M1}|}{I_D} = \frac{60}{25 \mu A} = 2.4 \text{ M}\Omega$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = 2.4 \text{ M}\Omega$$

$$r_{o5} = r_{o6} = r_{o7} = r_{o8} = \frac{r_{o1}}{2} = 1.2 \text{ M}\Omega$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = 25 \mu A$$

$$I_{D5} = I_{D6} = I_{D7} = I_{D8} = 50 \mu A$$

$$(V_{GS} - V_t)_{1,2,3,4,7} = \frac{25}{80}$$

$$(V_{GS} - V_t)_{5,6,8} = \frac{50}{80}$$

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = \frac{2I_D}{(V_{GS} - V_t)} = \frac{50 \mu}{25/80} = 0.16 \text{ mS}$$

$$g_{m7} = \frac{100 \mu}{25/80} = 0.32 \text{ mS}$$

$$g_{m5} = g_{m6} = g_{m8} = \frac{40 \mu}{50/80} = 0.16 \text{ mS}$$

(b)

Gain of diff. stage  $\rightarrow \frac{V_{g7}}{V_{in+} - V_{in-}} \approx -g_{m1}(r_{o2} \parallel r_{o4}) = -0.16 \text{ mS} (1.2 \text{ M}\Omega)$

gain of the common source  $\rightarrow \frac{V_{d7}}{V_{g7}} = -g_{m7}(r_{o8} \parallel r_{o2}) = -0.32 \text{ mS} \cdot 0.6 \text{ M}\Omega$

$$A_{vo} = \frac{V_{d7}}{V_{in+} - V_{in-}} = \frac{V_{g7}}{V_{in+} - V_{in-}} \cdot \frac{V_{d7}}{V_{g7}} = +36864$$

$$V_{DD} - V_{GS,5} - I_{ref} \cdot R_{ref} = -V_{SS}$$

$$10 - 0.764 = 50 \mu A \cdot R_{ref}$$

$$R_{ref} = 184.70 \text{ k}\Omega$$

$$V_{DD} = V_{SS} = 5 \text{ V}$$

$$(V_{GS,5} - V_t)^2 = \frac{50}{80} \rightarrow V_{GS,5} = 0.764 \text{ V}$$


$$V_{GS,5} = 0.764 \text{ V}$$

$$I_{ref} = 50 \mu A$$

(c)

(8)



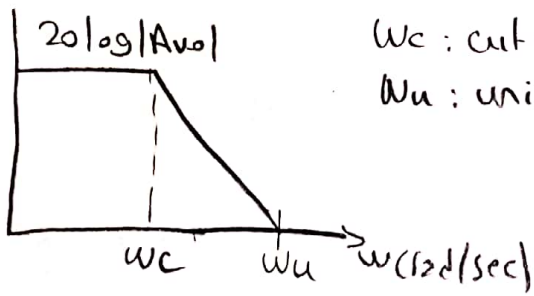


$w_c$ : cut off freq  
 $w_u$ : unity gain freq.

$$A_{vo} \cdot w_c = w_u \rightarrow w_c = \frac{w_u}{A_{vo}}$$

(d)

Miller theorem to transform  $C_x$

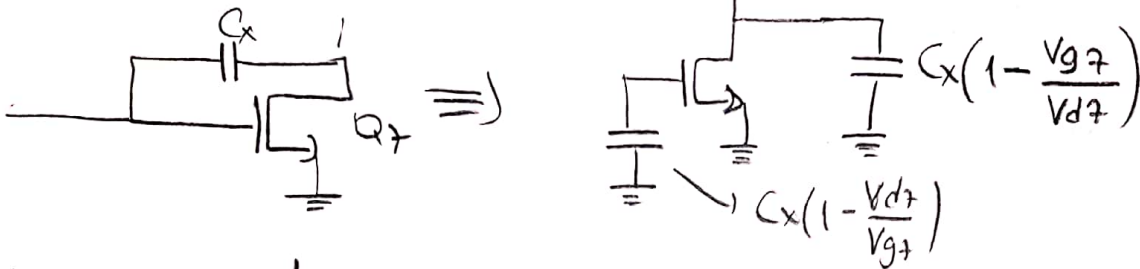

$$w_c = \frac{1}{C_x \left(1 - \frac{V_{dt}}{V_{gt}}\right) \cdot (r_{o2} \parallel r_{o4})}$$

Thevenin eq. res.

$$w_u = 1 \text{ MHz}$$

$$w_u = A_{vo} \cdot w_c$$

$$1 \times 10^6 = 36864 \cdot \frac{1}{C_x (1 + g_{m2}(r_{o2} \parallel r_{o4})) (r_{o2} \parallel r_{o4})}$$

$\downarrow \quad \quad \downarrow \quad \quad \downarrow$   
 $0.32 \text{ M} \quad 0.6 \text{ M} \quad 1.2 \text{ M}$

$$27.12 = \frac{1}{C_x \cdot 231.6 \times 10^6} \rightarrow C_x = \frac{1}{27.12 \times 231.6 \times 10^6} = 1.592 \times 10^{-10} = 15.92 \text{ nF}$$

$$\text{Slew rate} = \frac{I_Q}{C_x} = \frac{50 \text{ MA}}{15.92 \text{ nF}} = 3140.70$$

$$C_x = 15.92 \text{ nF}$$

(g)

Fig 8

$$V_{CM, \max} = V_{DD} - [V_{SG6} - |V_t|] - V_{S61} \rightarrow V_{SD6} \geq V_{S66} - |V_t|$$

$$V_{CM, \max} = 5 - (0.765 - 0.025) - 0.533$$

$$V_{S61} = 0.533 \text{ V}$$

$$V_{CM, \max} = 3.727 \text{ V}$$

$$V_{S66} = 0.765 \text{ V}$$

$$V_{SD,1} \geq V_{S6,1} - |V_t|$$

$$|V_t| \geq V_{S6,1} - V_{SD,1} = V_{DS1}$$

$$V_{DS,1} \geq -|V_t| \rightarrow (V_{G1} - V_{D1}) \geq -|V_t|$$

$$V_{GS,3} = 0.765 \text{ V}$$

$$V_{G1} \geq -|V_t| + (-V_{SS}) + V_{GS,3}$$

$$V_{G1} \geq -0.025 + 5 + 0.765$$

$$V_{CM, \min} = -4.26 \text{ V}$$

9

$$V_{SD,8} \geq V_{S6,8} - |V_t|$$

→ Q8 saturasyonunda  
yolunda  
Q2 saturasyonunda

$$V_{DS,7} \geq V_{GS,7} - |V_t|$$

$$V_{GS,7} = 0.533 \text{ V}$$

$$V_{SG,8} = 0.765 \text{ V}$$

$$V_{D, \max} = V_{DD} - (V_{SG,8} - |V_t|)$$

$$V_{D, \min} = -V_{SS} + (V_{GS,7} - |V_t|)$$

$$V_{D, \max} = 5 - (0.765 - 0.025)$$


$$V_{D, \max} = 4.26 \text{ V}$$

$$V_{D, \min} = -5 + (0.533 \text{ V} - 0.025)$$

$$V_{D, \min} = -4.492 \text{ V}$$


10

(e)

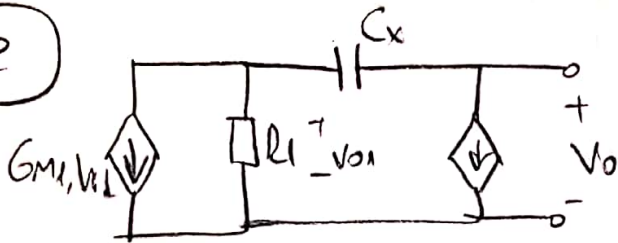

$$GM_2 V_{o1} = (V_{o1} - V_o) \omega C_x \quad \omega z = \text{zero} \quad V_o = 0$$
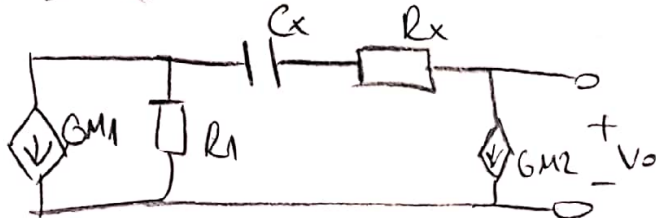
$$GM_2 V_{o1} = V_{o1} \omega z C_x \quad \omega z = \frac{GM_2}{C_x}$$




$$GM_2 V_{o1} = \frac{V_{o1} - V_o}{R_x + \frac{1}{j\omega C_x}}$$

$$GM_2 V_{o1} = \frac{V_{o1} j\omega z C_x}{1 + j\omega z R_x C_x}$$

$$GM_2 + j\omega z R_x C_x GM_2 = j\omega z C_x \Rightarrow GM_2 + j\omega z C_x (R_x GM_2 - 1) = 0$$

$$GM_2 \left[ 1 + \frac{j\omega z}{C_x (R_x - \frac{1}{GM_2})} \right] \rightarrow \text{zero freq.} \quad \frac{1}{C_x (R_x - \frac{1}{GM_2})}$$
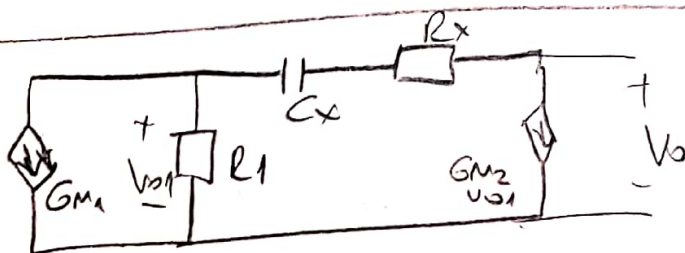
$$R_x = \frac{1}{GM_2} \text{ is zero freq.} \rightarrow +\infty$$



$$GM_1 V_d + \frac{V_{o1}}{R_1} + \frac{V_{o1} - V_o}{z_x} = 0$$

$$GM_1 V_d + \frac{V_{o1}}{R_1 \parallel \frac{1}{GM_2}} = 0 \quad GM_2 V_{o1}$$

$$V_o = -GM_2 V_{o1} [z_x] + V_{o1}$$

$$= V_{o1} [1 - GM_2 z_x]$$

$$\frac{V_o}{V_d} = \frac{V_{o1}}{V_d} [1 - GM_2 z_x]$$

$$\frac{V_o}{V_d} = -\frac{GM_1 R_1}{1 + GM_2 R_1} [1 - GM_2 z_x]$$

(11)





$$\frac{V_o}{V_d} = - \frac{G_{M1} R_1}{1 + G_{M2} R_1} \left[ 1 - G_{M2} \left[ R_x + \frac{1}{j\omega C_x} \right] \right]$$

$$= \frac{G_{M1} R_1}{1 + G_{M2} R_1} \left[ (G_{M2} R_x - 1) + \frac{G_{M2}}{j\omega C_x} \right]$$

$$= \frac{G_{M1} R_1}{1 + G_{M2} R_1} \left[ \frac{1 + j\omega C_x \left( R_x - \frac{1}{G_{M2}} \right)}{j\omega C_x} \right] G_{M2}$$
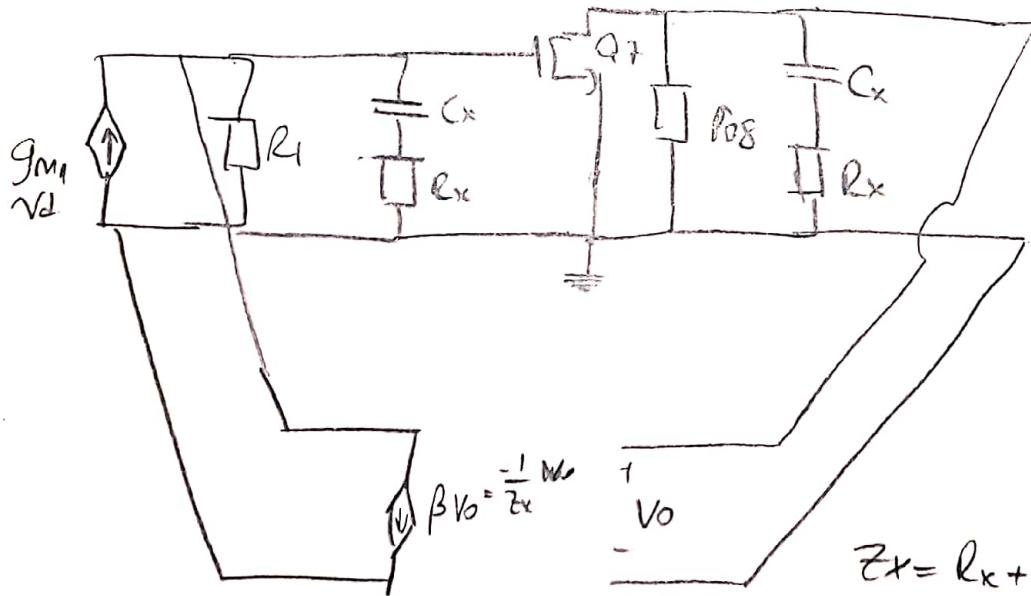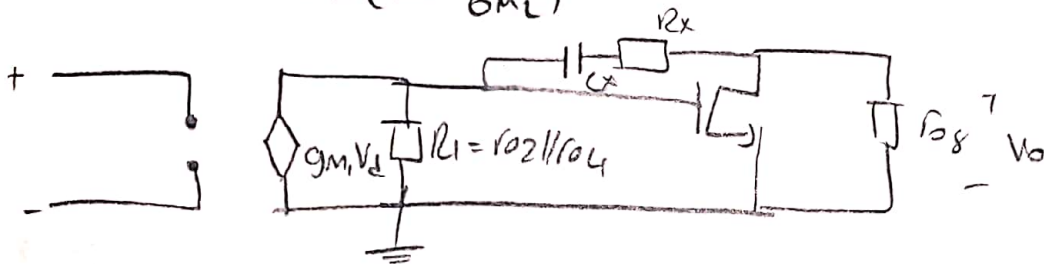
$$\omega_z = \frac{1}{C_x \left( R_x - \frac{1}{G_{M2}} \right)} \quad R_x = \frac{1}{G_{M2}} \text{ ise zero freq} \rightarrow +\infty$$



$$Z_x = R_x + \frac{1}{j\omega C_x}$$

$$\beta = 0 \quad A_{TRA} = ?$$

$$A_{TRA} = \frac{V_o}{i_s} = [R_1 || Z_x] [-g_{m7}] [R_2 || Z_x]$$

$$A_f = \frac{A_{TRA}}{1 + \beta A_{TRA}} = \frac{V_o}{i_s} = \frac{-g_{m7} [R_1 || Z_x] [R_2 || Z_x]}{1 + g_{m7} [R_1 || Z_x] [R_2 || Z_x] \frac{1}{Z_x}}$$

12

$$I_S = -g_{m1} V_d$$

$$\frac{V_o}{I_S} = \frac{V_o}{-g_{m1} V_d} \quad \frac{V_o}{V_d} = \frac{g_{m1} g_{m7} \cdot [R_1 \parallel Z_x] [R_2 \parallel Z_x]}{1 + g_{m7} [R_1 \parallel Z_x] [R_2 \parallel Z_x] \frac{1}{Z_x}}$$

$$\frac{V_o}{V_d} = \frac{g_{m1} g_{m7} \frac{R_1 Z_x}{R_1 + Z_x} \cdot \frac{R_2 Z_x}{R_2 + Z_x}}{1 + g_{m7} \frac{R_1 Z_x}{R_1 + Z_x} \cdot \frac{R_2 Z_x}{R_2 + Z_x} \cdot \frac{1}{Z_x}}$$

$$= \frac{g_{m1} g_{m7} R_1 R_2 Z_x^2}{(R_1 + Z_x)(R_2 + Z_x) + g_{m7} R_1 R_2 Z_x}$$

$$= \frac{g_{m1} g_{m7} R_1 R_2 Z_x^2}{R_1 R_2 + Z_x(R_1 + R_2 + g_{m7} R_1 R_2) + Z_x^2}$$

$$= \frac{g_{m1} g_{m7} R_1 R_2 Z_x^2}{R_1 R_2 + Z_x g_{m7} R_1 R_2 + Z_x^2} \rightarrow \text{root } \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \quad \begin{matrix} g_{m7} R_1 R_2 - 2r_{sm} \\ \uparrow \end{matrix}$$

$$\frac{V_o}{V_d} = \frac{g_{m1} g_{m7} R_1 R_2 Z_x^2}{(Z_x + r_{sm}) \cdot (Z_x + g_{m7} R_1 R_2)}$$

$$Z_x = R_x + \frac{1}{j\omega C_x}$$

$$\frac{Z_x^2}{(Z_x + r_{sm}) \cdot (Z_x + g_{m7} R_1 R_2)} = \frac{(1 + j\omega C_x R_x)^2}{[1 + j\omega C_x (R_x + r_{sm})] \cdot [1 + j\omega C_x (R_x + g_{m7} R_1 R_2)]}$$

$$-g_{m7} R_1 R_2 \pm \sqrt{(g_{m7} R_1 R_2)^2 - 4r_{sm} R_1 R_2}$$

$$(g_{m7} R_1 R_2)^2 \gg 4r_{sm} R_1 R_2$$

$$r_1 = -g_{m7} R_1 R_2 + r_{sm}$$

$$R_2 = -r_{sm}$$

(13)

$$\frac{(1 + j\omega C_x R_x)^2}{1 + j\omega C_x (R_x + r_{sm})} \approx \frac{(1 + j\omega 2C_x R_x)(1 - j\omega C_x (R_x + r_{sm}))}{1 + \omega^2 [C_x (R_x + r_{sm})]^2}$$

$$\approx 1 + j\omega C_x (R_x - r_{sm})$$

$$\frac{V_o}{V_d} = \underbrace{g_{m1} g_{m2} \cdot R_1 \cdot R_2}_A \cdot \frac{1 + j\omega C_x (R_x - r_{sm})}{1 + j\omega C_x (R_x + g_{m2} R_1 R_2)}$$

$$\omega_z = \frac{1}{C_x (R_x - r_{sm})}$$

$$\omega_p = \frac{1}{C_x (R_x + g_{m2} R_1 R_2)}$$



$$\omega_p = \frac{1}{C_x (1 + g_{m2} R_1) \cdot R_1} \quad \text{wherein eq. ref.}$$

$\downarrow$   
 $r_{o2} \parallel r_{o1}$   
 $\underbrace{\hspace{1cm}}_{\text{Miller}}$


$$\omega_z \rightarrow +\infty \quad R_x \approx r_{sm} \text{ olur.}$$



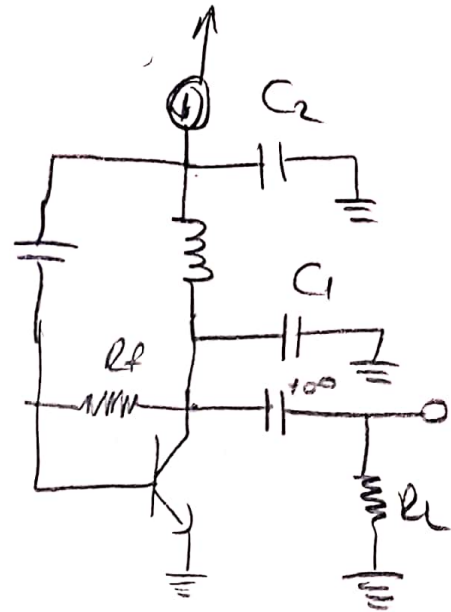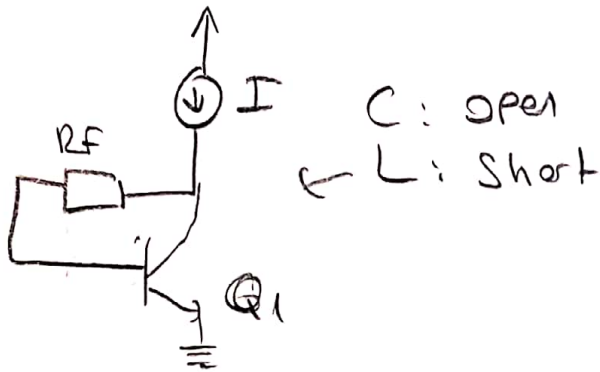Q5. Figure P.13.21 shows four oscillator circuits of the Colpitts type, complete with bias detail. For each circuit, derive an equation governing circuit operation and find the frequency of oscillation and the gain condition that ensures that oscillation starts.




SS equivalent

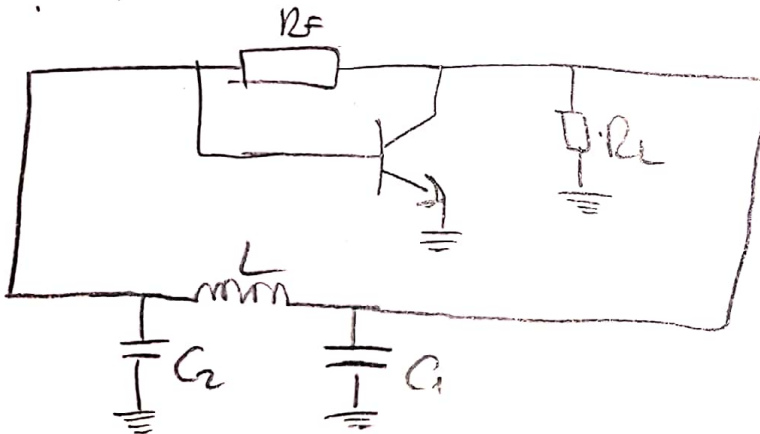

$$R_F \gg \omega_0 L$$

$$R_F / j\omega_0 L \approx j\omega_0 L$$

$R_F$  - open circuit demand

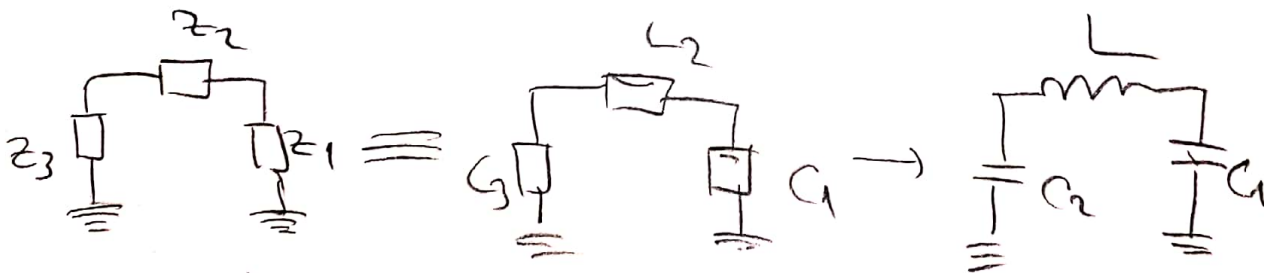

$$\omega_0 = \frac{1}{\sqrt{L + \frac{C_1 C_2}{C_1 + C_2}}}$$

$$g_m R_L \geq \frac{C_2}{C_1}$$

15