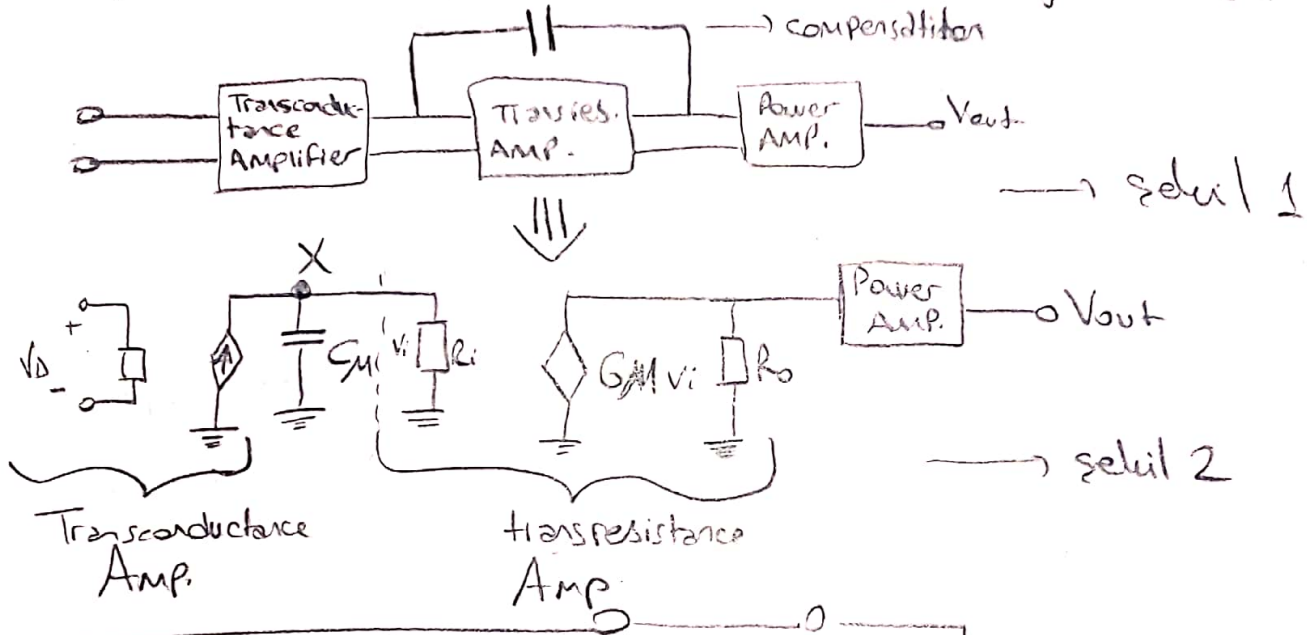


Q1. Derive an expression for the slew rate of an

OPAMP, considering that an Opamp consists of a differential amplifier stage followed by a gain stage. What is the relation between the high-frequency cut-off and the slew rate? Is there a trade-off between the slew rate and the phase/gain margins of a compensated and stable OPAMP? Could you use a compensated Opamp as a comparator, whose responses are expected to be almost instantaneous to step inputs?

Opamp elemanı, Amplifier'ların kaskat bağlanmalarıyla oluşan yapıdır.



Voltage gain of the transres. amp. stage

$$-G_m R_o \rightarrow \text{Miller effect } C_m = C_c [1 - (-G_m R_o)] = C_c [1 + G_m R_o] \quad \text{eq.1}$$

Open Circuit Time Constant Method. ( $W_H$  of the OPAMP)

$$W_H \approx \frac{1}{R_i C_m} \rightarrow C_m \text{ eq.1'de hesaplandığında } W_H \text{ bulunur}$$

şekil 2'de  $X$  node'üne KCL uygulanırsa;

$$C_m \frac{dv_i}{dt} + \frac{v_i}{R_i} - I_o = 0 \quad \frac{v_i}{R_i} \ll I_o \text{ old.}$$

$$C_m \frac{dv_i}{dt} \approx I_o \quad \text{eq.2}$$

$$\text{Slew Rate} = \frac{dv_o}{dt} \approx \frac{dv_x}{dt}$$

$$v_o \approx v_x$$

$$\text{Slew Rate} = \left| \frac{dv_x}{dV_i} \right| \cdot \frac{dV_i}{dt} = \frac{dv_x}{dt}$$

$\underbrace{\quad}_{Gm_{Ro}} \quad \underbrace{\quad}_{\frac{I_o}{G_m}}$

$$\text{Slew Rate} = \frac{Gm_{Ro} \cdot I_o}{C_c(1+Gm_{Ro})} \quad \leftarrow \text{from eq. 1}$$

$$\text{Slew Rate} = \frac{I_o \cdot Gm_{Ro}}{C_c \cdot (Gm_{Ro})} \quad \underbrace{Gm_{Ro} \gg 1}_{\Rightarrow} \quad \boxed{\frac{I_o}{C_c} = \text{Slew Rate}}$$

$$W_H = \frac{1}{R_i G_m} = \frac{1}{R_i C_c (1+Gm_{Ro})} \rightarrow \boxed{\frac{1}{C_c} = W_H \cdot R_i \cdot (1+Gm_{Ro})} \rightarrow \frac{W_H Gm_{Ro} R_i}{\text{eq. 4}}$$

$$\text{Slew Rate} = \frac{I_o}{C_c} = I_o \cdot \frac{1}{C_c} = \boxed{I_o \cdot W_H \cdot Gm_{Ro} \cdot R_i}$$



$\leftarrow \text{from eq. 4}$

Eğer  $C_c$  (compensation capacitance) değeri artarsa, faz ve kazanç marginleri opampın daha stabil çalıştığını gösterir.


1 Slew Rate'in ideal değeri sonsuzdur.  $\frac{I_o}{C_c} \approx \infty$  ise  $C_c \rightarrow 0$  ideal değerdir. Slew Rate'i ideal duruma getirmek istediğimizde Compensation efektini kaybetmiyoruz. Bu ilişkiye trade-off ilişkisi denir. Slew rate'in ideallığı ya da opampın stabilitesi arasında seçim yapmalıyız. Hangisi tasarıma daha uygun ise  $C_c$  değeri ona uygun seçilmelidir.


(2)



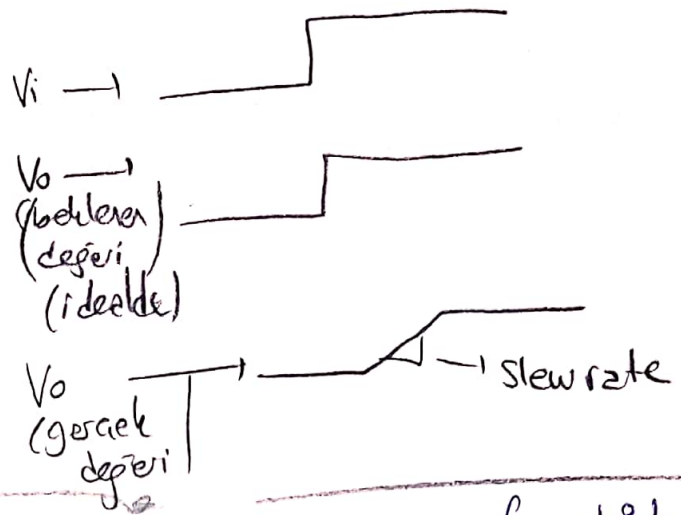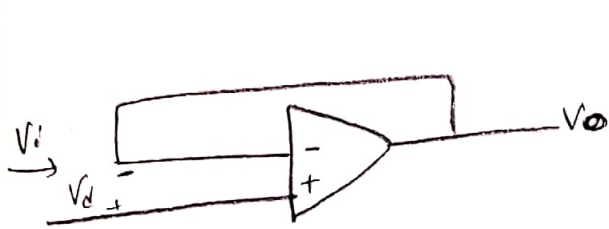

Q2. The CMOS opamp of Fig 9.1 is fabricated in a process for which  $V'_{an} = 25 \text{ V}/\mu\text{m}$  and  $|V'_{ap}| = 20 \text{ V}/\mu\text{m}$ . Find  $A_1$ ,  $A_2$ , and  $A_v$  if all devices are  $0.8 \mu\text{m}$  long and are operated at equal overdrive voltages of  $0.25 \text{ V}$  magnitude. Also, determine the opamp output resistance obtained when the second stage is biased at  $0.4 \text{ mA}$ . What do you expect the output resistance of a unity-gain voltage amplifier to be, using this opamp?

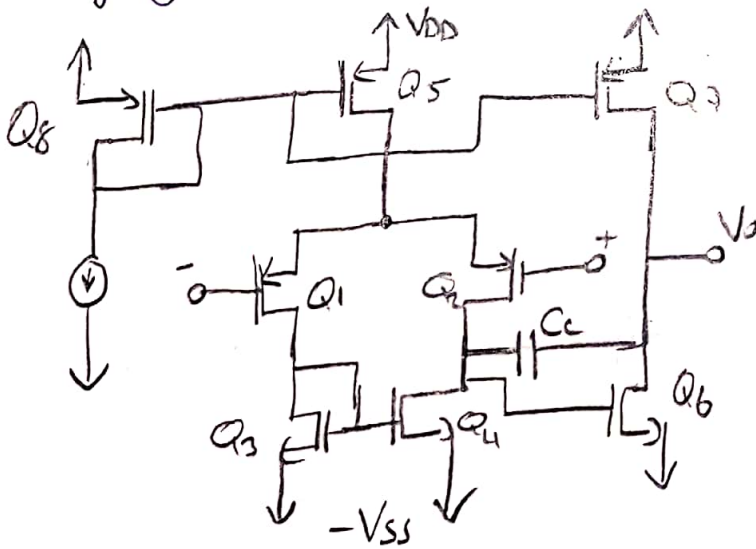

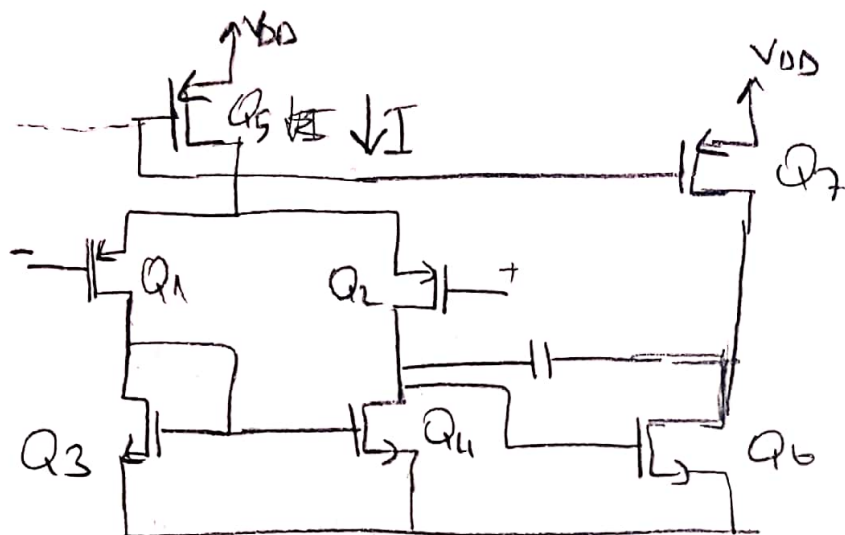

$$\rightarrow I_{D5} = 2I_{D4} = I \quad V_{G6} \approx V_{D4} \approx V_{D3}$$

$$I_{D6} = \frac{(W/L)_6}{(W/L)_4} I_{D4} = \frac{(W/L)_6}{(W/L)_4} \frac{I}{2} = I_{D6}$$

$$I_{D7} = \frac{(W/L)_7}{(W/L)_5} I_{D5} = \frac{(W/L)_7}{(W/L)_5} I$$

$$I_{D6} = I_{D7}$$

$$\frac{(W/L)_6}{(W/L)_4} \frac{I}{2} = \frac{(W/L)_7}{(W/L)_5} I \rightarrow \frac{(W/L)_6}{(W/L)_4} = 2 \cdot \frac{(W/L)_7}{(W/L)_5}$$

$$I_{D4} = I_{D1} = \frac{0.4}{2} \text{ mA} = 0.2 \text{ mA}$$

$$I_{D6} = I_{D7} = 0.4 \text{ mA}$$

$$I_{D5} = I_{D7}$$

$$g_{m1} = \frac{2I_{D1}}{V_{GS1} - V_{th}} = \frac{2I_{D1}}{V_{ov1}} = \frac{2 \cdot 0.2 \times 10^{-3}}{0.25} = 1.6 \text{ mS}$$

$$g_{m6} = \frac{2I_{D6}}{V_{GS6} - V_{th,n}} = \frac{2 \cdot (0.4) \times 10^{-3}}{0.25 \text{ V}} = 3.2 \text{ mS}$$

$$r_{op} = \frac{V_{A,P}}{I_D} \Rightarrow r_{O2} = \frac{V_{A,P}}{0.2 \text{ mA}} \quad r_{O4} = \frac{V_{A,n}}{0.2 \text{ mA}}$$

$$r_{O,b} = \frac{V_{A,n}}{0.4 \text{ mA}} \quad r_{O,7} = \frac{V_{A,P}}{0.4 \text{ mA}}$$

(4)

$$V_{A,P} = E_{A,P} \cdot L = 20 \text{ V}/\mu\text{m} \cdot 0.8 \mu\text{m} = 16 \text{ V}$$

$$r_{ob} = \frac{V_{A1n}}{I_{D6}} = \frac{20V}{0.4 \times 10^{-3}} = 50k\Omega$$

$$r_{o7} = \frac{V_{A1P}}{I_{D7}} = \frac{16V}{0.4 \times 10^{-3}} = 40k\Omega$$

$$A = \begin{bmatrix} -g_{m1} & (r_{o2} || r_{o4}) \end{bmatrix} \cdot \begin{bmatrix} -g_{m6} & (r_{o6} || r_{o7}) \end{bmatrix}$$

$\downarrow$                        $\downarrow$                        $\downarrow$                        $\downarrow$                        $\downarrow$                        $\downarrow$   
 $1.6\text{mS}$                        $80\text{k}\Omega$                        $100\text{k}\Omega$                        $3.2\text{mS}$                        $50\text{k}\Omega$                        $40\text{k}\Omega$

$$A = [(-1.6), (44.44), (-3.2), (22.22)]$$

$$1 = \frac{A}{1 + A \cdot \beta} \rightarrow A = 1 + A \beta \rightarrow \boxed{1 + A \beta = 5056.739}$$

$$\beta = 0.99$$

$$\beta = 0.99980$$

$$R_{out,f} = \frac{R_{o1} || R_{o2}}{1 + A\beta} = \frac{22.22k\Omega}{5056.739} = 4.3945\Omega$$

feedback ile çıkış empedansı  $\approx 5000$  kat daha azalmıştır.