

HW3

Abdullah MEMİŞOĞLU

171024001

İsim

Q1. A CMOS amplifier is shown in fig P9.14

The parameters for the NMOS are $V_t = +2V$, $V_M = -40V$, and $V_{GS} = +4V$ at $I_D = 1mA$: the parameters for the PMOS are $V_t = -3V$, $V_M = 40V$, and $V_{GS} = -6V$ at $I_D = 1mA$. Calculate (a) A_d , A_c and CMRR and (b) R_{id} and R_{ic} .

= M_6, M_7 ve M_8 in
Gate-Drain bağlantısından
dolayı
= $V_G = V_D$
 $V_{GS} = V_{DS} \rightarrow (M_6, M_7, M_8)$

$$- V_{DS_8} + V_{DS_7} + V_{DS_6} = V_{DD} - V_{SS}$$

$$= V_{GS} + V_{GS} + V_{GS} = 5 - (-5)$$

Bağlantıdan kaynaklı 3 transistörün saturasyonda olduğu görülmektedir.

$$I_D = \frac{1}{2} M_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

NMOS'lar için verilen değerler

$$V_t = 2V \quad V_{GS} = V_{DS} = \frac{10}{3} = 3.33V$$

$$M_n C_{ox} = 8.5 \mu A/V^2$$


$$\frac{W}{L} = \frac{30}{10} \rightarrow \text{her Mosfet için } \frac{30}{10} \text{ verilmesi.}$$

$$I_D = 22.553 \mu A$$

$$I_{TAIL} = I_D$$

$$I_{TAIL} = 22.553 \mu A$$

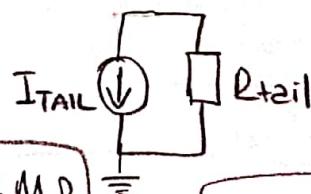
$$R_{tail} = \frac{V_M}{I_{tail}} = \frac{40V}{22.553 \mu A} = 1.773 M\Omega$$



$$R_{tail} = 1.773 M\Omega$$

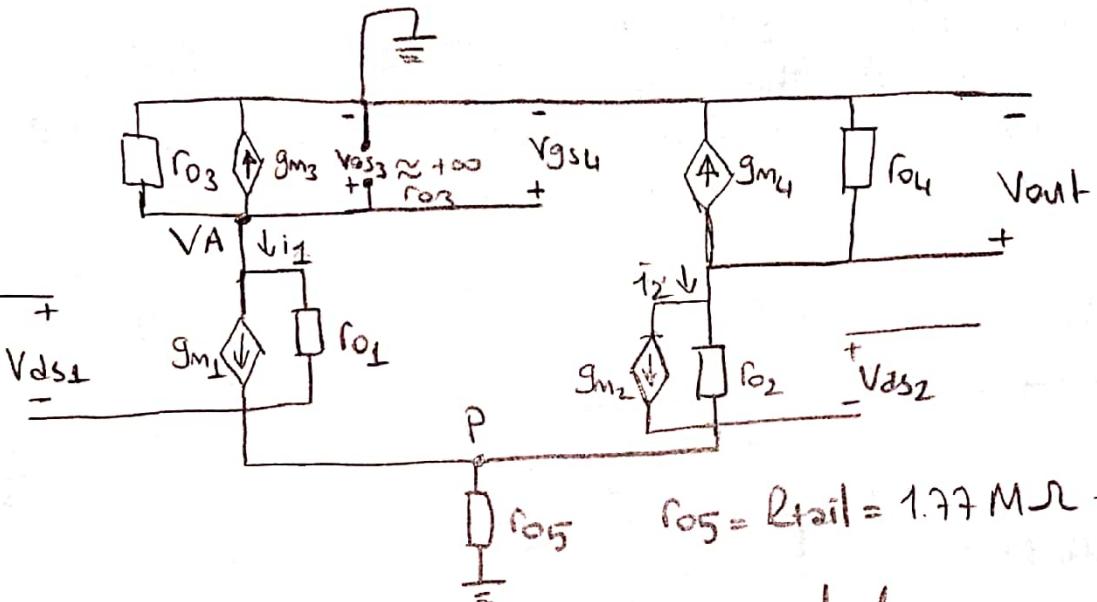(1)

Differential Mode (active loaded single ended differential amp. gibi davranış) (symmetric)



$r_{O5} = R_{tail} = 1.77 \text{ M}\Omega \rightarrow \text{azik devre}$
kabul edilebilecek
kadar büyük.

PMOS'lar ve NMOS'lar eş transistörlerdir
(NMOS'lar kendi aralarında
PMOS'lar kendi aralarında)

$$g_{m3} = g_{m4}, g_{m1} = g_{m2}$$

$$r_{O3} = r_{O4}$$

$$r_{O1} = r_{O2}$$

$$V_{gs3} = V_{gs4} = V_A$$

$$\bar{i}_1 + \bar{i}_2 = 0$$

symetrideki gelen eşitlikler yararlıdır.

$$V_{gs3} = -\bar{i}_1 \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) \rightarrow \text{eq.1}$$

$$\bar{i}_2 + g_{m3} V_A + \frac{V_{out}}{r_{O3}} = 0$$

$$g_{m3} V_A + \frac{V_{out}}{r_{O3}} = -\bar{i}_2 \quad \rightarrow \quad g_{m3} \cdot \bar{i}_1 \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) + \frac{V_{out}}{r_{O3}} = \bar{i}_1$$

$$\bar{i}_1 + \bar{i}_1 g_{m3} \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) = \frac{V_{out}}{r_{O3}} \rightarrow \bar{i}_1 \left(1 + g_{m3} \cdot \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) \right) = \frac{V_{out}}{r_{O3}}$$

$$\bar{i}_1 = \frac{\frac{V_{out}}{r_{O3}}}{r_3 \cdot \left(1 + g_{m3} \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) \right)} \rightarrow \text{eq.2}$$

Gelişim

$$-V_2 + (i_1 - g_{m1} \cdot V_{ds1}) r_{o1} - (i_2 - g_{m1} \cdot V_{ds2}) r_{o2} + V_{out} = 0$$

$$i_1 = -i_2$$

$$-V_2 + (2i_1 r_{o1}) - g_{m1} r_{o1} (V_{ds1} - V_{ds2}) + V_{out} = 0$$

eq.1 ve eq.2 (V_2 ve i_1) yerine yazılırsa

$$= -\left(-i_1 \cdot \left(\frac{1}{g_{m3}} \parallel r_{o3}\right)\right) + (2i_1 r_{o1}) - g_{m1} r_{o1} (V_{ds1} - V_{ds2}) + V_{out} = 0$$

$$= \frac{V_{out} \cdot (1/g_{m3} \parallel r_{o3})}{r_3 \cdot (1 + g_{m3} \left(\frac{1}{g_{m3}} \parallel r_{o3}\right))} + \frac{2 V_{out} \cdot r_{o1}}{r_{o3} \cdot (1 + g_{m3} \left(\frac{1}{g_{m3}} \parallel r_{o3}\right))} - g_{m1} r_{o1} (V_{ds1} - V_{ds2}) + V_{out} = 0$$

$$= \frac{V_{out} \cdot \left(\frac{1}{g_{m3}}\right)}{r_{o3} \cdot 2} + \frac{2 V_{out} r_{o1}}{r_{o3} \cdot 2} + V_{out} = g_{m1} r_{o1} (V_{ds1} - V_{ds2})$$

$$= V_{out} \left[\frac{\frac{1}{g_{m3}} + 2r_{o1} + 2r_{o3}}{2r_{o3}} \right] = g_{m1} r_{o1} (V_{ds1} - V_{ds2})$$

$$\Rightarrow V_{out} \cdot I = g_{m1} r_{o1} (V_{ds1} - V_{ds2}) \rightarrow \frac{V_{out}}{(V_{ds1} - V_{ds2})} = \frac{g_{m1} r_{o1}}{I}$$

$$V_{ds1} - V_{ds2} = V_{in1} - V_{in2}$$



buylece $\frac{V_{out}}{V_{in1} - V_{in2}}$ → kazanç verir.

$$\frac{V_{out}}{V_{in1} - V_{in2}} = g_{m1} r_{o1} \cdot \frac{1}{I} = g_{m1} r_{o1} \cdot \frac{2r_{o3}}{\frac{1}{g_{m3}} + 2r_{o1} + 2r_{o3}} \quad \frac{1}{g_{m3}} \ll r_{o1} \parallel r_{o3}$$

$$\frac{V_{out}}{\Delta V_{in1}} = g_{m1} \cdot \frac{2r_{o1} \cdot r_{o3}}{2r_{o1} + 2r_{o3}} = g_{m1} \cdot \underbrace{\left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}}\right)}_{r_{o1} \parallel r_{o3}} \quad (3)$$

$$\frac{V_{out}}{\Delta V_{in}} = g_m \cdot (r_{o1} \parallel r_{o3})$$

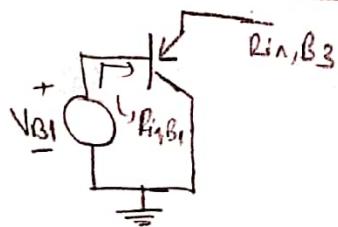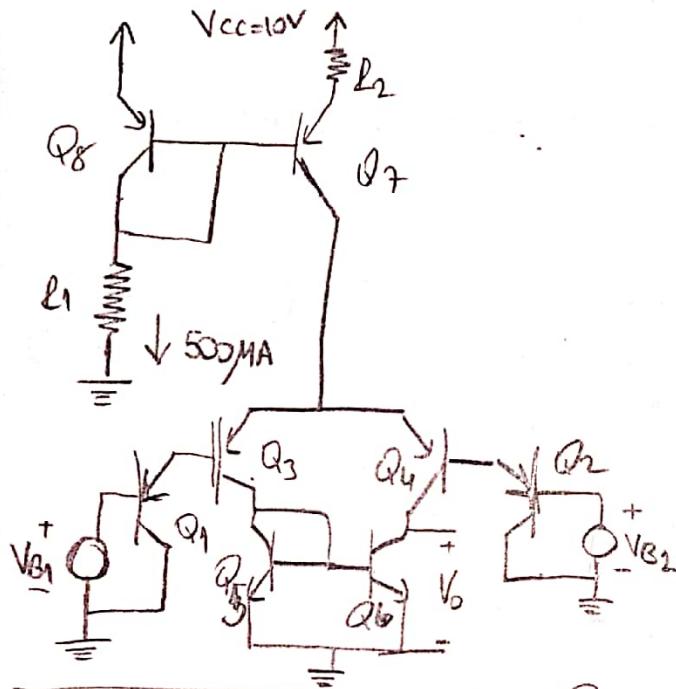Q2 A differential amplifier is shown in Fig P9.42. The transistors are identical. Assume $V_{BE} = 0.7V$, $V_T = 26mV$, $\beta_F(npn) = 100$, $\beta_F(pnp) = 50$, $V_A = 40V$ and $V_{CC} = 10V$. Calculate the values of R_1 , R_2 , A_d , R_{id} , A_c , R_{ic} and CMRR.



$$R_{in,B1} \approx (1 + g_m \cdot R_{in,B3}) R_{\pi 1}$$

$$R_{in,B2} \approx (1 + g_m \cdot R_{in,B4}) R_{\pi 2}$$

$$V_{B3} = V_{B1} \frac{R_{in,B3}}{R_{in,B3} + \frac{1}{g_m}}$$

$$V_{B4} = V_{B2} \frac{R_{in,B4}}{R_{in,B4} + \frac{1}{g_m}}$$


$$R_{in,B3} \gg \frac{1}{g_m}$$

$$R_{in,B4} \gg \frac{1}{g_m}$$

$$V_{B3} \approx V_{B1} \cdot 1 \quad V_{B4} \approx V_{B2}$$

(4)

Differential Mode in small signal.

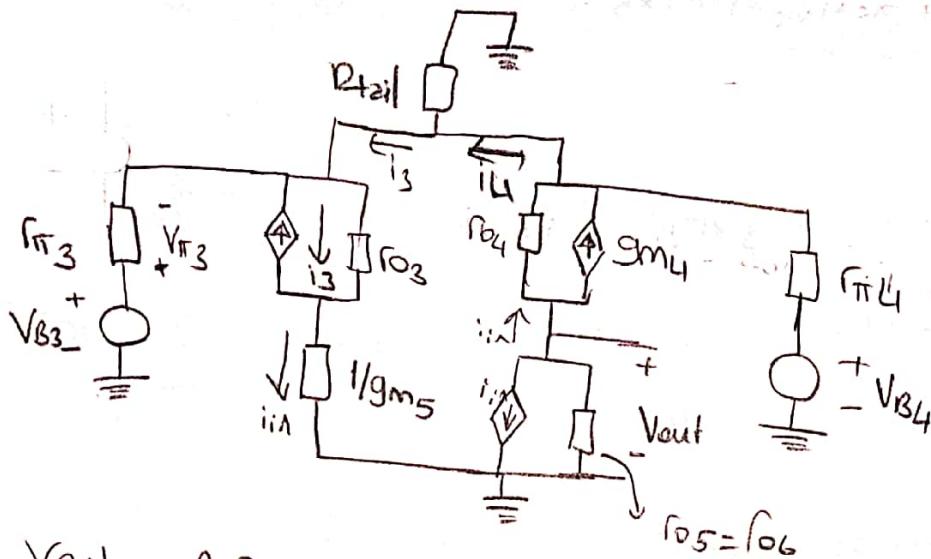

$$V_{out} = -2 \bar{i}_{in} R_O5$$

$$\bar{i}_D = \bar{i}_3 + \bar{i}_{tail}$$

$$-\bar{i}_3 + \bar{i}_{O3} - g_{m3} V_{\pi_3} + \frac{(i_4 - i_3) R_{tail} - V_{B3}}{R_{\pi_3}} = 0$$

$$V_{\pi_3} = V_{B3} - (i_4 - i_3) R_{tail}$$

$$\bar{i}_{in} + g_{m3} V_{\pi_3} - \bar{i}_{O3} = 0, \quad -\bar{i}_{in} + \bar{i}_{O4} + g_{m4} V_{\pi_4} = 0$$

$$i_4 - i_{O4} - g_{m4} V_{\pi_4} + \frac{(i_4 - i_3) R_{tail} - V_{B4}}{R_{\pi_4}} = 0$$

$$V_{\pi_4} = V_{B4} - (i_4 - i_3) R_{tail}$$

$$V_{B3} - V_{\pi_3} = V_{B4} - V_{\pi_4}, \quad V_{B3} - V_{B4} = V_{\pi_3} - V_{\pi_4}$$

$$\bar{i}_{O3} R_O3 + \bar{i}_{in} \cdot \frac{1}{g_{m5}} + 2 \bar{i}_{in} R_O5 + \bar{i}_{O4} R_O4 = 0 \quad \text{eq.1//}$$

$$\bar{i}_{O3} = \bar{i}_{in} + g_{m3} V_{\pi_3}, \quad \bar{i}_{O4} = \bar{i}_{in} - g_{m4} V_{\pi_4} \rightarrow \text{bu iki esitlik}$$

$$\boxed{(\bar{i}_{in} + g_{m3} V_{\pi_3}) R_O3 + \bar{i}_{in} \frac{1}{g_{m5}} + 2 \bar{i}_{in} R_O5 + (i_{in} - g_{m4} V_{\pi_4}) R_O4 = 0} \quad \text{eq.1 de yesil} \\ \text{yezilise}$$

$$R_O3 = R_O4 \quad \text{ve} \quad g_{m3} = g_{m4} \quad \text{eq.2}$$

esitlikleri eq.2 de yesine yazilrsa

(5)

$$\left((i_{in} + g_m V_{T3}) R_3 + i_{in} \cdot \frac{1}{g_m s} + 2i_{in} R_5 + (i_{in} - g_m V_{T4}) R_4 = 0 \right)$$

$R_3 = R_4, g_m = g_m$

$$2i_{in} R_3 + 2i_{in} R_5 + g_m R_3 V_{T3} - g_m R_3 V_{T4} + i_{in} \frac{1}{g_m s} = 0$$

$$= 2i_{in} R_3 + 2i_{in} R_5 + \underbrace{g_m R_3}_{VB_3 - VB_4} (V_{T3} - V_{T4}) + i_{in} \cancel{\frac{1}{g_m s}}$$

$\frac{1}{g_m s} \ll R_3$

$$= 2i_{in}(R_3 + R_5) + g_m R_3 (VB_3 - VB_4), \quad -2i_{in} R_5 = V_{out}$$

$$= 2i_{in} \cdot \frac{-2i_{in} R_5}{2i_{in} R_5} \cdot (R_3 + R_5) = -g_m R_3 (VB_3 - VB_4)$$

$$= -2i_{in} R_5 \left(\frac{R_3 + R_5}{R_5} \right) = V_{out} \cdot \left(\frac{-(R_3 + R_5)}{R_5} \right) = -g_m R_3 (VB_3 - VB_4)$$

$$= \frac{V_{out}}{VB_3 - VB_4} = g_m R_3 \cdot \frac{1}{\left(\frac{R_3 + R_5}{R_5} \right)} \Rightarrow \frac{g_m R_3 R_5}{R_3 + R_5}$$

$$\frac{V_{out}}{VB_3 - VB_4} = g_m \cdot \left(\frac{1}{\frac{1}{R_3} + \frac{1}{R_5}} \right) \rightarrow \frac{V_{out}}{VB_3 - VB_4} = g_m \cdot (R_3 \parallel R_5)$$

differential mode gain


common mode gain $VB_3 = VB_4$ ise $V_{out} = 0$ oldugundan

$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{g_m (R_3 \parallel R_5)}{0} \approx +\infty$$

$A_c = 0$

6

Design (Tail Current)

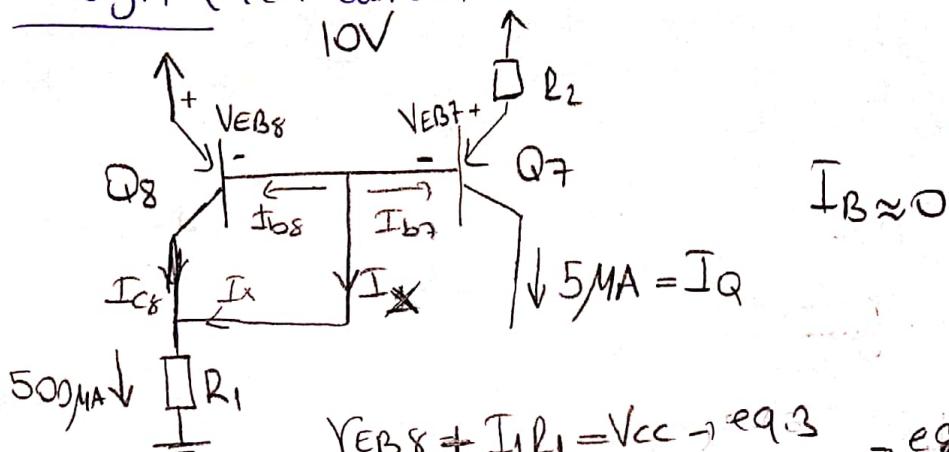

$$V_{EB8} + I_1 R_1 = V_{CC} \rightarrow \text{eq.3} \quad \text{eq.4}$$

$$-V_{EB8} + V_{EB7} + I_Q R_2 = 0 \quad V_T = 26mV$$

$$I_1 = I_s \cdot \exp\left(\frac{V_{EB8}}{V_T}\right) \quad V_{CC} = 10V$$

$$I_Q = I_s \cdot \exp\left(\frac{V_{EB7}}{V_T}\right) \quad \text{eq.5} \quad I_1 = 500\text{mA}$$

$$\text{eq.6} \quad I_Q = 5\text{mA}$$

$$V_{EB8} + 500 \cdot 10^{-6} R_1 = 10 \rightarrow \text{eq.3}$$

$$-V_{EB8} + V_{EB7} + 5 \cdot 10^{-6} R_2 = 0$$

$$500 \cdot 10^{-6} = I_s \cdot \exp\left(\frac{V_{EB8}}{26 \cdot 10^{-3}}\right)$$

$$5 \cdot 10^{-6} = I_s \cdot \exp\left(\frac{V_{EB7}}{26 \cdot 10^{-3}}\right)$$

$$\frac{5 \cdot 10^{-6}}{10^{-13}} = \exp\left(\frac{V_{EB7}}{26 \cdot 10^{-3}}\right) \text{ eq.6} \rightarrow b_1\left(\frac{5 \cdot 10^{-6}}{10^{-13}}\right) = \frac{V_{EB7}}{26 \cdot 10^{-3}}$$

$$\text{eq.5} \Rightarrow 500 \cdot 10^{-6} = 10^{-13} \exp\left(\frac{V_{EB8}}{26 \cdot 10^{-3}}\right)$$

$$17.727 = \frac{V_{EB7}}{26 \cdot 10^{-3}}$$

$$b_1(5 \cdot 10^{-6}) = \frac{V_{EB7}}{26 \cdot 10^{-3}} \rightarrow V_{EB7} = 0.460V$$

$$\text{eq.4} \rightarrow -0.580V + 0.460V + 5 \cdot 10^{-6} \cdot R_2 = 0 \rightarrow 5 \cdot 10^{-6} \cdot R_2 = 0.1206$$


$$\text{eq.3} \rightarrow 0.580 + 500 \cdot 10^{-6} \cdot R_1 = 10$$

$$R_2 = 24.130k\Omega$$

$$R_1 = 18.840k\Omega$$

7

R_{tail} iain

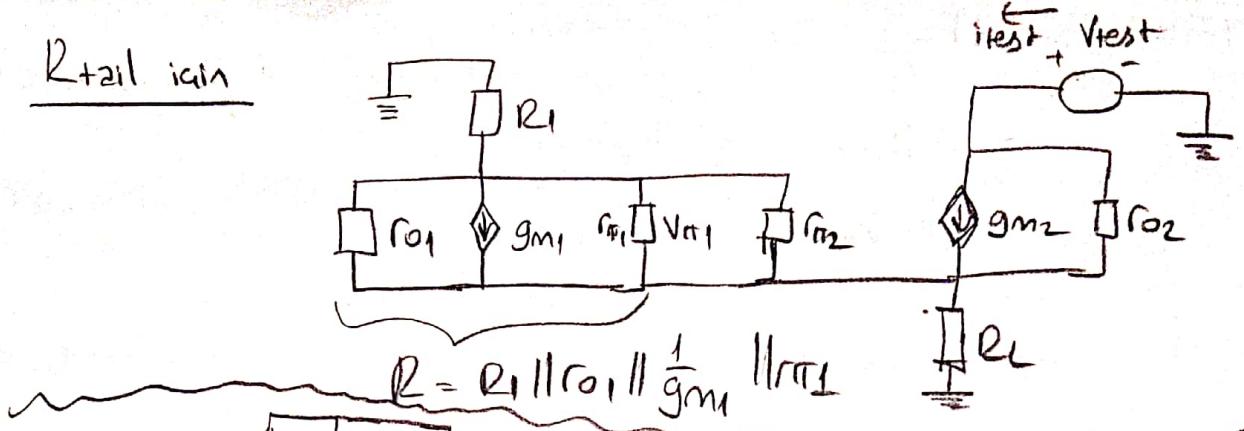


$$R_{out} = \frac{V_{test}}{i_{test}} = r_{o2} + g_{m2}r_{o2} \frac{R_2r_{\pi 2}}{R_2+r_{\pi 2}+R} + \frac{R_2(R+r_{\pi 2})}{R_2+r_{\pi 2}+R}$$

$$V_{test} = (i_{test} - g_{m2}V_{\pi 2})r_{o2} + i_{test} \cdot \frac{R_2(R+r_{\pi 2})}{R_2+r_{\pi 2}+R}$$

$$R_{out} = \frac{V_{test}}{i_{test}} = r_{o2} + g_{m2}r_{o2} \frac{R_2r_{\pi 2}}{R_2+r_{\pi 2}+R} + \frac{R_2(R+r_{\pi 2})}{R_2+r_{\pi 2}+R}$$

$$R_{out} = r_{o2} + (g_{m2}r_{o2} + 1) \frac{R_2 \cdot r_{\pi 2} + R_2 \cdot R}{R_2 + r_{\pi 2} + R} + \frac{R_2 \cdot R}{R_2 + r_{\pi 2} + R}$$

Large signal analysis

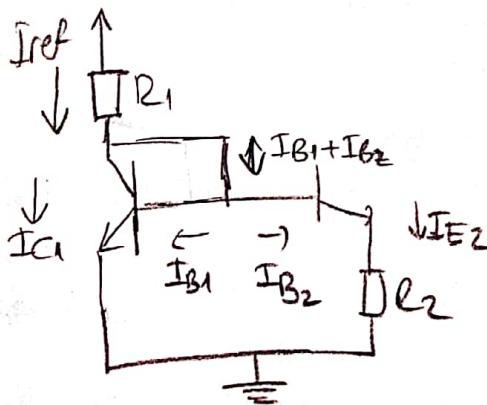

$$I_{ref} = I_{c1} + I_{B1} + I_{B2} \quad \boxed{I_{ref} = I_{B1}(\beta + 1) + I_{B2}}$$

$$I_{ref} = \frac{V_{cc} - V_{BE1}}{R_1} = \frac{V_{cc} - V_T \ln \frac{I_{c1}}{I_s}}{R_1}$$

$$I_{ref} = I_{B1}(\beta + 1) + I_{B2} = \frac{V_{cc} - V_T \ln \left(\frac{I_{c1}}{I_s} \right)}{R_1}$$

$$I_{c1} = I_s \exp \left(\frac{V_{BE1}}{V_T} \right) \quad I_{c2} = I_o = I_s \exp \left(\frac{V_{BE2}}{V_T} \right) = \beta I_{B2} \quad \text{eq.7}$$

$$V_{BE1} = V_{B2} + (\beta + 1) \cdot I_{B2} \cdot R_2$$

$$V_T \ln \frac{I_{c1}}{I_{c2}} = (\beta + 1) \cdot I_{B2} R_2 = V_T \ln \left(\frac{I_{B1}}{I_{B2}} \right) \rightarrow \text{eq.8}$$

(8)

eq.7 ve eq. 8 kullanılsak

$$I_{B1}(\beta+1) + I_{B2} = \frac{V_{cc} - V_T \ln\left(\frac{I_{C1}}{I_S}\right)}{R_1}$$

$$I_{B1}.101 + I_{B2} = \frac{10 - 26 \times 10^{-3} \ln\left(\frac{100 I_{B1}}{I_S}\right)}{18.840 k\Omega}$$

$$101 I_{B1} + \frac{26 \times 10^{-3}}{18.840 k\Omega} \cdot \ln(10^{-11} I_{B1}) + I_{B2} = \frac{10}{18.840 k\Omega}$$

→ $10^{-15} \text{ ve } 10^{-12}$ arası
 I_S tipik değer $10^{-13} A$

$$V_T = 26 mV$$

$$V_{cc} \sim 10 V$$

$$\beta = 100$$

$$R_1 = 18.840 k\Omega$$

$$R_2 = 24.130 k\Omega$$

eq.8 → $101 I_{B2} R_2 = 26 \times 10^{-3} \ln\left(\frac{I_{B1}}{I_{B2}}\right)$

$$101 I_{B2} \cdot 24.130 k\Omega = 26 \times 10^{-3} \ln\left(\frac{I_{B1}}{I_{B2}}\right)$$

$$93.735 \times 10^6 I_{B2} = \ln\left(\frac{I_{B1}}{I_{B2}}\right)$$

$$I_{B1} = I_{B2} \cdot e^{93.735 \times 10^6 I_{B2}} \quad \text{eq.9}$$

eq.7'de yerine yazdırıldım.

$$101 I_{B2} \cdot e^{93.735 \times 10^6 I_{B2}} + \frac{26 \times 10^{-3}}{18.840 k\Omega} \cdot \ln\left(10^{-11} I_{B2} \cdot e^{93.735 \times 10^6 I_{B2}}\right) + I_{B2} = \frac{10}{18.840 k\Omega}$$

$$\ln(10^{-11} I_{B2}) + \ln(e^{93.735 \times 10^6 I_{B2}})$$


$$101 I_{B2} e^{x \cdot I_{B2}} + \frac{26 \times 10^{-3}}{18.840 k\Omega} \left(\ln(10^{-11} I_{B2}) + x \cdot I_{B2} \right) + I_{B2} = \frac{10}{18.840 k\Omega}$$

$$I_{B2} (101 e^{x \cdot I_{B2}} + 1) + \frac{26 \times 10^{-3}}{18.840 k\Omega} \cdot \ln(10^{-11} I_{B2}) + \frac{26 \times 10^{-3}}{18.840 k\Omega} \cdot x \cdot I_{B2} = \frac{10}{18.840 k\Omega}$$

x bir sabt olduğundan I_2 burdan bulunur. eq.9'da yerine yazılarsa

I_{B1} ve I_{B2} bulunur

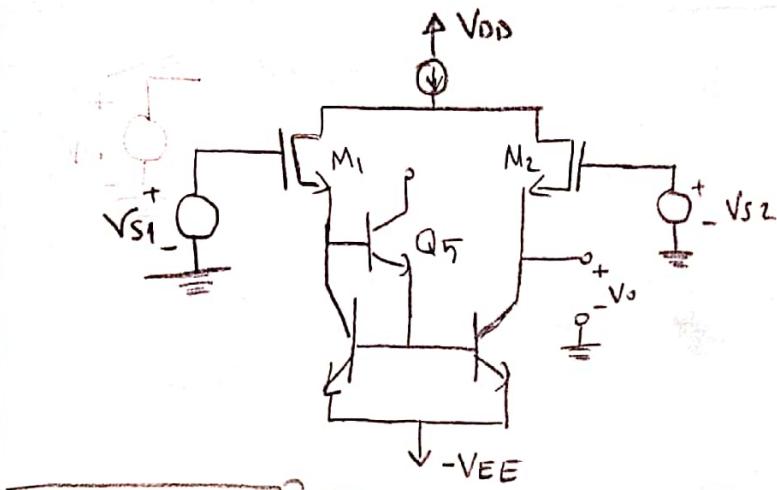Q3: A Bi CMOS amplifier is shown in fig Pg.47. The PMOS parameters are $V_T = -3V$ and $V_{GS} = -6V$ at $I_D = 1mA$. The BJT parameters are $\beta_{F(npn)} = 100$, $\beta_F(pnp) = 50$ and $V_A = 2.10V$. Assume $V_{DD} = -V_{EE} = 15V$ and $I_Q = 200\mu A$. Ad = ? Acc = ? CMRR




$$I_Q = 200\text{mA} \quad I_{D1} = I_{D2} = 100\mu\text{A} \quad I_{D2} = \frac{1}{2} M_p C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$1\text{mA} = \frac{1}{2} M_p C_{ox} \frac{W}{L} (6 - |-3V|)^2 = \frac{9}{2} M_p C_{ox} \frac{W}{L} = 1\text{mA}$$

$$100\mu\text{A} = \frac{1}{2} \cdot 2.22 \times 10^{-4} \cdot (V_{GS} - 3)^2$$

$$0.900 = (V_{GS} - 3)^2 \rightarrow \sqrt{0.900} = |V_{GS} - 3| = 0.949 \rightarrow V_{GS} = 3.949\text{V}$$

Small signal analysis

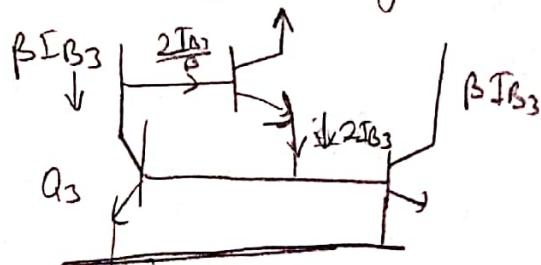

$$g_{m3} = g_{m4} = \frac{\beta I_{B3}}{V_T}$$

$$f_{\pi3} = f_{\pi4} = \frac{\beta}{g_{m3}} = \frac{V_T}{I_{B3}}$$


$$g_{m5} = \frac{2\beta I_{B3}}{(\beta+1)V_T}$$

$$f_{\pi5} = \frac{(\beta+1)V_T}{2IB_3}$$


$$f_{o3} = f_{o4} = \frac{V_A}{\beta I_{B3}}$$

$$f_{o5} = \frac{(\beta+1)V_A}{2\beta I_{B3}}$$

K

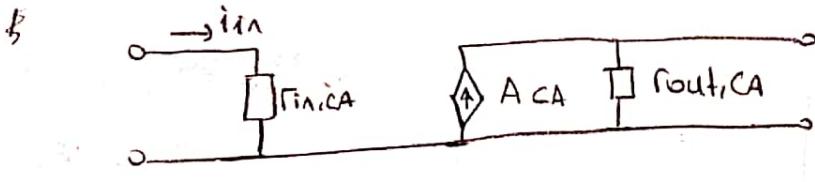

$R_{in,CA}$ A_{CA}

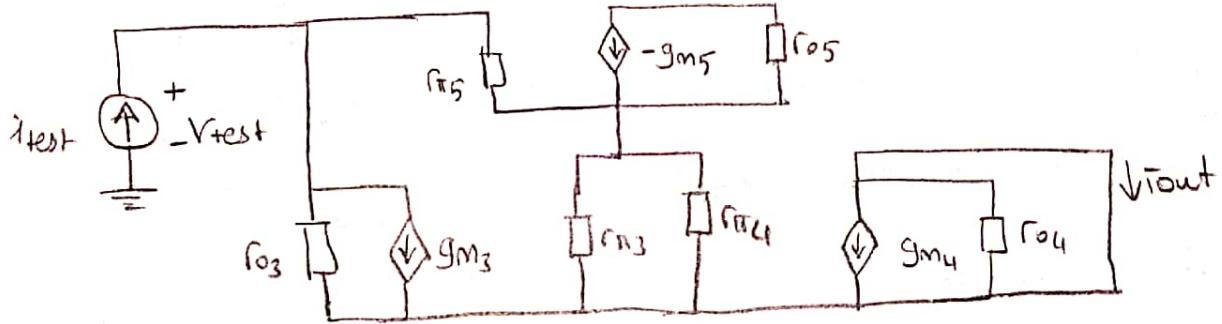

$$V_{test} = V_{\pi_3} + V_{\pi_5} \quad -I_{test} + \frac{V_{test}}{r_{\pi_3}} + g_{m3} V_{\pi_3} + \frac{V_{test} - V_{\pi_3}}{r_{\pi_5}} = 0$$

$$-g_{m5} V_{\pi_5} + \frac{V_{\pi_3}}{r_{\pi_5}} + \frac{V_{\pi_3}}{r_{\pi_3}} + \frac{V_{\pi_3}}{r_{\pi_4}} + \frac{V_{\pi_3} - V_{test}}{r_{\pi_5}} = 0$$

$$I_{test} = \frac{V_{test}}{r_{\pi_3} || r_{\pi_5}} + V_{\pi_3} \left[g_{m3} - \frac{1}{r_{\pi_5}} \right] \quad \xrightarrow{\text{tipi L degeri}}$$

$$I_{test} = \frac{V_{test}}{r_{\pi_3} || r_{\pi_5}} + V_{\pi_3} g_{m3} = 0 \quad V_A = 100V \quad V_T = 26mV$$

$$\beta = 100 \quad r_{\pi_3} = \frac{100V}{26mV} = \frac{1}{I_{B3}}$$

$$r_{\pi_5} = \frac{100 \cdot (26mV)}{2I_{B3}} = \frac{1.3}{I_{B3}}$$

$$\frac{V_{\pi_3}}{\frac{1}{g_{m5}} || r_{\pi_5} || r_{\pi_3} || r_{\pi_4} || r_{\pi_5}} = \frac{V_{test}}{\frac{1}{g_{m5}} || r_{\pi_5}} = \frac{V_{test}}{r_{\pi_5} / (1 + \beta)}$$

$$\frac{1}{g_{m5}} \ll r_{\pi_5} \quad r_{\pi_3} \ll r_{\pi_5}$$

$$\frac{V_{\pi_3}}{\frac{1}{g_{m5}} || \frac{r_{\pi_3}}{2}} \rightarrow \frac{1}{g_{m5}} = \frac{V_T}{2I_{B3}} \rightarrow \frac{V_{\pi_3}}{\underbrace{r_{\pi_3}/4}_{\geq r_{\pi_3} || r_{\pi_4}}} = \frac{V_{test}}{\underbrace{r_{\pi_5}/(1+\beta)}_{V_T/2I_{B3}}} \quad 2V_{\pi_3} = V_{test}$$

$$\frac{1}{g_{m5}} = \frac{V_{\pi_3}}{2}$$

(11)

$$\dot{i}_{test} = \frac{V_{test}}{r_{03} \| r_{\pi 5}} + \frac{V_{test}}{2/gm_3} \quad \frac{2}{gm_3} \ll r_{03} \quad r_{\pi 5} = \frac{2V_T}{B \beta B_3}$$

$$\frac{V_{test}}{\dot{i}_{test}} \approx \frac{2}{gm_3} = \frac{2V_T}{B \beta B_3}$$

$$\frac{V_{test}}{\dot{i}_{test}} = r_{in, CA} = \frac{2}{gm_3}$$

ACA i_{in}

$$V_{\pi 3} = V_{\pi 4} = \frac{V_{test}}{2} \quad gm_u V_{\pi 4} = -i_{out} \quad gm_u \frac{V_{test}}{2} = -i_{out}$$

$$\frac{gm_u}{2} \cdot \frac{2\dot{i}_{test}}{gm_3} = -i_{out} \quad \frac{i_{out}}{\dot{i}_{test}} = -1 = A_{CA}$$


 A_{CA} i_{in}

$$i_{out, CA} = f_{04} = f_{03}$$

$$V_{test} = 0$$



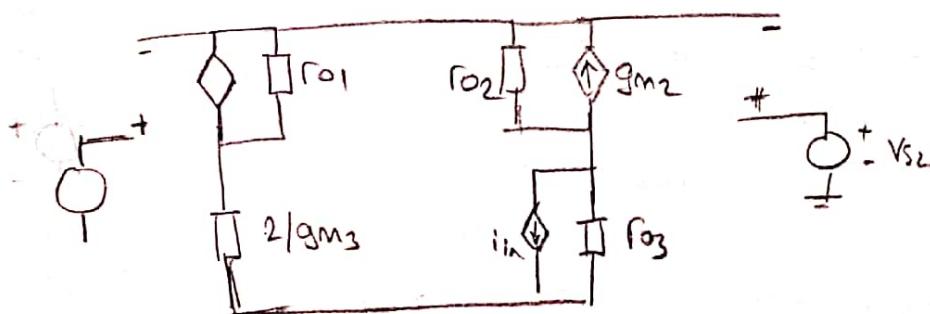R_o small signal equivalent with active load.



$$\frac{2}{gm_3} i_{in} + 2i_{in} R_{03} + (i_{in} - gm_2 V_{GS2}) R_{02} + (i_{in} + gm_1 V_{GS1}) R_{01} = 0$$

note $gm_1 = gm_2$, $r_{01} = r_{02}$, $V_{out} = -2i_{in} R_{03}$

$$\dot{i}_{in} \left[\frac{2}{gm_3} + 2R_{03} + \underbrace{R_{02} + R_{01}}_{2R_{01}} \right] + gm_1 R_{01} (V_{GS1} - V_{GS2}) = 0$$

$$2i_{in}(R_{03} + R_{01}) = -gm_1 R_{01} (V_{GS1} - V_{GS2})$$

(12)

and inout resistance of the amplifier

$$V_{S1} - V_{GS1} = V_{S2} - V_{GS2} \rightarrow V_{S1} - V_{S2} = V_{GS1} - V_{GS2}$$

$$\left[-2 \text{ in } R_{O3} \right] \left[-\frac{R_{O1} + R_{O2}}{R_{O3}} \right] = -g_m r_{o1} (V_{S1} - V_{S2})$$

$$\frac{V_{out}}{V_{S1} - V_{S2}} = g_{m1} \left[\frac{R_{O1} \cdot R_{O3}}{R_{O1} + R_{O3}} \right] = g_{m1} \left[\frac{1}{\frac{1}{R_{O1}} + \frac{1}{R_{O3}}} \right] = g_{m1} (R_{O1} // R_{O3})$$

common mode gain

$$V_{S1} = V_{S2} \rightarrow V_{out} = 0 \quad A_c = 0$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{g_{m1} (R_{O1} // R_{O3})}{0} \approx +\infty \approx CMRR$$



Q4. Calculate the common mode gain of the circuit depicted in Fig 10.87. Assume $d \gg 0$, $g_m r_o \gg 1$, and use the relationship $A_d = -g_m R_{out}$

$M_5 \rightarrow$ current source

$R_{out,CS} =$ current source \rightarrow R_{out} .

$R_{out,CS} = R_{O5}$


Differential Mode

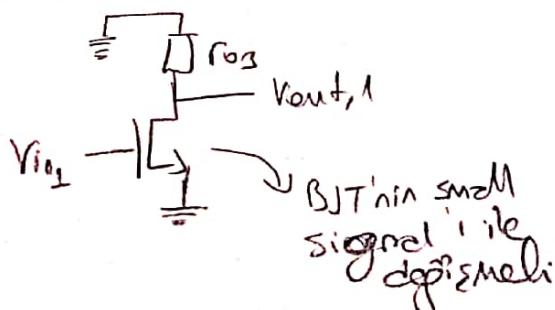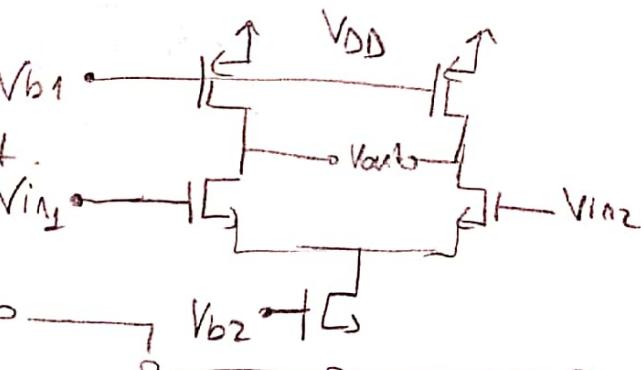

$$\frac{V_{out,1}}{V_{in,1}} = -g_{m1} (R_{O1} // R_{O3})$$

$$A_d = \frac{V_{out,1} - V_{out,2}}{V_{in,1} - V_{in,2}} = -g_{m1} (R_{O1} // R_{O3})$$

Common Mode

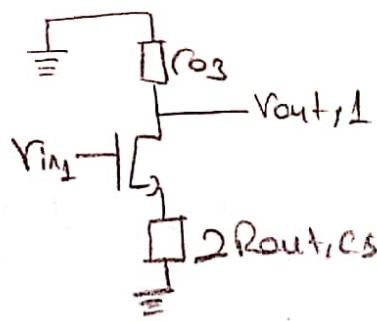

$$A_C = \frac{V_{out,1}}{V_{in,1}} = \frac{-g_m 1}{1 + g_m 1 \cdot 2R_{out,cs}} \cdot [R_03 \parallel R_{out, TCA}]$$

$$R_{out, TCA} = (1 + g_m 1 \cdot R_01) \cdot 2R_{out,cs} + R_01$$

$R_03 \ll R_{out, TCA}$

$$A_C = \frac{-g_m 1}{1 + g_m 1 \cdot 2R_{out,cs}} \cdot [R_03 \parallel R_{out, TCA}] \underset{\approx R_03}{\sim} = \frac{-g_m 1 \cdot R_03}{1 + g_m 1 \cdot 2R_{out,cs}}$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{-g_m 1 \frac{R_01 \cdot R_03}{R_01 + R_03}}{\frac{-g_m 1 \cdot R_03}{1 + g_m 1 \cdot 2R_{out,cs}}} = \boxed{\frac{R_01 \cdot (1 + g_m 1 \cdot 2R_{out,cs})}{R_01 + R_03}}$$

(14)

Q5. The differential pair depicted in Fig 10.95 must provide a gain of 5 and a power budget of 4 mW. Moreover, the gain of the circuit must change by less than 2% if the collector current of either transistor changes by 10%. Assuming $V_{cc} = 2.5V$ and $R_A = \infty$, design the circuit. (Hint: 10% change in I_C leads to a 10% change in g_m)

$$V_{in,1} = V_{in,2} \text{ (DC degasser)}$$

R_E overdriven zekm element

$$V_{BE1} = V_{BE2} \text{ durch } b_1 = b_2$$

$$V_{B1} = V_{B2}$$

$$V_{cc}, 2I_{EE} = \text{DC power}$$

$$2.5 \cdot 2 I_{EE} \leq 4 \text{ mW}$$

$$I_{EE} \leq \frac{4}{5} \text{ mA} = 0.8 \text{ mA}$$

Differential mode half circuit


$$A_d = \frac{V_{out,1}}{V_{in,1}} = -\frac{g_m}{1 + g_m \frac{R_{EE} \cdot R_c}{2}}$$

$$g_m = \frac{I_{C1}}{V_T} = \frac{I_{EE}}{25 \text{ mV}}$$


$$A_d = 5 = \left| \frac{-\frac{I_{C1}}{V_T} \cdot R_c}{1 + \frac{I_{C1}}{V_T} \cdot \frac{R_{EE}}{2}} \right|$$

$$= \left| \frac{\Delta I_D}{I_D} \cdot \frac{I_c}{\Delta I_c} \right| \leq \frac{2}{10} \rightarrow \left| \frac{\Delta I_D}{\Delta I_c} \cdot \frac{I_c}{I_D} \right| \leq \frac{1}{5}$$
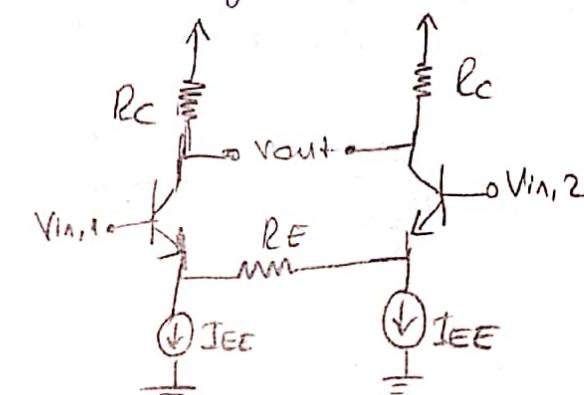
$$A_d = \frac{-2 I_c \cdot R_c}{2V_T + I_c \cdot R_{EE}}$$



$$I_{EE} \leq 0.8 \text{ mA}$$

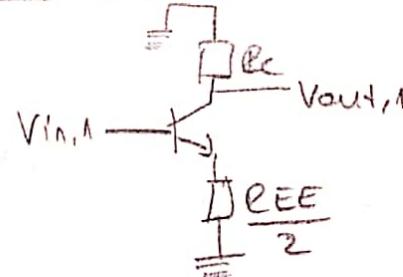

$$\left| \frac{\Delta I_D}{I_D} \right| \leq 2 \% \text{ oda mali}$$

$$\left| \frac{\Delta I_c}{I_c} \right| = 10 \% \text{ lek}$$

$$\left| \frac{\Delta I_D}{\Delta I_c} \cdot \frac{I_c}{I_D} \right| \leq \frac{1}{5}$$

$$\frac{\partial A_d}{\partial I_c} = -R_c \left[\frac{2 \cdot (2V_T + I_c \cdot R_{EE}) - R_{EE}(2I_{c1})}{(2V_T + I_c \cdot R_{EE})^2} \right]$$

(15)

$$\frac{\partial A_d}{\partial I_{C1}} = -R_C \left[\frac{4V_T + 2I_{C1}R_{EE} - R_{EE}2I_{C1}}{(2V_T + I_{C1}R_{EE})^2} \right] = \frac{-R_C \cdot 4V_T}{(2V_T + I_{C1}R_{EE})^2}$$

$$\begin{aligned} \frac{\partial A_d}{\partial I_{C1}} \cdot \frac{I_{C1}}{A_d} &= \frac{-R_C \cdot 4V_T}{(2V_T + I_{C1}R_{EE})^2} \cdot \left(\begin{array}{l} \frac{I_{C1}}{-R_C \cdot 2I_{C1}} \\ \frac{2V_T + I_{C1}R_{EE}}{4V_T} \end{array} \right) \\ &= \frac{-R_C \cdot 4V_T}{(2V_T + I_{C1}R_{EE})^2} \cdot \frac{(2V_T + I_{C1}R_{EE})}{-R_C} = \frac{4V_T}{2V_T + I_{C1}R_{EE}} = \frac{\partial A_d}{\partial I_{C1}} \cdot \frac{I_{C1}}{A_d} \end{aligned}$$

$$\left| \frac{\partial A_d}{\partial I_{C1}} \cdot \frac{I_{C1}}{A_d} \right| = \left| \frac{4V_T}{2V_T + I_{C1}R_{EE}} \right| \leq \frac{1}{5} \quad 20V_T \leq 2V_T + I_{C1}R_{EE}$$

$\frac{18V_T}{26mV} \leq \frac{I_{C1}R_{EE}}{I_{EE}R_{EE}}$

$\Rightarrow 468mV \leq I_{EE}R_{EE}$

$$I_{EE} \leq 0.8mA \quad 468mV \leq I_{EE}R_{EE}$$

$$|A_d| = \frac{2I_{EE} \cdot R_C}{2V_T + I_{EE}R_{EE}} = 5 \quad I_{EE} = 0.6mA \text{ iste}$$

$$468mV \leq 0.6mA \cdot R_{EE}$$

$$780\Omega \leq R_{EE}$$


$$R_{EE} = 800\Omega \text{ secalebilir.}$$

$$|A_d| = \frac{2 \cdot (0.6 \times 10^{-3}) R_C}{2 \cdot 26 \times 10^{-3} + (0.6 \times 10^{-3}) \cdot 800} = 5$$

$$2 = \frac{1.2 R_C \times 10^{-3}}{0.532} = 5 \rightarrow R_C = 2.216k\Omega$$

(16)

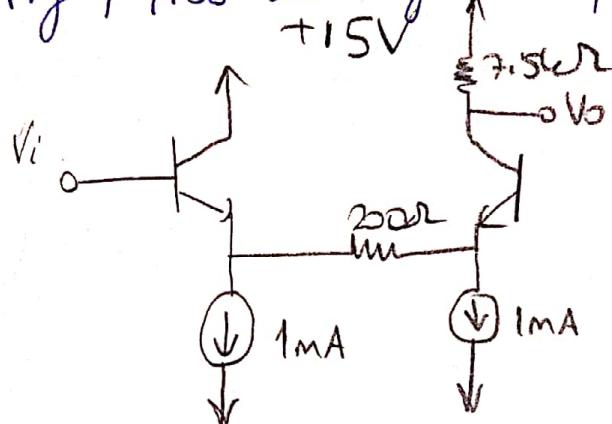Q6. Find the voltage gain and input resistance of the amplifier in fig P7.38 assuming that $\beta = 100$



DC biasing

$V_i = 0 \text{ V}$ ise (DC icin)

$Q_1 \text{ ve } Q_2 \text{ } V_i = 0 \text{ ise dengeli durumda}$


$$I_{C1} = I_{C2} = 1 \text{ mA}$$

$$g_m = \frac{I_{C1}}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} = 0.038 = g_{m1} \approx g_{m2}$$


$$r_{\pi 1} \approx r_{\pi 2} = \frac{\beta}{g_{m1}} = \frac{100}{0.038} = 2.6315 \text{ k}\Omega$$

small signal

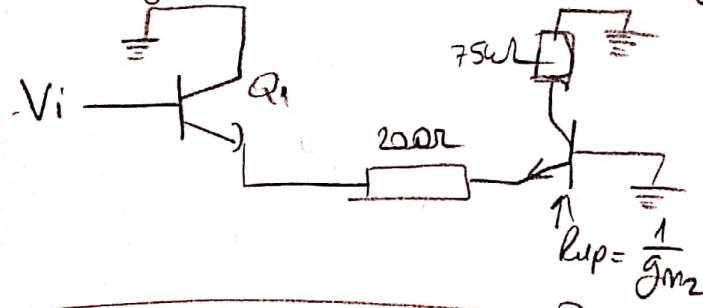small signalde kaskatikmis yapıda gerekli common collector ve base



Common Collector

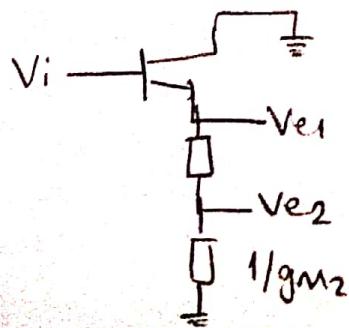

$$\frac{Ve_1}{Vi} \approx \frac{200\Omega + 1/gm_2}{200\Omega + 1/gm_2 + 1/gm_1} < 1$$

$$\frac{Ve_2}{Vi} = \frac{1/gm_2}{200\Omega + 1/gm_2}$$

$$\boxed{\frac{Ve_2}{Vi} = \frac{Ve_2}{Ve_1} \cdot \frac{Ve_1}{Vi} = \frac{1/gm_2}{200\Omega + 1/gm_2 + 1/gm_1}}$$

Eq. 10

(1)

Common Base

$$7.5k \quad \frac{V_{out}}{V_{e2}} = g_{m2} \approx 7.5 \text{ S} \quad V_{out} = g_{m2} \cdot 7.5 \text{ V}$$

$$\frac{V_e}{V_{i2}} = \frac{1/g_{m2}}{200 + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}} \rightarrow \text{eq.10}$$

$$\boxed{\frac{V_{out}}{V_i} = \frac{V_{out}}{V_{e2}} \cdot \frac{V_{e2}}{V_i} = \frac{\frac{1}{g_{m2}} \cdot 7.5 \text{ V}}{200 + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}}}$$

$$= \frac{7.5 \text{ V}}{200 + 25 + 25} =$$

$$= \frac{7.5 \text{ V}}{250} = \underline{\underline{30}}$$

$\frac{1}{1 \text{ mA}} = 25 \Omega$
 $\frac{1}{25 \text{ mV}} = 25 \text{ k}\Omega$

$$R_I = \left[1 + g_{m1} \left[200 + \frac{1}{g_{m2}} \right] \right] R_{T1}$$

$$= R_I = \left[1 + (g_{m1} \cdot 200 + 1) \right] R_{T1} = \underbrace{2\pi T_1}_{5 \text{ k}\Omega} + \underbrace{200g_{m1} \cdot \pi T_1}_{20 \text{ k}\Omega} \quad \beta, 2.25 = 100, 2.25 = 2500$$

β

$R_I = 25 \text{ k}\Omega$ bulunur